An Energy Efficient 1 Gb/s, 6-to-10 GHz CMOS IR-UWB Transmitter and Receiver With Embedded On-Chip Antenna

Zeshan Ahmad, Khaled Al-Ashmouny, Kuo-Ken Huang

EECS 522 Analog Integrated Circuits

(Winter'09)



OUTLINES

INTRODUCTION

- What and Why UWB?
- Comparison with other Schemes
- How can UWB open new application opportunities?

Overall System Architecture

Ultra-wideband Transmitter

- Data Modulation and Pulse Generation
- Fully-Integrated On-Chip Antenna
- Power Amplifier and FCC Mask Compliance

Ultra-wideband Receiver

- On-Chip Active Bandpass Filter
- Low-Power, Low-Noise Amplifier

Results and Comparison with Previous Work

Conclusions and Future Directions

Introduction

What is Impulse-Radio Ultra-Wideband (IR-UWB)?

- Short-range, High-Bandwidth Communication
- Bandwidth (BW): ٠
 - 3.1 10.6 GHz <-41.3 dBm/MHz Power Spectral Density Emission:
- Emitted Signal BW (-10dB): ٠







Why UWB?

•

- Low-Power, Low-cost (min RF electronics)
- Small Interference to other Narrow-band Systems (e.g WLAN, Wi-Fi) .



Introduction

Comparison with Others

• Example: for Bio-Implantable Devices

Group	Design	Frequency	Bandwidth	Data Rate	Energy/bit	Process	Size mm ²
Harrison' 04	FM	433 MHz	22 MHz	Test 300Hz	21.2 nJ/b	0.5 μm	1.29 mm ²
Najafi'05	FM	96.5 MHz	4 MHz	3-CH	N/A	1.5 μm	0.21 mm ²
Chae'08	OOK-PPM UWB	4.2 GHz	1 GHz	90 MHz	17 pJ/b	0.35 μm	N/A
Kuroda'09	BPSK UWB	6-10 GHz	4 GHz	750 MHz	41 pJ/b	0.18 μm	0.29 mm ²

New Applications?

- Low-power for more number of channels
- Less interference to other microsystem components
- Small, simple circuit for the transmission (*less area requirements*)
- Bio-Implants, Wireless Sensor Nodes, and Integrated Microsystems



Overall System Architecture



Overall System Architecture





IR-UWB Transmitter



Design Choices

- Frequency Band: 6-10GHz
- Why 6-10GHz?
 - Relatively Low Interference (WLAN Operates around 2.4/5.5GHz)
 - Relatively Narrow Bandwidth w.r.t. center frequency
- Modulation Scheme: BPSK
- Why BPSK?
 - No Discrete Spectra
 - 3-dB Higher Modulation Efficiency compared to PPM, PAM/OOK
- Pulse Generation and Shaping: Digital
- Why Digital?
 - Take Advantage of Technology Scaling
 - Any Downside?



Pulse Generation/Shaping





On-Chip Tapered Monopole Antenna

- Integration for short range communication
- Monopole topology
- Taper for broad bandwidth
- Matched to power amplifier

			An
	[1]	This Work	
f _c	9.0 GHz	7.7 GHz	out d th
Area	4.4 mm ²	0.30 mm ²	Green 1 h
Directivity	5 dBi	- 10 dBi	the Quant
Efficiency	0.6 % (-22 dB)	4.23 % (-13 dB)	liaidh
Bandwidth	2.2 GHz	4.0 GHz	





300 µm

4 mm



UWB Power Amplifier

Transformer feedback to increase bandwidth

$$Zin = \frac{gmLs}{Cgs} + j \left[\omega(Lg + Ls) - \frac{1}{\omega Cgs} \right]$$
$$Zin_{FB} = \frac{gm(Ls - M)}{Cgs} + j \left[\omega(Lg + 2Ls - 2M) - \frac{1}{\omega Cgs} \right]$$

 No additional output matching network for efficiency
2.0010.











IR-UWB Receiver



On-Chip Active Bandpass Filter

- On-chip solution for pre-select bandpass filter
- 3rd order shunt-type resonance capacitive coupled bandpass filter
- Efficient loss compensation for Qfactor boosting





Low-Power Low-Noise Amplifier

Schematic





Low-Power Low-Noise Amplifier

Schematic



Results and Performance Comparison with previous work



Simulation Result - UWB Power Amplifier

Group Delay of S21 – GD21 sec - S21 dB20 - S11 dB20 - S12 dB20 95.0-20.0 90.0-10.0-85.0-0-280.0 ଞ୍ଚି-10.0-ଅଞ୍ଚ ⊱-20.0-⊎ 9,75.0--30.0-70.0--40.0-65.0--50.0-60.0-6.0 7.0 8.0 9.0 10.0 11.0 5.0 7.0 5.0 6.0 8.0 9.0 10.0 11.0 freq (GHz) X0 (E9)

Reference	CMOS Tech.	Bandwidth	Avg. Gain	Avg. OP _{1dB}	Group Delay Variation	Power Consumption	Avg. PAE
[1]	0.18 μm	8 - 10 GHz	13.2 dB	N/A	N/A	20.0 mW	N/A
[8]	0.18 μm	3.1 – 4.8 GHz	19.0 dB	-4.2 dBm	N/A	25.0 mW	1.5 %
[9]	0.18 μm	6 - 10 GHz	8.5 dB	5.0 dBm	N/A	18.0 mW	14.4 %
This Work	0.13 μm	5.1 – 10.5 GHz	10.1 dB	0.1 dBm	18.6 % from 90 ps	4.2 mW	21.6 %

17



Simulation Result - UWB Transmitter



Transmitted Signal (w/o PA)







Simulation Result - Active Bandpass Filter



Bandwidth	Insertion Loss	Return loss	Noise Figure	Out-of-Band Attenuation	Power Consumption
3.9 GHz	2.9 dB	-11.2 dB	6.2 dB @ 7 GHz	30 dB @ 3 GHz 28 dB @ 13 GHz	0.4 mW



Simulation Result – LNA and Filter



S-parameters and NF of LNA only

S-parameters and NF of LNA + Filter



Reference	Technology	BW [GHz]	NF [dB]	S ₂₁ [dB]	S ₁₁ [dB]	llP3 [dBm]	Supply [V]	Power [mW]	Area [mm ²]
[10]	130 nm	3-5	3.5 - 5.5	6.4 - 9.5	< -10.0	- 0.8	1.2	16.5	~ 1.08
[11]	90 nm	0.5-5	2.3-2.6	21-22*	< -10.0	- 8.8	1.8	12.0	0.012
[12]	180 nm	6-10	4.8	11.6	<-9	1.2	1.8	11.6	0.81
This Work	130 nm	6.3-9.4	3.3-3.7	7-10	<-13	-6.8	1	2.56	0.51

University of Michigan

*Voltage Gain

Layout View of UWB Transmitter and Receiver



Results and Comparison with previous work

Parameter	[1]	[2]	[3]	[4]	This Work
Supply Voltage [V]	1.8-2.2	1	1.8	1	1.2 (Tx)/1(Rx)
Process Technology	180 nm	90 nm	180 nm	180 nm	130 nm
BW [GHz]	6 - 10	3.2 - 5	3.3 - 4.8	3.1 - 10	6 -10
Data Rate	750 Mb/s	10 Mb/s	1 Gb/s	1.8 Gb/s	1Gb/s
Modulation	BPSK	Delay-based BPSK	BPSK	BPSK	BPSK
Radiated Power [dBm/MHz]	-62.49	-42	-42	-42	-55
FOM [pJ/b]	41	47	108	126	7



Conclusions and Future Directions

Tailoring Designs up to what the application needs



Conclusion

- Low-power implementation of IR-UWB transmitter for short range (7 pJ/bit)
- Broadband power amplifier and on-chip antenna
- Transmitter can be a part of fully-integrated wireless microsystems
- Low-power, low-noise analog front-end for IR-UWB receiver
- On-chip active bandpass filter reducing the Impact of out band interferers
- The performances of all implemented blocks is comparable and outperforms state-of-the-art publications
- Future work should include implementing the remaining blocks (inc PLL) as well as testing the real chip performance



References

- 1. V.V. Kulkarni, M. Muqsith, K. Niitsu, H. Ishikuro, and T. Kuroda, "A 750Mb/s, 12pJ/b, 6-10GHz IR-UWB Transmitter with Embedded On-Chip Antenna," IEEE JSSC, vol. 44, no. 2, pp, 394-403, February 2009.
- 2. D. D. Wentzloff et al., "A 47 pJ/pulse 3.1-to-5GHz all-digital UWB transmitter in 90nm CMOS," IEEE ISSSC Dig. Tech. Papers, pp. 118-119, February 2007.
- 3. A. Medi, W. Namgoong, "A high data-rate Energy-Efficient Interference-Tolerant Fully Integrated CMOS Frequency Channelized UWB Transceiver for Impulse Radio," IEEE JSSC, vol. 43, no. 4, pp, 974-980, April 2008.
- 4. M. Demirkan et al., "A 1.8 Gpulses/s UWB transmitter in 90nm CMOS," IEEE ISSSC Dig. Tech. Papers, pp. 114-115, February 2008.
- 5. M. L. Welborn, "System Considerations for Ultra-Wideband Wireless Networks," IEEE Radio and Wireless Conference, August 2001.
- 6. H. Kim, D. Park and Y. Joo, "All-digital low-power CMOS pulse generator for UWB system," IEE Electronic Letters, vol. 40, no. 24, November 2004.
- 7. J. Ryckaert, G. Van der Plas, V. De Heyn, C. Desset, B. Van Poucke, J. Craninckx, "A 0.65-to-1.4 nJ/Burst 3-to-10 GHz UWB All-Digital TX in 90 nm CMOS for IEEE 802.15.4a," IEEE JSSC, vol. 42, no. 12, pp. 2860-2869, December 2007.
- 8. S. Jose, H-Jin Lee and D. Ha, S. S. Choi, "A low power CMOS Power Amplifier for Ultra wideband (UWB) Applications," IEEE Symp. on Circ. and Sys., vol. 5, pp.5111-5114, May 2005.
- 9. H. –W. Chung, C.-Y. Hsu, C.-Y Yang, K.-F. Wei, and H.–R. Chuang, "A 6-10GHz CMOS Power Amplifier with an Interstage Wideband Impedance Transformer For UWB Transmitters," 38th EuMC, October 2008.
- 10. A. Bevilacqua, et al., "A Fully Integrated Differential CMOS LNA for 3–5-GHz Ultrawideband Wireless Receivers," IEEE Microwave and Wireless Components Letters, vol. 16, no. 3, pp. 134-136, March 2006.
- B. G. Perumana, J.-H. C. Zhan, S. S. Taylor, and J. Laskar, "A 12 mW, 7.5 GHz bandwidth, inductor-less CMOS LNA for low-power, lowcost, multi-standard receivers," in Proc. IEEE Radio Frequency Integrated Circuits Symp., Honolulu, HI, Jun. 2007, pp. 57–60.
- 12. Y.-C. Chen and C.-N. Kuo, "A 6-10-GHz Ultra-Wideband Tunable LNA," in Proc. IEEE Intl. Symp. Cir. and Sys., May 2005, pp. 5099– 5102.



Thank you Questions?



Overall System Architecture

