
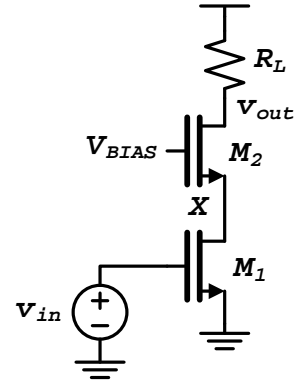


**University of Michigan**  
**EECS 522: Analog Integrated Circuits**  
**Winter 2009**

Problem Set 3


Issued 2/4/2009 – Due 2/18/2009

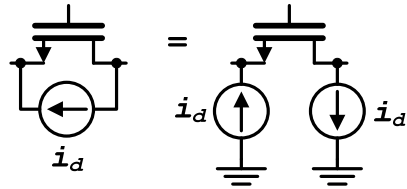**Problem 3.1:** Use the circuit to the right for this problem. Ignore channel length modulation ( $\lambda = 0$ ). All devices are in saturation. Consider only drain thermal noise in the FETs (no thermal noise in  $R_L$ ). Find an expression for the input referred noise voltage neglecting induced gate noise. How does  $M_2$  affect the noise contributed by the circuit? Hint: the following circuit transformation may be useful.



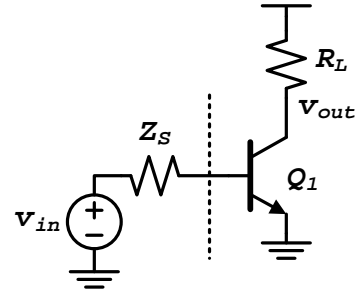**Problem 3.2:** Use the circuit to the right for this problem. Assume the BJT is in the forward active region, ignore  $r_o$  and  $r_b$ . Consider only shot noise in the collector and base (no thermal noise in  $R_L$ ). Assume  $\beta$  is constant with frequency.

- Derive expressions for the input-referred short-circuit noise voltage and open-circuit noise current (not including  $Z_S$ ).
- Derive an expression for the correlation admittance  $Y_c$ .
- Derive expressions for the 4 noise parameters  $G_c$ ,  $B_c$ ,  $R_n$ , and  $G_u$ .
- Find the source impedance resulting in minimum noise factor and evaluate it assuming  $I_{C1} = 1\text{mA}$  and  $\beta_F = 100$ .



**Problem 3.3:** Suppose you have a choice between two amplifiers, both having  $10\text{nV}/\sqrt{\text{Hz}}$  input noise voltage density; however, amplifier A has  $50\text{fA}/\sqrt{\text{Hz}}$  input noise current density and amplifier B has  $100\text{fA}/\sqrt{\text{Hz}}$ .

- What is the optimum source resistance (resulting in lowest noise factor) for each amplifier? Assume the input noise sources are uncorrelated.
- If the source resistance is  $100\text{k}\Omega$ , which amplifier should you use for lowest noise?
- For your choice in part b), what is the noise factor?

**Problem 3.4:** Find expressions for the mean-square input referred short-circuit noise voltage and open-circuit noise current for the following circuits. You may neglect  $r_o$  and  $g_{mb}$ , and  $r_b$ . Include only drain noise in FET's, thermal noise in  $R$ 's, and base and collector shot noise in BJT's.

