
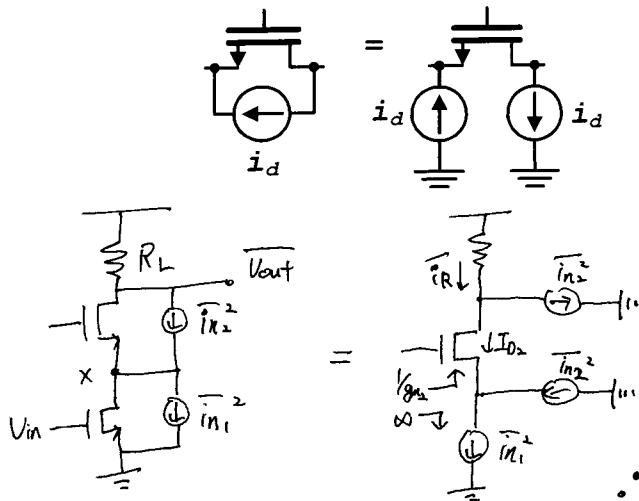


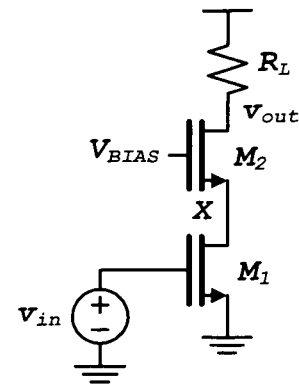Problem 3.1: Use the circuit to the right for this problem. Ignore channel length modulation ($\lambda = 0$). All devices are in saturation. Consider only drain thermal noise in the FETs (no thermal noise in R_L). Find an expression for the input referred noise voltage neglecting induced gate noise. How does M_2 affect the noise contributed by the circuit? Hint: the following circuit transformation may be useful.



KCL

$$\bar{i}_R - \bar{i}_{n2} = I_{D2} = \bar{i}_{n1} - \bar{i}_{n2}$$

$$\therefore \bar{i}_R = \bar{i}_{n1}$$


$$\therefore \overline{v_{out,n}}^2 = \bar{i}_{n1}^2 R_L^2 = 4kT \gamma g_{m1} R_L^2 \Delta f$$

Input-referred noise:



$$\overline{v_{in,n}}^2 = \frac{\overline{v_{out,n}}^2}{A_v^2} = \frac{4kT \gamma g_{m1} R_L^2}{g_{m1}^2 R_L^2} \Delta f$$

$$\therefore \frac{\overline{v_{in,n}}^2}{\Delta f} = 4kT \gamma \frac{1}{g_{m1}} \Rightarrow M_2 \text{ does not affect the noise.}$$

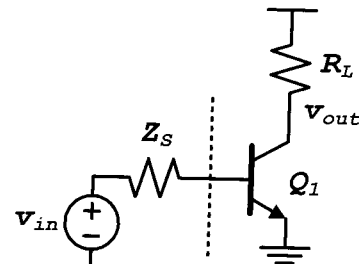Problem 3.2: Use the circuit to the right for this problem. Assume the BJT is in the forward active region, ignore r_o and r_b . Consider only shot noise in the collector and base (no thermal noise in R_L). Assume β is constant with frequency.



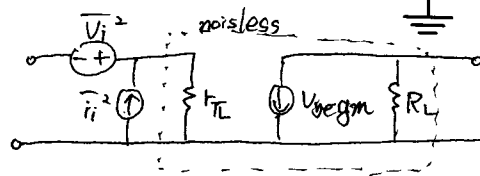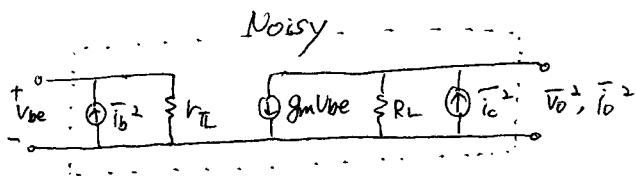- a) Derive expressions for the input-referred short-circuit noise voltage and open-circuit noise current (not including Z_S).



To get $\overline{v_i}^2$, short both inputs (noisy and noisless)

$$\overline{v_o}^2 = [(g_m V_{be})^2 + \bar{i}_c^2] R_L^2, \quad V_{be} = 0$$

$$\overline{v_o}^2 = \bar{i}_c^2 R_L^2$$

$$\overline{v_i}^2 = \frac{\overline{v_o}^2}{A_v^2} = \frac{\bar{i}_c^2 R_L^2}{g_m^2 R_L^2} = \frac{\bar{i}_c^2}{g_m^2} = \frac{2qI_c \Delta f}{g_m^2}$$

$$\boxed{\frac{\overline{v_i}^2}{\Delta f} = 2qI_c \frac{1}{g_m^2}}$$

To get $\bar{i}_i^2$, open both inputs

$$\bar{i}_o^2 = (g_m V_{be})^2 + \bar{i}_c^2$$

$$\bar{i}_o^2 = g_m^2 \bar{i}_b^2 h_{\pi}^2 + \bar{i}_c^2$$

$$\bar{i}_o^2 = (g_m V_{be})^2 = (g_m \bar{i}_i h_{\pi})^2$$

$$\therefore g_m^2 \bar{i}_i^2 h_{\pi}^2 = g_m^2 \bar{i}_b^2 h_{\pi}^2 + \bar{i}_c^2$$

$$\bar{i}_i^2 = \bar{i}_b^2 + \frac{\bar{i}_c^2}{g_m^2 h_{\pi}^2} = \bar{i}_b^2 + \frac{\bar{i}_c^2}{\beta^2}$$

$$\bar{i}_i^2 = 2q(I_B + \frac{I_c}{\beta}) \Delta f = 2q(I_B + \frac{I_c}{\beta}) \Delta f$$

$$\boxed{\frac{\bar{i}_i^2}{\Delta f} = 2qI_B \frac{\beta+1}{\beta}}$$

b) Derive an expression for the correlation admittance Y_c .

$$i_c = \frac{\bar{i}_c}{g_m r_\pi}, \quad v_i = \frac{\bar{i}_c}{g_m}$$

$$Y_c = \frac{i_c}{v_i} = \boxed{\frac{1}{r_\pi}}$$

c) Derive expressions for the 4 noise parameters G_c , B_c , R_n , and G_u .

$$R_n = \frac{\bar{v}_i^2}{4kT\Delta f} = \frac{2qI_c \frac{1}{g_m^2} \Delta f}{4kT\Delta f} = \frac{1}{2} \left(\frac{q}{kT} \right) I_c \frac{1}{g_m^2} = \frac{1}{2} \frac{I_c}{V_T} \cdot \frac{1}{g_m^2} = \frac{1}{2g_m^2}$$

$$Y_c = G_c + jB_c \Rightarrow G_c = \frac{1}{r_\pi}, \quad B_c = 0$$

$$G_u = \frac{\bar{i}_b^2}{4kT\Delta f} = \frac{2qI_B \Delta f}{4kT\Delta f} = \frac{1}{2} \left(\frac{q}{kT} \right) I_B = \frac{g_m}{2\beta}$$

d) Find the source impedance resulting in minimum noise factor and evaluate it assuming $I_{C1} = 1\text{mA}$ and $\beta_F = 100$.

$$B_{S,opt} = -B_c = 0$$

$$G_{S,opt} = \sqrt{\frac{G_u}{R_n} + G_c^2} = \sqrt{\frac{I_B}{I_c} g_m^2 + \frac{1}{r_\pi^2}}$$

$$G_{S,opt} = \sqrt{\frac{g_m}{r_\pi} + \frac{1}{r_\pi^2}} = \sqrt{\frac{I_c^2}{V_T^2} \cdot \frac{1}{\beta} + \frac{1}{\beta^2} \cdot \frac{I_c^2}{V_T^2}}$$

$$= 0.004$$

Problem 3.3: Suppose you have a choice between two amplifiers, both having $10\text{nV}/\sqrt{\text{Hz}}$ input noise voltage density; however, amplifier A has $50\text{fA}/\sqrt{\text{Hz}}$ input noise current density and amplifier B has $100\text{fA}/\sqrt{\text{Hz}}$.

a) What is the optimum source resistance (resulting in lowest noise factor) for each amplifier? Assume the input noise sources are uncorrelated.


$$Y_s = G_{S,opt} = \sqrt{\frac{G_u}{R_n} + G_c^2}, \quad G_c = 0$$

$$G_u = \frac{\bar{i}_i^2}{4kT\Delta f}, \quad R_n = \frac{\bar{v}_i^2}{4kT\Delta f}$$

$$Y_s = \sqrt{\frac{\bar{i}_i^2}{\bar{v}_i^2}} \Rightarrow R_s = \frac{\bar{v}_i}{\bar{i}_i}$$

$$R_{sA} = \frac{10\text{n}}{50\text{f}} = \boxed{200\text{ k}\Omega}, \quad R_{sB} = \frac{10\text{n}}{100\text{f}} = \boxed{100\text{ k}\Omega}$$

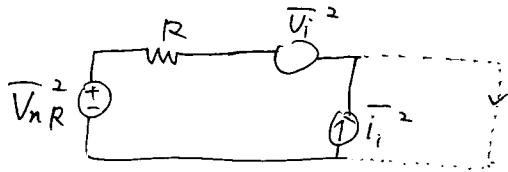b) If the source resistance is 100kΩ, which amplifier should you use for lowest noise?



$$F = \frac{\frac{\overline{V_{nR}^2} + \overline{V_i^2}}{R^2} + \overline{i_i^2}}{\frac{\overline{V_{nR}^2}}{R^2}} = \frac{\overline{V_{nR}^2} + \overline{V_i^2} + \overline{i_i^2} R^2}{\overline{V_{nR}^2}}$$

$$F = 1 + \frac{\overline{V_i^2}}{\overline{V_{nR}^2}} + \frac{\overline{i_i^2} R^2}{\overline{V_{nR}^2}} = 1 + \frac{\overline{V_i^2}}{4kTR\Delta f} + \frac{\overline{i_i^2} R}{4kT\Delta f}$$

→ For Amp A,

$$R_{SA} = 200 \text{ k}\Omega$$

$$F = 1 + \frac{(10 \text{ nV})^2}{4 \cdot 1.38 \cdot 10^{-23} \cdot 300 \cdot 200 \text{ k}} + \frac{(50 \text{ f})^2 \cdot 1200 \text{ k}}{4 \cdot 1.38 \cdot 10^{-23} \cdot 300}$$

$$= 1.076$$

→ For Amp B,

$$F = 1 + \frac{(10 \text{ nV})^2}{4 \cdot 1.38 \cdot 10^{-23} \cdot 300 \cdot 100 \text{ k}} + \frac{(100 \text{ f})^2 \cdot 100 \text{ k}}{4 \cdot 1.38 \cdot 10^{-23} \cdot 300}$$

$$= 1.121$$


Therefore Amplifier A is the better option.

c) For your choice in part b), what is the noise factor?

From part b), F = 1.076

Problem 3.4: Find expressions for the mean-square input referred short-circuit noise voltage and open-circuit noise current for the following circuits. You may neglect r_o and g_{mb} , and r_b . Include only drain noise in FET's, thermal noise in R's, and base and collector shot noise in BJT's.

a)

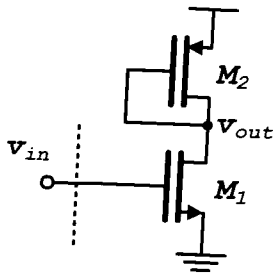


$$\overline{V_{out}}^2 = 4kT(\delta_n g_{m1} + \delta_p g_{m2}) \left(\frac{1}{g_{m2}} \right)^2 \Delta f$$

$$\overline{V_{in}}^2 = \frac{\overline{V_{out}}^2}{A_v^2}, \quad A_v = -\frac{g_{m1}}{g_{m2}}$$

$$\frac{\overline{V_{in}}^2}{\Delta f} = 4kT(\delta_n g_{m1} + \delta_p g_{m2}) \frac{1}{g_{m1}^2}$$

$$\frac{\overline{I_{in}}^2}{\Delta f} = \frac{\overline{V_{in}}^2}{Z_{in}^2} \frac{1}{\Delta f} = \omega^2 C_{gs}^2 \cdot 4kT(\delta_n g_{m1} + \delta_p g_{m2}) \frac{1}{g_{m1}^2}$$

b)

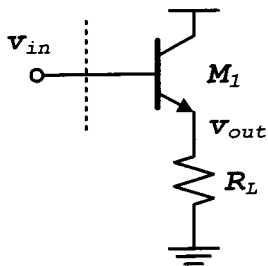

$$V_{out}|_{V_{in}=0} = (i_b + i_c + i_{R_L}) \cdot \left(\frac{1}{g_m} \parallel R_L \parallel \frac{1}{j\omega C_{\pi}} \right)$$

$$\overline{V_{out}}^2 = (\overline{i_b}^2 + \overline{i_c}^2 + \overline{i_{R_L}}^2) \left(\frac{R_L}{1 + g_m R_L + j\omega C_{\pi} R_L} \right)^2$$


$$A_v = 1 \quad V_{out} \approx V_{in} \Rightarrow \overline{V_{in}}^2 = \overline{V_{out}}^2$$

$$\frac{\overline{V_{in}}^2}{\Delta f} = \left(2qI_B + 2qI_C + \frac{4kT}{R_L} \right) \cdot \left(\frac{R_L}{1 + g_m R_L + j\omega C_{\pi} R_L} \right)^2$$

$$= \frac{2qR_L^2 I_C \left(\frac{1}{H_{\beta}} \right) + 4kTR_L}{(1 + g_m R_L)^2 + \omega^2 R_L^2 C_{\pi}^2}$$

$$\frac{\overline{I_{in}}^2}{\Delta f} = \left| R_L + R_L \parallel \frac{1}{j\omega C_{\pi}} + R_L g_m \cdot R_L \parallel \frac{1}{j\omega C_{\pi}} \right|^2 \cdot \frac{2qR_L^2 I_C \left(\frac{1}{H_{\beta}} \right) + 4kTR_L}{(1 + g_m R_L)^2 + \omega^2 R_L^2 C_{\pi}^2}$$

c)

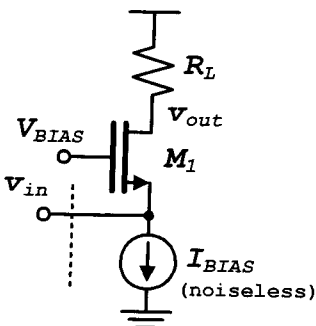

$$\overline{V_{out}}^2 = \left[4kT \delta g_m + 4kT \frac{1}{R_L} \right] R_L^2$$

$$A_v^2 = (g_m + g_{mb})^2 R_L^2 \approx g_m^2 R_L^2$$

$$\overline{V_{in}}^2 = \frac{\overline{V_{out}}^2}{A_v^2} = (4kT \delta g_m + 4kT \frac{1}{R_L}) \frac{\Delta f}{g_m^2}$$

$$\Rightarrow \frac{\overline{V_{in}}^2}{\Delta f} = 4kT \left(\delta g_m + \frac{1}{R_L} \right) \left(\frac{1}{g_m^2} \right)$$

$$\frac{\overline{I_{in}}^2}{\Delta f} = \left(\omega^2 C_{gs}^2 + \frac{1}{g_m^2} \right) 4kT \left(\delta g_m + \frac{1}{R_L} \right) \frac{1}{g_m^2}$$