


**Problem 6.1:** Use the common-gate amplifier below for this problem. Use the combined model for drain and gate noise,  $\overline{i_{ndg}^2}$ , derived in lecture, making the same assumptions on the small-signal model (no  $r_o$ , include  $C_{gs}$ , etc.). Assume  $C_{BIG}$  is a short at AC, and the circuit is operated at the self-resonant frequency  $\omega_0 = 1/\sqrt{L_S(C_S + C_{gs})}$ .

- a) What is the small-signal transconductance  $G_m = i_{out}/v_{in}$  of the circuit at  $\omega = \omega_0$  assuming the transistor is biased so that  $1/g_m = R_S$ .

$$V_S = V_{in} \cdot \frac{\frac{1}{g_m} // sL_S // \frac{1}{s(C_{gs} + C_S)}}{R_S + \frac{1}{g_m} // sL_S // \frac{1}{s(C_{gs} + C_S)}}$$

$$= V_{in} \cdot \frac{\frac{1}{g_m}}{R_S + \frac{1}{g_m}} = \frac{1}{2} V_{in}$$
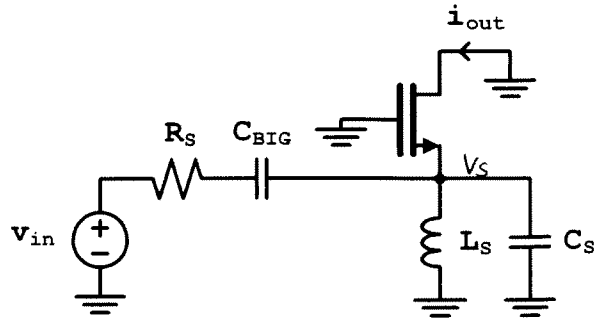
$$i_{out} = g_m \cdot (0 - V_S) = g_m \cdot -\frac{1}{2} V_{in} \quad \therefore G_m = \frac{i_{out}}{V_{in}} = -\frac{1}{2} g_m$$



- b) Derive expressions for  $\eta$  and  $Z_{gs}$  for the combined drain and gate noise,  $\overline{i_{ndg}^2}$ .

$$Z_{gs} = \frac{1}{sC_{gs}} // \frac{Z_{deg} + Z_g}{1 + g_m Z_{deg}}$$

$$\cdot Z_g = 0 \quad \cdot Z_{deg} = R_S // sL_S // \frac{1}{sC_S} = \frac{1}{\frac{1}{R_S} + \frac{1}{j\omega L_S} + j\omega C_S} = \frac{j\omega L_S R_S}{R_S - \omega^2 C_S L_S R_S + j\omega L_S}$$

$$\therefore Z_{gs} = \frac{1}{j\omega C_{gs} + \frac{R_S - \omega^2 C_S L_S R_S + j\omega L_S}{j\omega L_S R_S}} = \frac{j\omega L_S R_S}{- \omega^2 C_S L_S R_S + R_S - \omega^2 C_S L_S R_S + j\omega L_S + j\omega L_S \cdot R_S g_m} = \frac{j\omega L_S R_S}{2j\omega L_S} = \frac{R_S}{2}$$

$$\eta = 1 - \frac{g_m Z_{deg}}{Z_{deg} + Z_g} \cdot Z_{gs} = 1 - g_m \frac{R_S}{2} = \frac{1}{2} \quad (\because 1/g_m = R_S)$$

$$Z_{gs} = \omega C_{gs} Z_{gs} = \frac{\omega C_{gs} R_S}{2}$$

$$\overline{i_{ndg}^2} = \overline{i_{nd}^2} (|H|^2 + 2 \operatorname{Re} \{ c \chi_d \chi^* Z_{gs} \omega \}) + \chi_d^2 (Z_{gs} \omega)^2 = \overline{i_{nd}^2} \left( \frac{1}{4} + \chi_d^2 \cdot \frac{R_S^2}{4} \cdot \omega^2 C_{gs}^2 \right)$$

- c) Derive an expression for the noise factor of the amplifier using your results from b).


$$F = \frac{\overline{e_n^2} \cdot (-\frac{1}{2} g_m)^2 + \overline{i_{nd}^2} \left( \frac{1}{4} + \chi_d^2 R_S^2 \omega^2 C_{gs}^2 / 4 \right)}{\overline{e_n^2} \cdot (-\frac{1}{2} g_m)^2} = 1 + \frac{4kT\delta g_{d0} (\frac{1}{4} + \chi_d^2 R_S^2 \omega^2 C_{gs}^2 / 4)}{4kT\Delta f R_S \cdot \frac{1}{4} g_m^2} = 1 + \frac{\delta}{\alpha} + \frac{\alpha \delta \omega^2 C_{gs}^2}{5 g_m^2}$$

- d) Assuming  $c$  is negative and imaginary,  $\omega = \omega_0 = 1/\sqrt{L_S(C_S + C_{gs})}$ ,  $Q_{in} = \frac{1}{2} R_S (C_S + C_{gs}) \omega_0$ , and  $\omega_t = g_m / C_{gs}$ , simplify your expression from c) into a form containing these quantities and device constants.

$$F = 1 + \frac{\delta}{\alpha} + \frac{\alpha \delta}{5} \frac{\omega_0^2}{\omega_t^2}$$

**Problem 6.2:** Use the amplifier below for this problem. Consider only  $C_{gs}$  and  $g_m$  for the FET, neglect all other small signal parameters. Assume the input and output resonances are tuned to 1GHz, and that  $C_{BIG}$  is a short circuit at 10GHz.

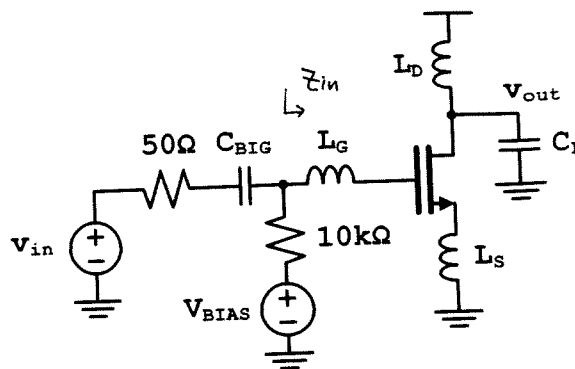- a) Assume that  $Q=10$  for all inductors at 1GHz, and the inductors are modeled as a series R and L. Given that  $\omega_t = 2\pi \cdot 3.2 \text{ GHz}$  and  $g_m = 10 \text{ mho}$ , calculate the values of  $L_G$  and  $L_S$  to provide a  $50\Omega$  match to the source.



$$\omega_t = 2\pi \cdot 3.2 \cdot 10^9 = \frac{g_m}{C_{gs}}$$

$$C_{gs} = \frac{10 \times 10^{-3}}{2\pi \cdot 3.2 \times 10^9}$$

$$Z_m = j\omega L_G + \frac{\omega L_G}{Q} + \frac{1}{j\omega C_{gs}} + \frac{j\omega C_{gs} + g_m}{j\omega C_{gs}} \cdot (j\omega L_S + \frac{\omega L_S}{Q})$$

$$= (\frac{\omega L_G}{Q} + \frac{\omega L_S}{Q} + \frac{g_m}{C_{gs}} L_S) + j(\omega L_G + \omega L_S - \frac{1}{\omega C_{gs}} - \frac{g_m L_S}{C_{gs} Q})$$

" 0

$$\begin{cases} \frac{\omega}{Q} (L_G + L_S) + \omega L_S = 50 & (1) \\ \omega (L_G + L_S) - \frac{1}{\omega C_{gs}} - \frac{\omega}{Q} L_S = 0 & (2) \end{cases}$$

by (1), (2)  $L_G = 50.34 \text{ nH}$ ,  $L_S = 0.886 \text{ nH}$

- b) Assuming  $V_{GS} - V_{th} = 150 \text{ mV}$ , calculate the bias current in the FET and the voltage drop across  $L_S$ .

$$I_D = \frac{1}{2} g_m \cdot (V_{GS} - V_{th}) = \frac{1}{2} \cdot 10 \text{ m} \cdot 150 \text{ m} = 0.75 \text{ mA}$$

$$R_{L_S} = \frac{\omega L_S}{Q} = \frac{2\pi \cdot 10^9 \cdot 0.886 \text{ nH}}{10} = 0.5567 \Omega$$

$$V_{L_S} = I_D \cdot R_{L_S} = 0.4175 \text{ mV}$$

- c) Assume this amplifier is loaded by an identical FET, therefore  $C_L = C_{gs}$ . Calculate the value of  $L_D$  required to resonate out this capacitance at 1GHz. Is this a reasonable value?

$$\omega_0 = \frac{1}{\sqrt{L_D C_{gs}}} \Rightarrow L_D = \frac{1}{\omega_0^2 C_{gs}} = \frac{1}{\omega_0^2 \cdot \frac{g_m}{\omega_t}} = 50.93 \text{ nH}$$

- d) What is the overall voltage gain of your amplifier at 1GHz? Provide a numerical value (still neglecting  $r_o$  of the FET) with  $Q=10$  for all inductors at 1GHz.

$$A_v(\omega_0) = -g_m \cdot Z_{out}(\omega_0)$$

$$= -g_m (1+Q^2) R_{L0} \cdot Q_{in}$$

$$= -g_m (1+Q^2) \frac{\omega_0 L_0}{Q} \cdot Q_{in}$$

$$\approx -103.42 \text{ V/V} \quad \left( Q_{in} = \frac{1}{2\omega_0 C_{gs} R_s} = 3.2 \right)$$

- e) What is the noise factor of your amplifier. Assume  $\gamma = 3$ ,  $\delta = 6$ ,  $\alpha = 0.75$ , and  $c = -0.55j$ .



$$\chi_d = \alpha \sqrt{\frac{\delta}{\gamma \delta}} \approx 0.494, \quad Q_{in} = \frac{1}{2\omega_0 C_{gs} R_s} \approx 3.2$$

$$F = 1 + \frac{\omega_0}{\omega_t} \cdot \frac{\gamma}{\alpha} \cdot \frac{1}{2Q_{in}} (1 - 2|c|\chi_d + (4Q_{in}^2 + 1)\chi_d^2)$$

$$= 2.936$$

$$NF = 4.68 \text{ dB}$$

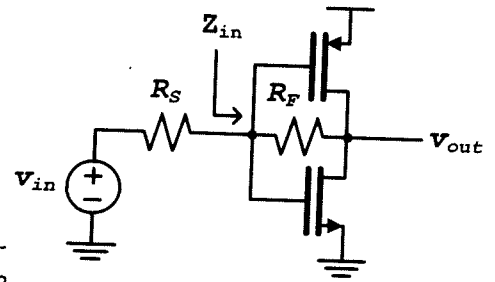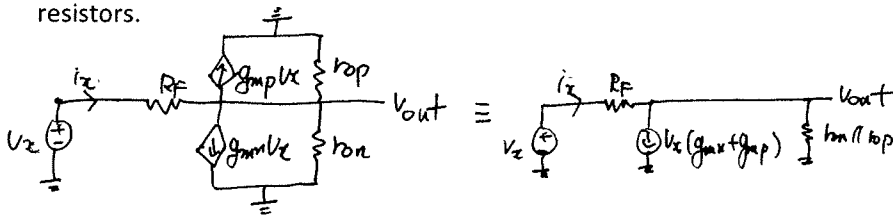**Problem 6.3:** Derive expressions for the input impedance  $Z_{in}$ , voltage gain  $v_{out}/v_{in}$ , and noise factor of the following circuit seen in lecture. Consider only drain thermal noise and thermal noise in the resistors.



$$V_{out} = - \frac{R_F}{R_F + r_{on} \parallel r_{op}} \cdot (g_{mn} + g_{mp}) v_x \cdot r_{op} \parallel r_{on} + v_x \cdot \frac{r_{on} \parallel r_{op}}{R_F + r_{on} \parallel r_{op}}$$

$$I_x = v_x \cdot (g_{mn} + g_{mp}) + \frac{V_{out}}{r_{on} \parallel r_{op}} = v_x (g_{mn} + g_{mp}) - \frac{R_F}{R_F + r_{on} \parallel r_{op}} v_x (g_{mn} + g_{mp}) + \frac{v_x}{R_F + (r_{on} \parallel r_{op})}$$


$$\cdot Z_{in} = \frac{v_x}{I_x} = \frac{1}{g_{mn} + g_{mp} - \frac{R_F (g_{mn} + g_{mp})}{R_F + r_{on} \parallel r_{op}} + \frac{1}{R_F + r_{on} \parallel r_{op}}}$$

$$\approx \frac{1}{g_{mn} + g_{mp}} \quad \text{for } r_{on} \parallel r_{op} \gg R_F$$

$$\cdot A_v = \frac{V_{out}}{V_{in}} = \frac{v_x}{V_{in}} \cdot \frac{V_{out}}{v_x} = \frac{Z_{in}}{R_s + Z_{in}} (-R_F (g_{mn} + g_{mp}) + 1) \cdot \frac{r_{on} \parallel r_{op}}{R_F + (r_{on} \parallel r_{op})}$$

$$\approx \frac{-\frac{g_{mn} + g_{mp}}{R_s + \frac{1}{g_{mn} + g_{mp}}} \cdot -R_F (g_{mn} + g_{mp})}{1 + (g_{mn} + g_{mp}) R_s} = - \frac{(g_{mn} + g_{mp}) \cdot R_F}{1 + (g_{mn} + g_{mp}) R_s}$$

: Noise Factor

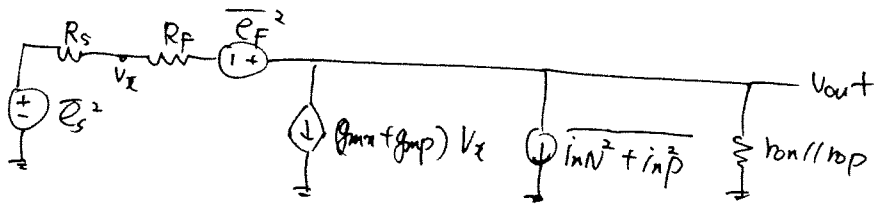

Find  $\frac{V_{out}}{e_F}$  : ignore other source.

KCL at  $V_{out}$ :

$$\frac{V_{out} - e_F}{R_s + R_F} + (g_{mn} + g_{mp}) \cdot (V_{out} - e_F) \cdot \frac{R_s}{R_s + R_F} + \frac{V_{out}}{r_{on} || r_{op}} = 0$$

$$\Rightarrow \frac{V_{out}}{e_F} = \left( \frac{1 + (g_{mn} + g_{mp}) R_s}{R_s + R_F} + \frac{1}{r_{on} || r_{op}} \right) / \frac{1 + (g_{mn} + g_{mp}) R_s}{R_s + R_F}$$

$$= 1 + \frac{R_s + R_F}{(1 + (g_{mn} + g_{mp}) R_s) \cdot r_{on} || r_{op}} \approx 1$$

Total Noise,  $\overline{e_{total}^2} = A_v^2 \cdot \overline{e_s^2} + \overline{e_F^2} + (\overline{i_{nN}^2} + \overline{i_{nP}^2}) \cdot \left( (R_s + R_F) || r_{on} || r_{op} \right) \cdot \frac{R_s + R_F}{R_s} \cdot \frac{1}{g_{mn} + g_{mp}}$

$$\therefore F = \frac{A_v^2 \cdot \overline{e_s^2} + \overline{e_F^2} + (\overline{i_{nN}^2} + \overline{i_{nP}^2}) \cdot R_F^2 / (1 + (g_{mn} + g_{mp}) R_s)^2}{A_v^2 \cdot \overline{e_s^2}}$$

$$= 1 + \frac{\frac{4kT \Delta f R_F}{(g_{mn} + g_{mp})^2 R_F^2} + \frac{4kT \Delta f (\sigma_n g_{don} + \sigma_p g_{dop}) \cdot R_F^2}{(1 + (g_{mn} + g_{mp}) R_s)^2}}{4kT \Delta f R_s}$$

$$= 1 + \frac{(1 + (g_{mn} + g_{mp}) R_s)^2}{(g_{mn} + g_{mp})^2 \cdot R_s R_F} + \frac{\sigma_n g_{don} + \sigma_p g_{dop}}{(g_{mn} + g_{mp})^2 R_s}$$

if input is matched, i.e.  $\frac{1}{g_{mn} + g_{mp}} = R_s$

$$F = 1 + \frac{4}{(g_{mn} + g_{mp})^2 \cdot R_s R_F} + \frac{1}{(g_{mn} + g_{mp}) R_s} \cdot \frac{\sigma_n g_{don} + \sigma_p g_{dop}}{g_{mn} + g_{mp}}$$


$$= 1 + \frac{4}{(g_{mn} + g_{mp}) R_F} + \frac{\sigma_n g_{don} + \sigma_p g_{dop}}{g_{mn} + g_{mp}}$$

**Problem 6.4:** Use the cascode LNA shown below.


- a) Derive an expression for the output-referred short-circuit noise current contributed from the drain thermal noise of transistor M2 neglecting  $r_o$  for both devices.

$$\overline{i_o^2} = \overline{i_{n2}^2} \cdot \left| \frac{\frac{1}{g_{m2}}}{s(C_p + (g_{s2})) + \frac{1}{g_{m2}}} \right|^2$$

$$\overline{i_o^2} = 4kT(\gamma_2 g_{d2}) \cdot \left| \frac{s(C_p + (g_{s2}))}{sC_p + (g_{s2}) + g_{m2}} \right|^2$$

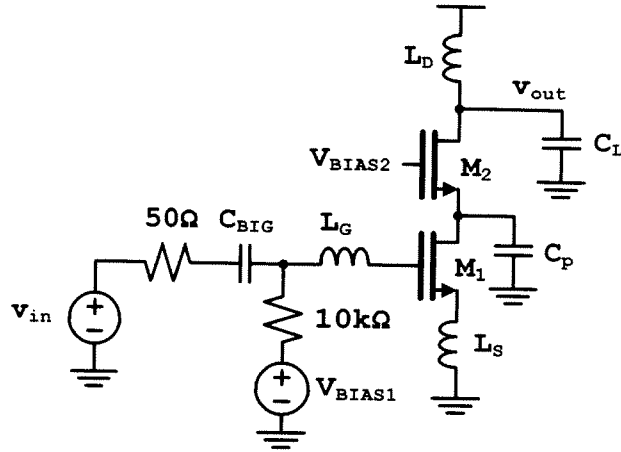

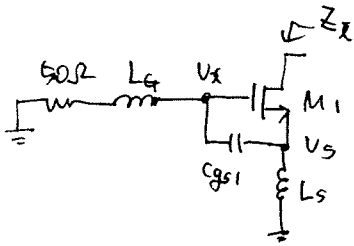- b) Now including  $r_{o1}$ , what is the impedance seen looking into the drain of M1 at the resonant frequency of the input matching circuit? Assume infinite Q in the inductors, and  $C_{BIG}$  is a short.




$$Z_x = \left[ 1 + \left( 1 - \frac{v_x}{v_s} \right) \cdot g_m Z_s \right] r_{o1}$$

$$\text{where } Z_s = \left( 50 + sL_G + \frac{1}{sC_{GS1}} \right) \parallel sL_S$$


$$\frac{v_x}{v_s} = \frac{50 + sL_G}{50 + sL_G + \frac{1}{sC_{GS1}}}$$

$$\therefore Z_x = \left[ 1 + \frac{\frac{1}{sC_{GS1}}}{50 + sL_G + \frac{1}{sC_{GS1}}} \cdot g_m \cdot \left( 50 + sL_G + \frac{1}{sC_{GS1}} \right) \parallel sL_S \right] \cdot r_{o1}$$

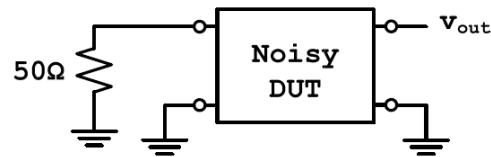**Problem 6.4:** This question concerns the measurement of noise figure of an arbitrary device under test (DUT).



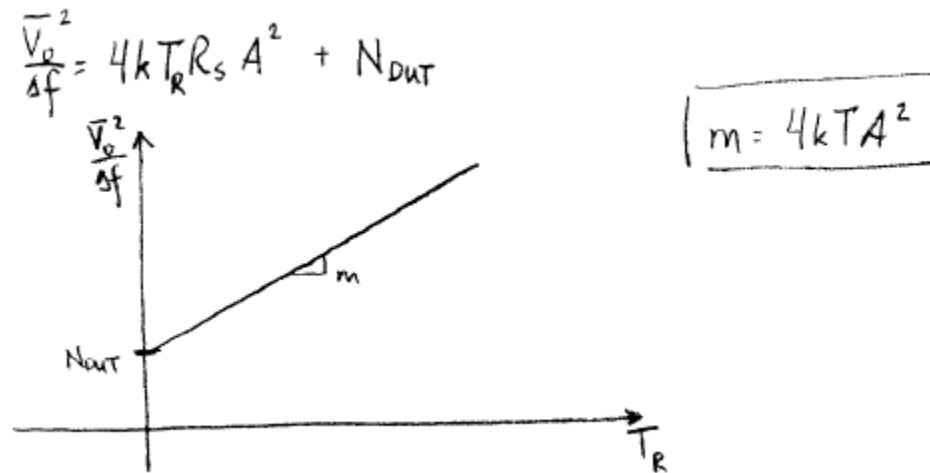- a) Assume that the temperature of the  $50\Omega$  source resistor can be precisely controlled. The noisy DUT has voltage gain  $A(s)$  and contributes a mean-square output referred noise voltage  $N_{DUT}$  in a given bandwidth  $\Delta f$ . Sketch a graph of the total mean square noise voltage measured at the output as a function of source resistor temperature. What is the slope of the line in  $V^2/T$ ?



- b) What is the significance of the intercept of this graph at  $T=0$  K?

At  $T=0$  K, the output mean square noise voltage is equal to  $N_{DUT}$ .

- c) Propose a technique to measure the noise figure (factor) of the DUT by only varying the temperature of the source. How many temperatures do you need? What if temperature control of  $R_s$  isn't available, but its temperature is known. How could you measure noise figure in this case?

① 2 measures:  $(T_{R1}, \overline{V_{o1}^2})$  and  $(T_{R2}, \overline{V_{o2}^2})$

$$m = \frac{\overline{V_{o2}^2} - \overline{V_{o1}^2}}{T_{R2} - T_{R1}}$$

$$\overline{V_{DUT}^2} = \overline{V_{o1}^2} - m T_{R1} = \overline{V_{o2}^2} - m T_{R2}$$

$$F = 1 + \frac{\overline{V_{DUT}^2}}{m R_s} = 1 + \frac{\overline{V_{o1}^2}}{m R_s} - \frac{T_{R1}}{R_s} = 1 + \frac{\overline{V_{o2}^2}}{m R_s} - \frac{T_{R2}}{R_s}$$

② 1 measure:  $(T_{R1}, \overline{V_{o1}^2})$

$$N_{OUT} = N_{R_s} G_p + N_{DUT} \Rightarrow N_{DUT} = N_{OUT} - N_{R_s} G_p$$

$$F = 1 + \frac{N_{DUT}}{N_{R_s} G_p} = \frac{N_{OUT}}{N_{R_s} G_p}$$

$N_{OUT}$  = output noise power  
 $N_{R_s}$  =  $R_s$  noise power  
 $G_p$  = power gain  
 measured (under  $N_{OUT}$ )  
 calculated (under  $N_{R_s} G_p$ )