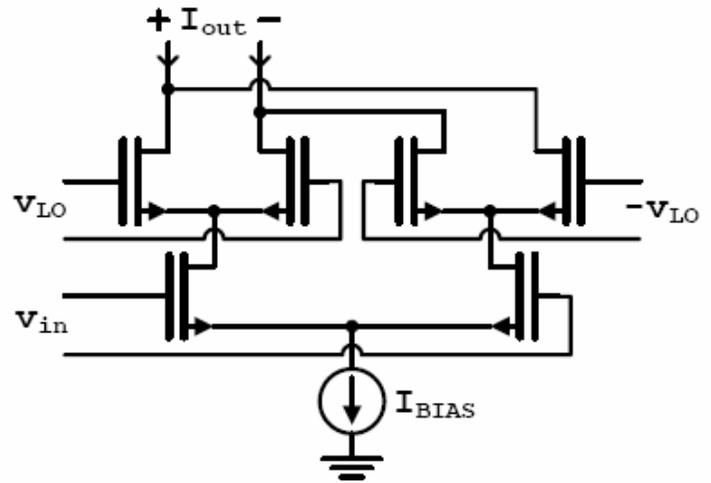


Problem 7.1: For this problem, assume the LO is a square wave at 900MHz, and the RF signal is a tone at 1GHz.

- a) Considering only the first harmonic component of the LO signal, what frequencies appear at the output of the mixer? Assume the mixer is perfectly balanced.

$$(900 + 1000) \text{ MHz} = 1900 \text{ MHz}$$

$$(1000 - 900) \text{ MHz} = 100 \text{ MHz}$$



- b) Derive an expression for the conversion gain of the mixer from the RF signal to the desired component at IF.

$$G_c = \frac{\text{IF amplitude}}{\text{RF amplitude}} = \left[\frac{2}{\pi} g_m \right]$$

- c) Now introduce a phase offset between the LO applied to the left and right mixers of $\Delta\theta$. Assume $\Delta\theta$ is small. Derive an expression for the output amplitude of the LO leakage at 900MHz as a result of the offset.

Hint: $\cos(A + \Delta) \approx \cos(A) - \Delta \sin(A)$ for small Δ .


Assume $v_{in} = \frac{i_{RF}}{g_m} = 0$ and consider only 1st harmonic

$$i_{IF}^+ = I_{BIAS} \left(\frac{4}{\pi} \cos(\omega_{LO} t) \right) \quad i_{IF}^- = I_{BIAS} \left(\frac{4}{\pi} \cos(\omega_{LO} t + \Delta) \right) \approx \frac{4 I_{BIAS}}{\pi} \left[\cos(\omega_{LO} t) - \Delta \sin(\omega_{LO} t) \right]$$

$$I_{out} = i_{IF}^+ - i_{IF}^- = \frac{4}{\pi} I_{BIAS} \Delta \sin(\omega_{LO} t)$$

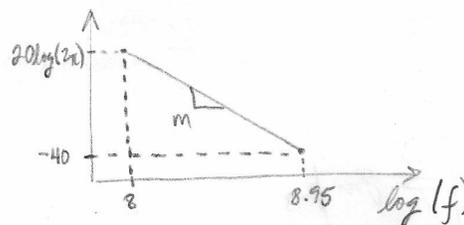- d) Using your expression for conversion gain from part b), find an expression for the ratio of LO leakage amplitude to IF signal amplitude in dBc. Assuming $G_m v_{in} = 1\%$ of I_{BIAS} for good linearity and $\Delta\theta = 2\pi/100$ (1%), what is the required slope of the IF filter in dB/decade to attenuate the LO signal to -40dBc below the IF signal level?

$$\frac{\frac{4}{\pi} I_{BIAS} \Delta}{\frac{4}{\pi} g_m v_{in}} = \frac{I_{BIAS} \frac{2\pi}{100}}{(0.01) I_{BIAS}} = 2\pi$$





$$m = \frac{20 \log(2\pi) - (-40)}{8 - 8.95}$$

$$m = -58.65 \text{ dB/dec}$$

Problem 7.2: You may neglect r_o and base current ($\beta = \infty$) for this problem.

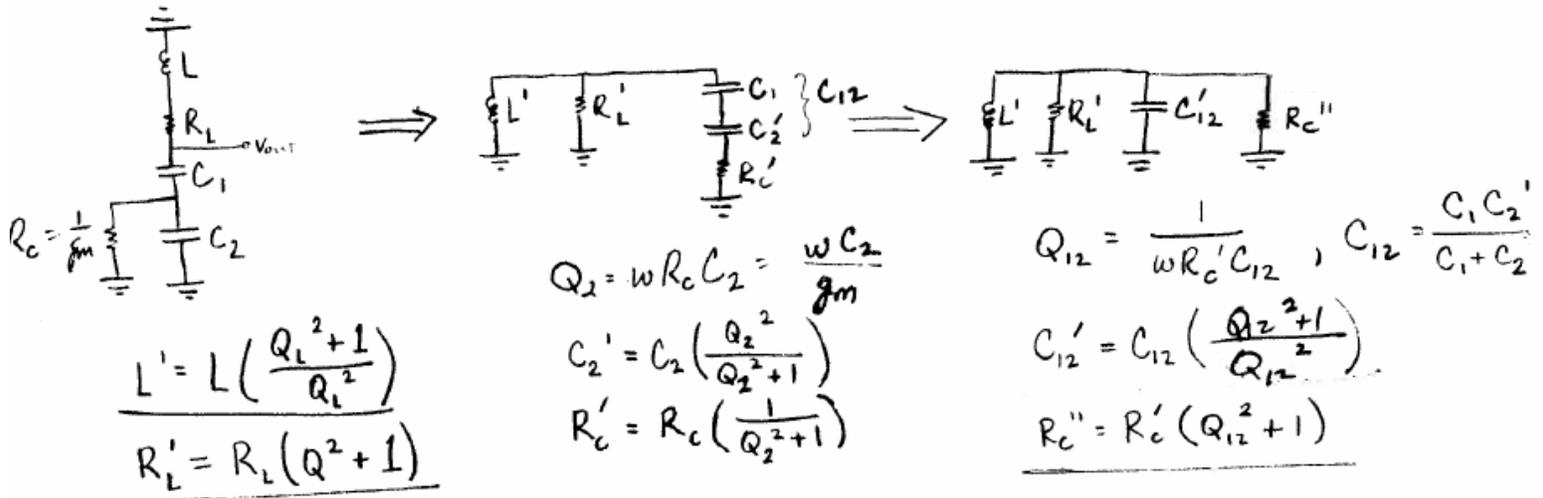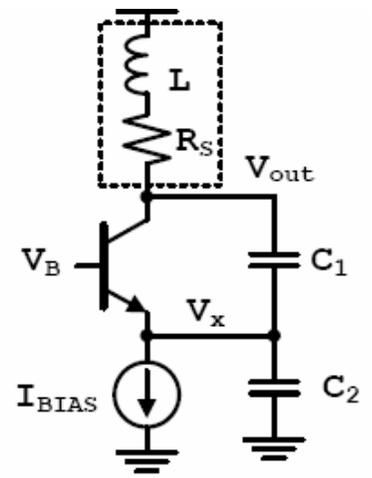- a) Simplify L , C_1 , and C_2 into an equivalent parallel RLC tank. Use the series-to-parallel resistance transformations discussed in lecture to find an expression for the equivalent loss R_{eq} of the parallel tank. Assume a series loss in the inductor R_S , and an inductor $Q_L = 10$. Do not neglect the impedance on node V_x in your expression for R_{eq} .



→ Assuming $Q_2^2 \gg 1$ we have

$$Q_{12} \approx \frac{\omega C_2}{g_m} \left(\frac{C_1 + C_2}{C_1} \right) \quad R_C' \approx \frac{g_m}{\omega^2 C_2^2}$$

therefore,

$$C_{12}' = \frac{C_1 C_2}{C_1 + C_2} \left(1 + \frac{g_m C_1}{\omega C_2 (C_1 + C_2)} \right)$$

and

$$R_C'' = \frac{1}{g_m} \left(\frac{C_1 + C_2}{C_1} \right)^2$$

$$Y_{eq} = \frac{j}{\omega L'} + \frac{1}{R_L'} + j\omega C_{12}' + \frac{1}{R_C''} = \left(\frac{1}{R_L'} + \frac{1}{R_C''} \right) + j \left(\omega C_{12}' - \frac{1}{\omega L'} \right)$$

$$R_{eq} = \text{Re}(Y_{eq}^{-1}) \approx \left(\frac{1}{R_L'} + \frac{1}{R_C''} \right)^{-1} \quad \text{for } \omega = \omega_{osc}$$


where $L' = \frac{101}{100} L \approx L$ $R_L' = 101 R_L$ $R_C'' = \frac{1}{g_m} \left(\frac{C_1 + C_2}{C_1} \right)^2$

b) Derive an expression for the oscillation frequency.

$$f_{osc} = \frac{1}{2\pi} \frac{1}{\sqrt{L' C_{12}'}} \approx \frac{1}{2\pi} \frac{1}{\sqrt{L C_{12}}} \quad \text{for } Q_{12}^2 \gg 1 \text{ and } Q_L^2 \gg 1$$

$$f_{osc} \approx \frac{1}{2\pi} \sqrt{\frac{C_1 + C_2}{L C_1 C_2}}$$

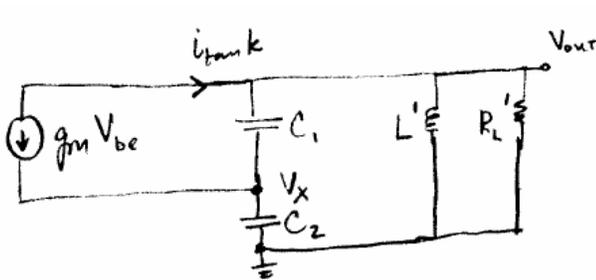c) Now incorporating the small-signal model of the BJT, derive an expression for I_{BIAS} that biases the oscillator just at the edge of oscillation. To simplify your expression, use the definition $n = C_1 / (C_1 + C_2)$.



$$V_{be} = -V_x = -V_{out} \left(\frac{C_1}{C_1 + C_2} \right)$$

$$i_{tank} = g_m V_x = g_m V_{out} \left(\frac{C_1}{C_1 + C_2} \right)$$

$$\frac{V_{out}}{i_{tank}} = \frac{(C_1 + C_2)}{g_m C_1} = \frac{1}{g_m n}$$

For oscillation

$$\frac{1}{n g_m} = Re Z = \frac{\left(\frac{1}{R_L} + n^2 g_m \right)}{\left(\frac{1}{R_L} + n^2 g_m \right)^2} \quad \text{for } \omega = \omega_{osc}$$

$$g_m = \frac{1}{(n - n^2) R_L} = \frac{1}{(n - n^2) (Q_L^2 + 1) R_L}$$

$$g_m = \frac{I_{Bias}}{V_T} = \frac{1}{n(1-n)(Q_L^2 + 1) R_L}$$

$$I_{Bias} = \frac{V_T}{n(1-n)(Q_L^2 + 1) R_L}$$

where

$$n = \frac{C_1}{C_1 + C_2}$$

$$Q_L = 10$$


$$V_T = \frac{kT}{q}$$

Problem 7.3: For this problem, assume L and C are lossless, and all losses are modeled by R_{eq} .


- a) Derive an expression for the differential amplitude of the fundamental oscillation across the tank. Assume all higher-order harmonics are perfectly filtered by the tank.

$$V_{osc} \approx I_{Bias} (R_{eq}) \left(\frac{4}{\pi}\right) \cos(\omega_0 t)$$


$$\boxed{|V_{osc}| \approx \left(\frac{4}{\pi}\right) (R_{eq} \cdot I_{Bias})}$$

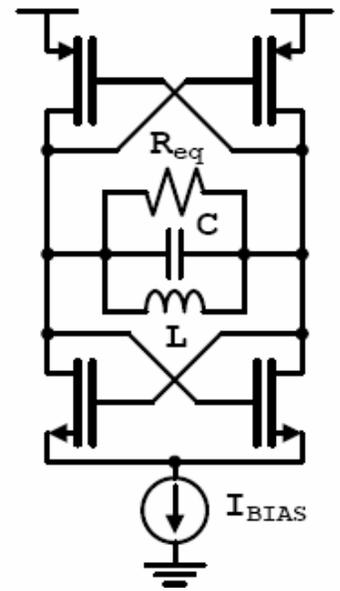

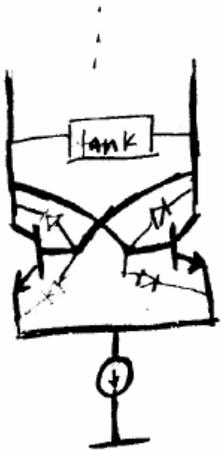- b) Replace the NMOS devices with NPNs. Explain how the amplitude is limited by the parasitic diodes in the BJT's. How would you modify the circuit to eliminate this limitation?



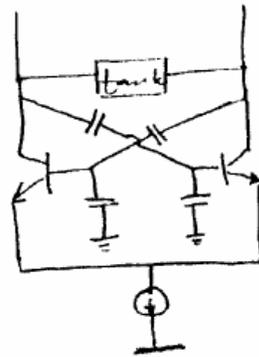- Amplitude is limited due to current path through parasitic diodes.
- To eliminate this effect you can add voltage dividers using capacitors




- The problem with this is that you will now need a biasing circuit for the BJTs

- You may also use buffers to reduce the limitation due to parasitic diodes.

Problem 7.4: This problem refers to the bandgap reference and corresponding expression for $\partial V_{BE}/\partial T$ shown in Lecture 22.

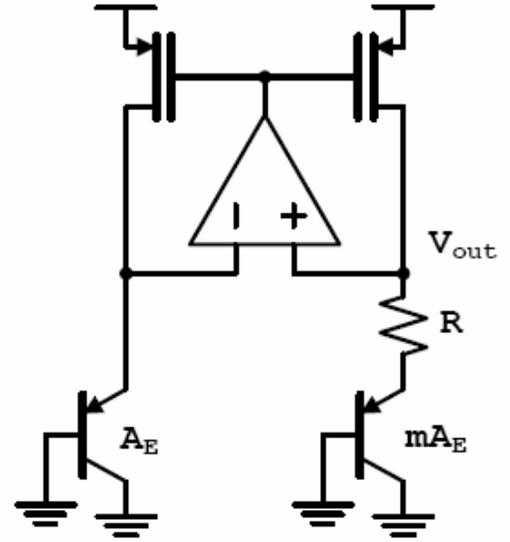- a) Assuming $V_{G0} = 1.2V$, $V_{BE} = 750mV$ at 300K, and from simulation, the exponent of I_S temperature dependency $r = 2$. What is the value of n , the exponent of I_C temperature dependency, determined by the circuit on the right?



$$V_{BE1} = V_{BE2} + I_C R$$

$$I_C R = \Delta V_{BE} = V_T \ln m = \frac{kT}{q} \ln m$$

$$I_C = \frac{kT}{qR} \ln m \Rightarrow I_C \propto T^1$$

Therefore, $n = 1$

- b) Using your answer from part, calculate $\partial V_{BE}/\partial T$ at 300K and determine the value of m (BJT area scaling ratio) to cancel this slope.

$$\frac{dV_{BE}}{dT} = -\frac{V_{G0} - V_{BE} + (r-n)V_T}{T} = -\frac{1.2 - 0.75 + (2-1)(0.026)}{300} = -1.587 \text{ mV/K}$$

$$\frac{d\Delta V_{BE}}{dT} = \frac{k}{q} \ln m = 1.587 \text{ mV/K} \Rightarrow \ln m = 18.4$$

$$m \approx 9.76 \times 10^7$$

- c) Now assume the resistor has a temperature dependency, typically proportional to \sqrt{T} . What is the new value of n , the exponent of I_C temperature dependency, and new value of $\partial V_{BE}/\partial T$?

$$\text{From part a) } I_C = \frac{kT}{qR} \ln m \Rightarrow I_C \propto \frac{T^1}{T^{1/2}}$$

$$I_C \propto T^{1/2} \Rightarrow n = 1/2$$

$$\frac{dV_{BE}}{dT} = -\frac{V_{G0} - V_{BE} + (r-n)V_T}{T} = -1.63 \text{ mV/K}$$

- d) Using your value of m from part b), and the value of $\partial V_{BE}/\partial T$ from part c) calculated at 300K, what is the error voltage at V_{out} at 0°C and 85°C , the extremes of the commercial temperature range?

$$\begin{aligned}V_{out_error} &= V_{be} + \Delta V_{be} + (\ln)m)V_T \\&= V_{be} + (-1.63\text{mV})(\Delta T) + 18.4 \frac{\text{mV}}{^\circ\text{C}} \\&= V_{be} + (-1.63\text{m})(T-300) + 18.4 \frac{\text{mV}}{^\circ\text{C}}\end{aligned}$$

$$V_{out_error} (T=273) \approx 1.2\text{mV}$$

$$V_{out_error} (T=358) \approx 2.54\text{mV}$$

Problem. 7.5


b)

Bias: 25 uA/um => Vbias = 512mV,

Bias: 75 uA/um => Vbias = 628mV

Bias: 200 uA/um => Vbias = 839mV

DC Response

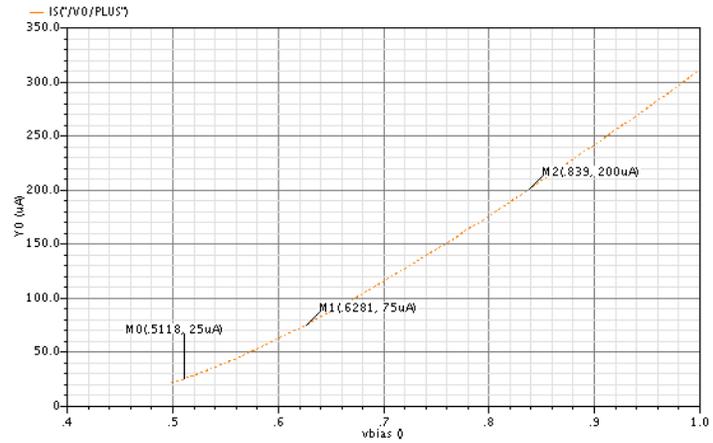



P1dB

Bias: 25 uA/um

Bias: 75 uA/um


Periodic Steady State Response

Periodic Steady State Response

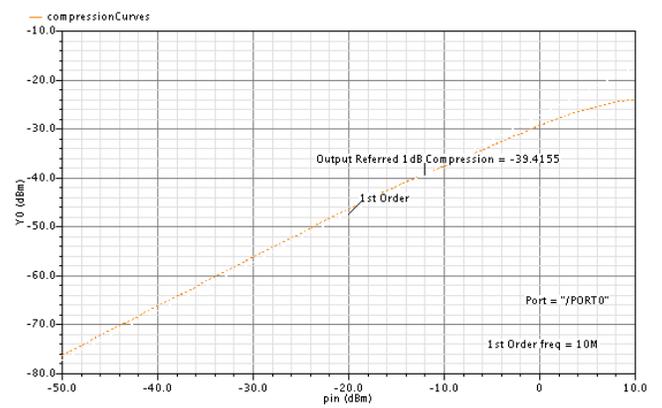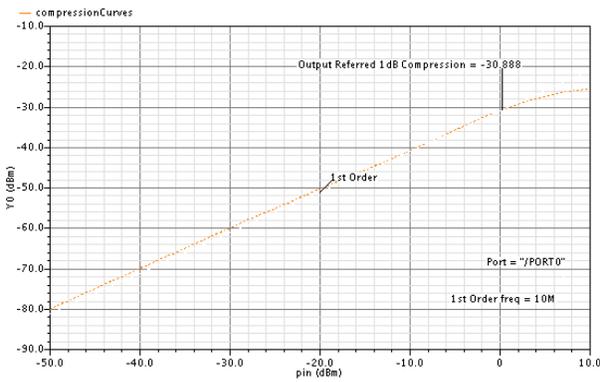


Bias: 200 uA/um

Periodic Steady State Response

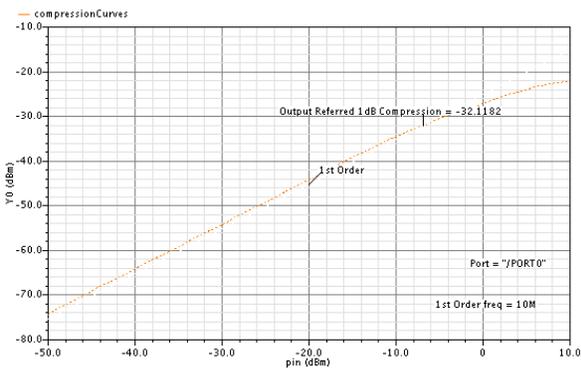


OIP3

Bias: 25 uA/um

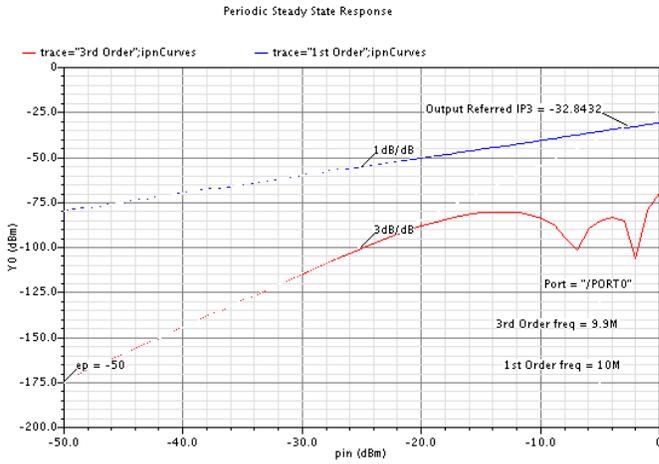

Bias: 75 uA/um

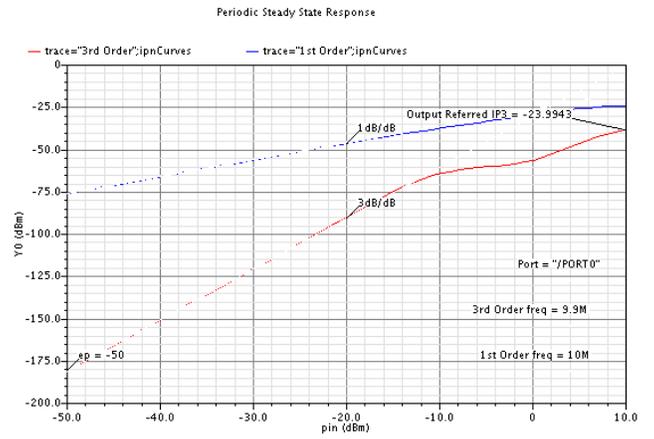

Bias: 200 uA/um

