


A Current Re-use Quadrature Front-End Receiver for ISM Band

Karan J, Abishek M, Aswin S


Introduction

- ▶ **Stacked current reuse architecture for front-end**
 - ▶ Low power, bias current re-use
 - ▶ No coupling required from stage to stage
- ▶ **I and Q demodulation**
 - ▶ Image rejection
- ▶ **ISM Band 915 MHz**
 - ▶ Intermediate frequency is 10 MHz
 - ▶ IF amplifier with LO leakage reduction
 - ▶ BPSK coding
- ▶ **Applications:**
 - ▶ Cordless phone
 - ▶ WSN nodes
 - ▶ ZigBee devices

Conventional Receiver Architecture

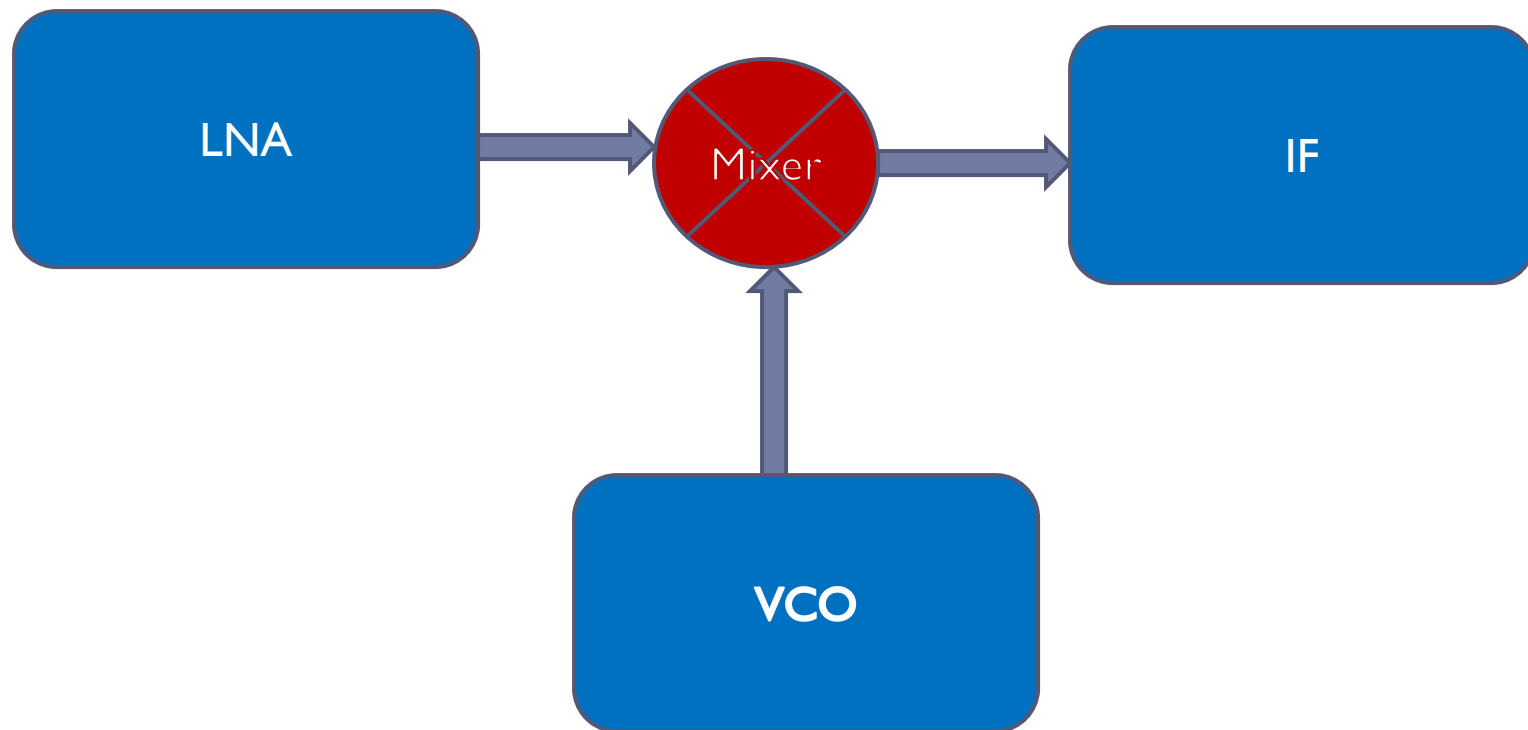


QLMV – Block level

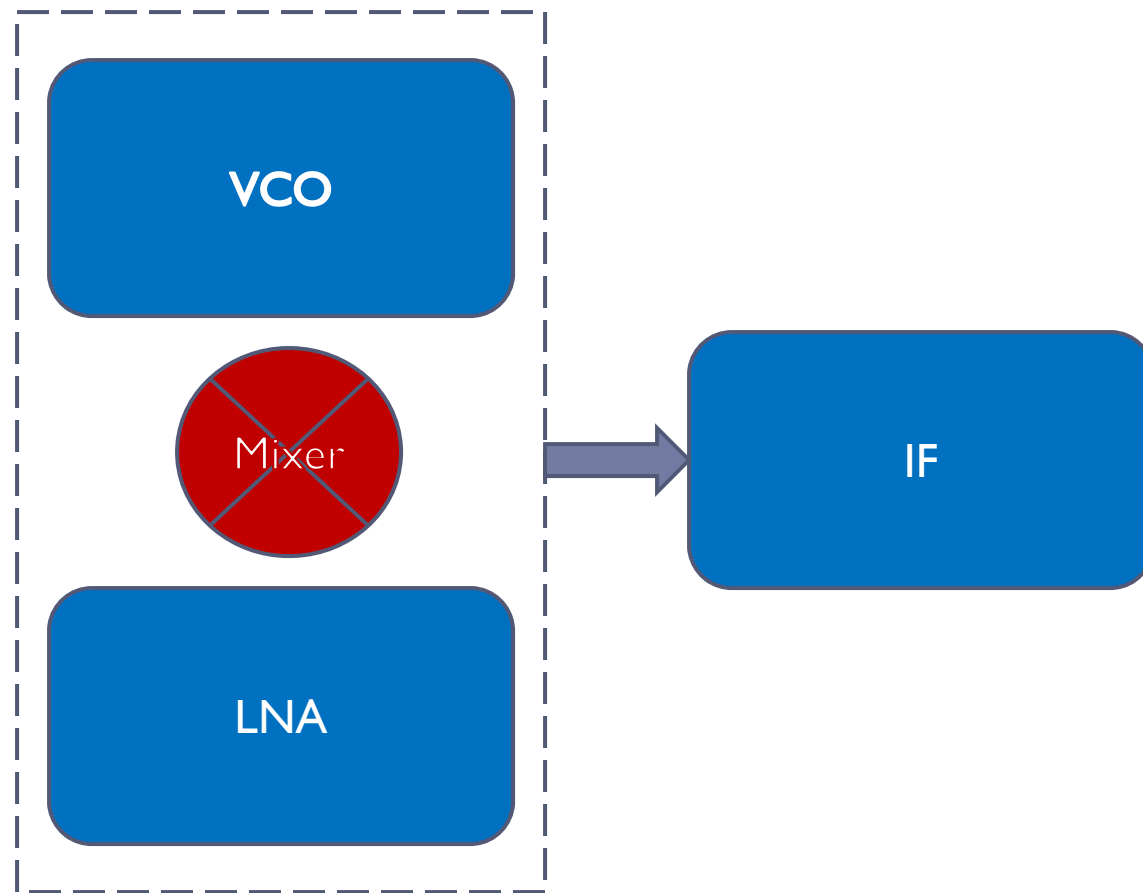

QLMV Cell Stack


QLMV Cell (Top-Level)

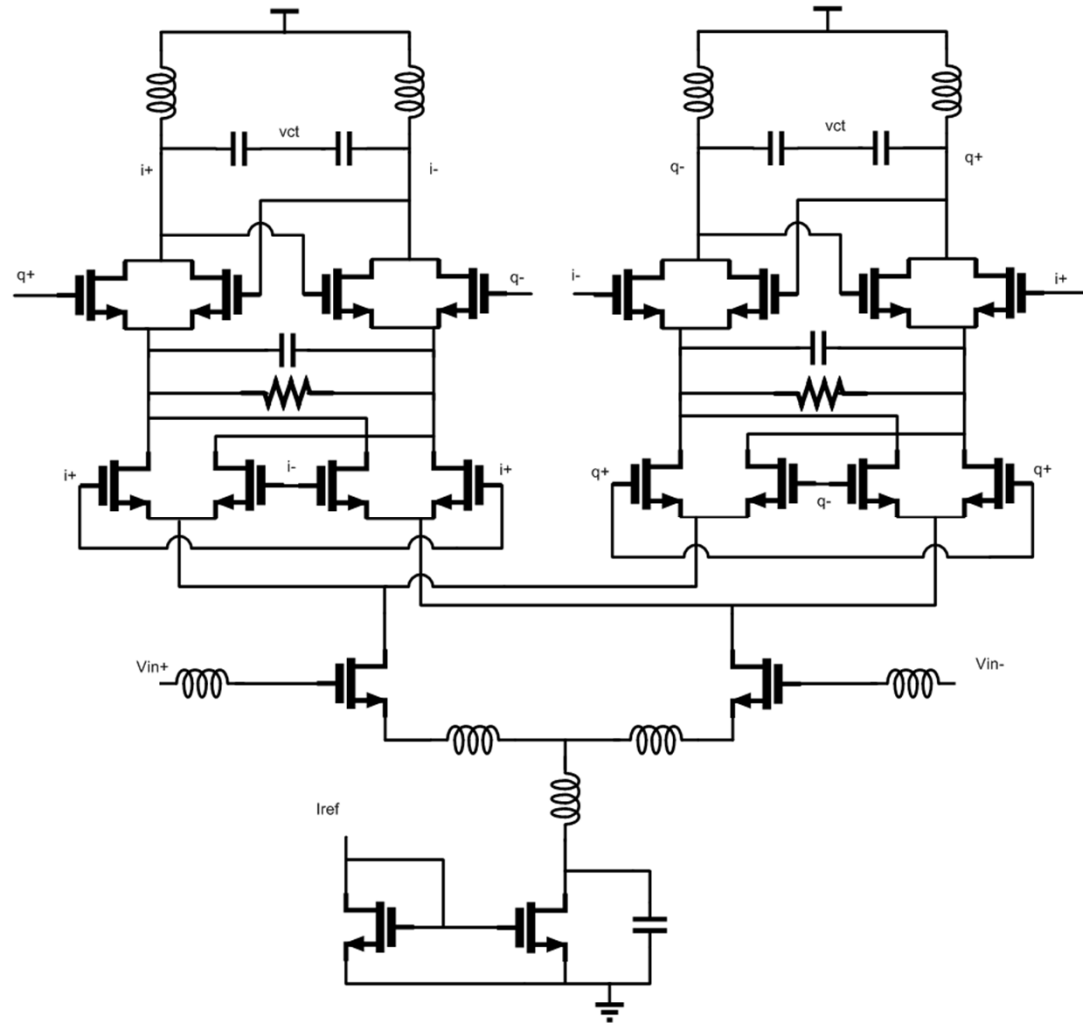


[1], [3]

LNA:

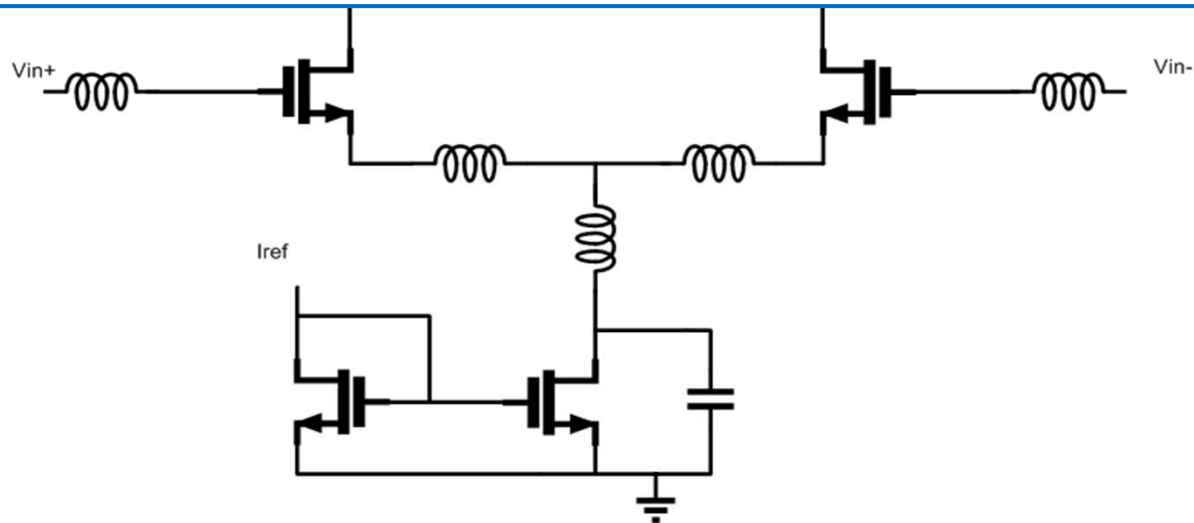
- Degenerated Common Source Amplifier
- Tested with balun as well as a direct input port
- S_{11} : -18dB @ 900MHz
- Inductor to decouple
 - Open circuit at high frequencies
- Tail current of 1.8mA.
- LNA NF (individual characterization) : 2.1 dB



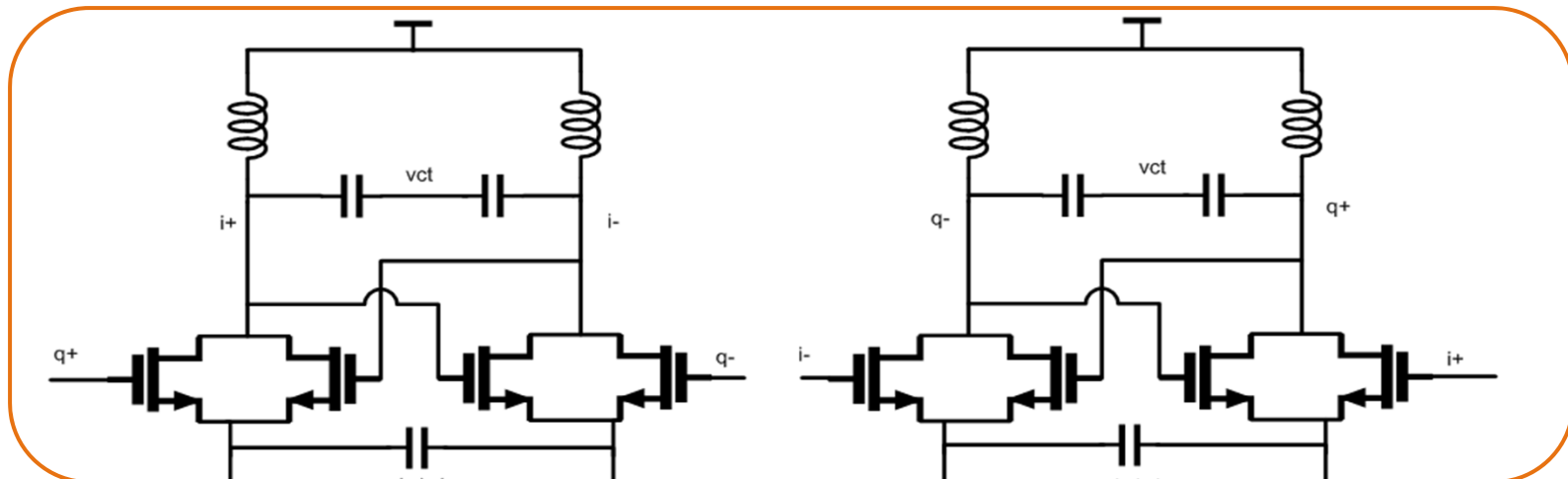


QVCO:

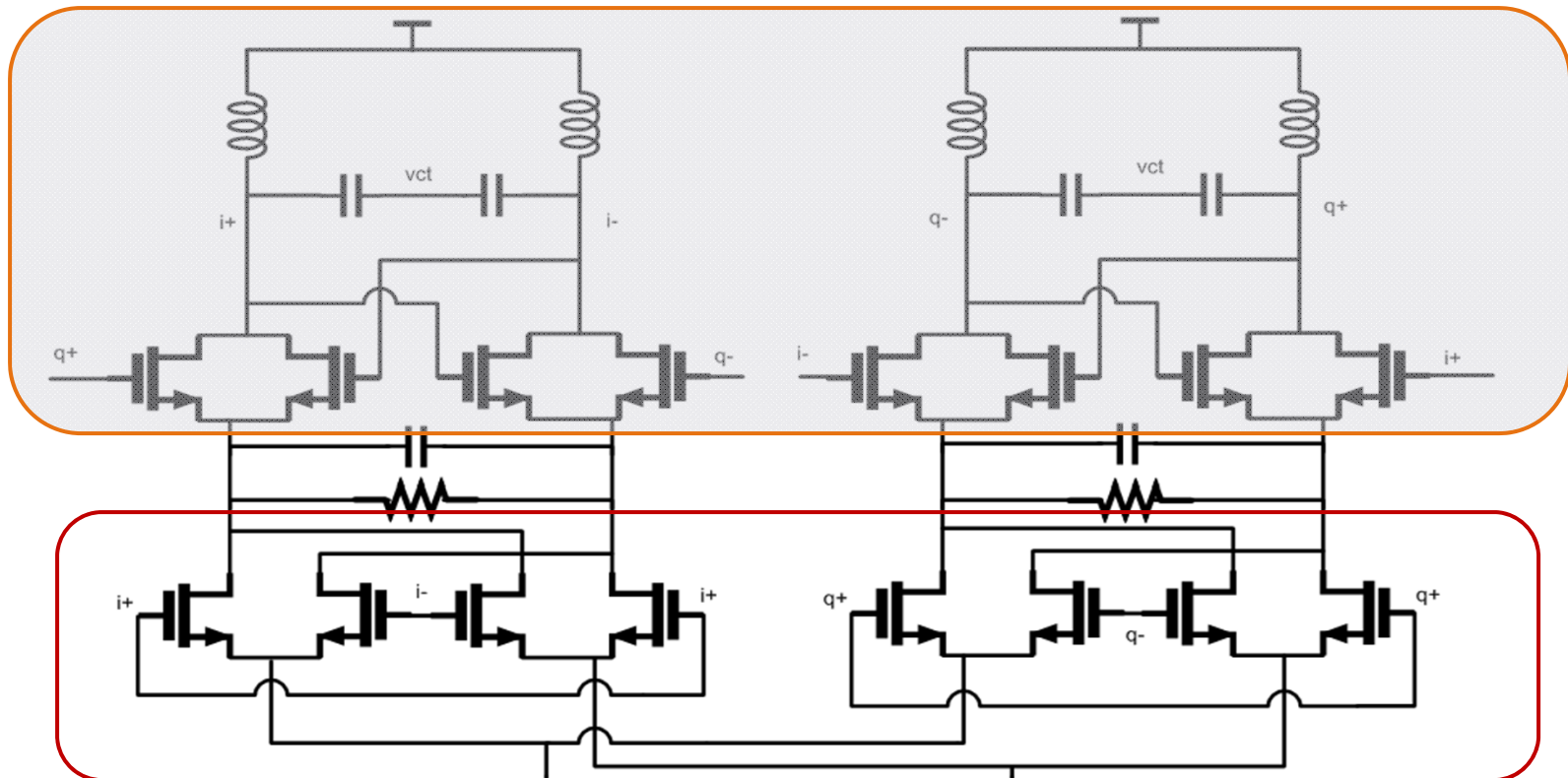- Gate-modulated architecture proposed by the paper
 - Less frequency pulling and increased phase noise
- Chose to implement a PVCO
- Phase Noise. - 115dBc (900Mhz – 940Mhz)
- Tunability: V_{ct} - 500mV – 700mV. (for PLL or outside tuning)
- Bottom cap for increasing Q-factor and reducing feedthrough of LO
- Transistors sized up to reduce flicker noise




Mixer:

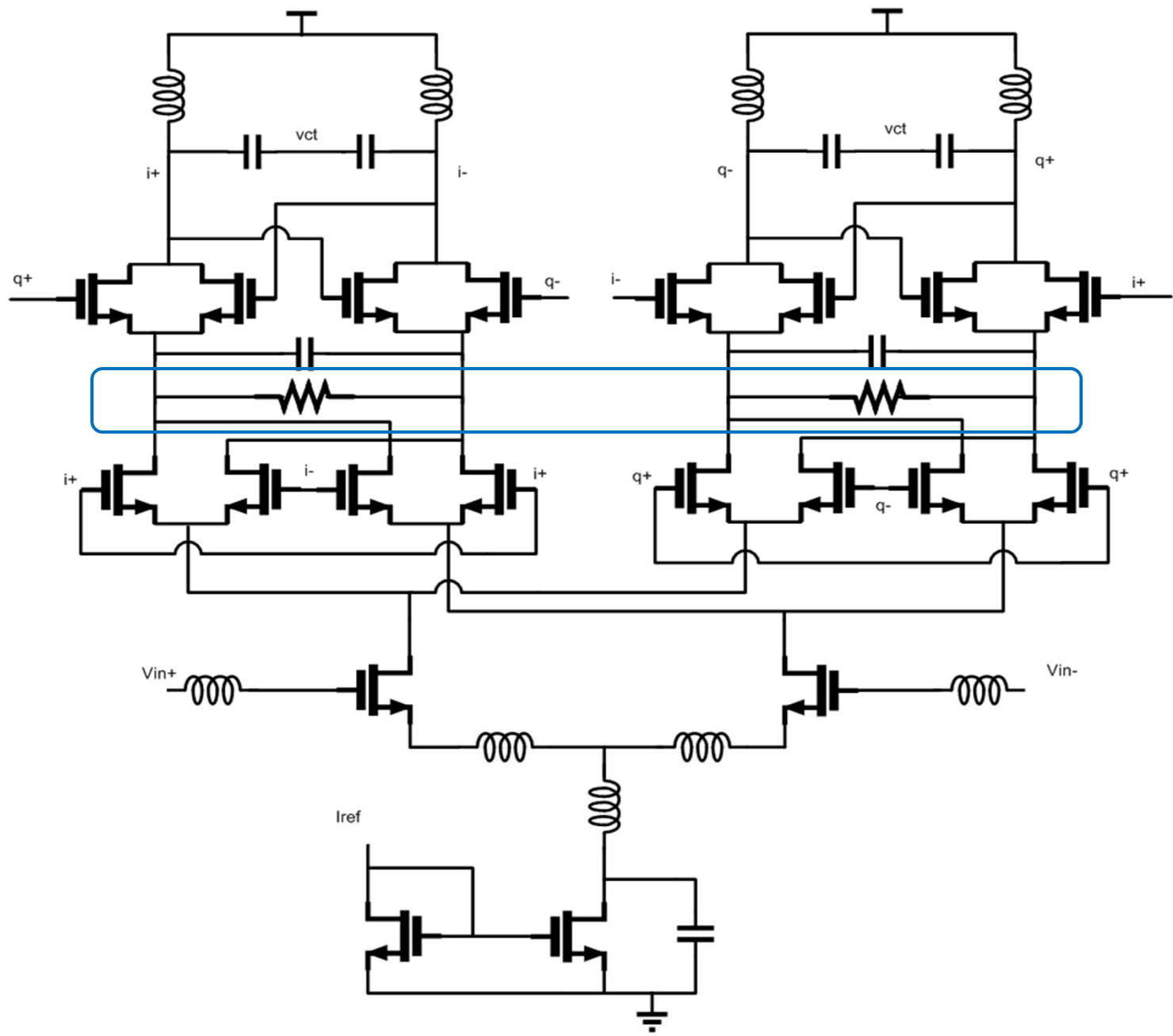- Doubly balanced Gilbert mixer
- Mixer works in triode
 - Running in saturation needs external circuitry (adds noise)




IF Amplifier 2 (IF_2)

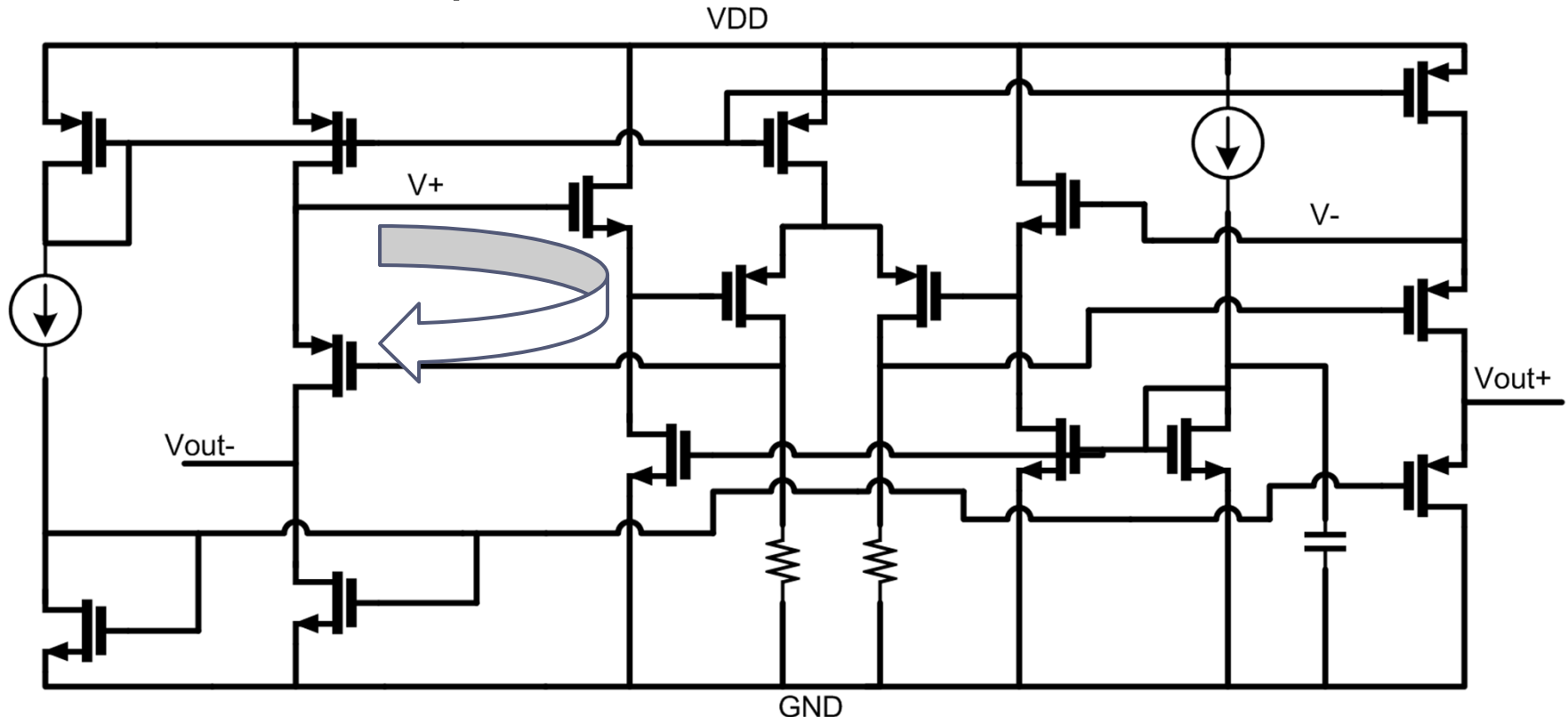- ▶ New architecture – trans-impedance amplifier
- ▶ 40dB/dec roll off
- ▶ Power consumption: 1mW



IF Amplifier 1 (IF_1)

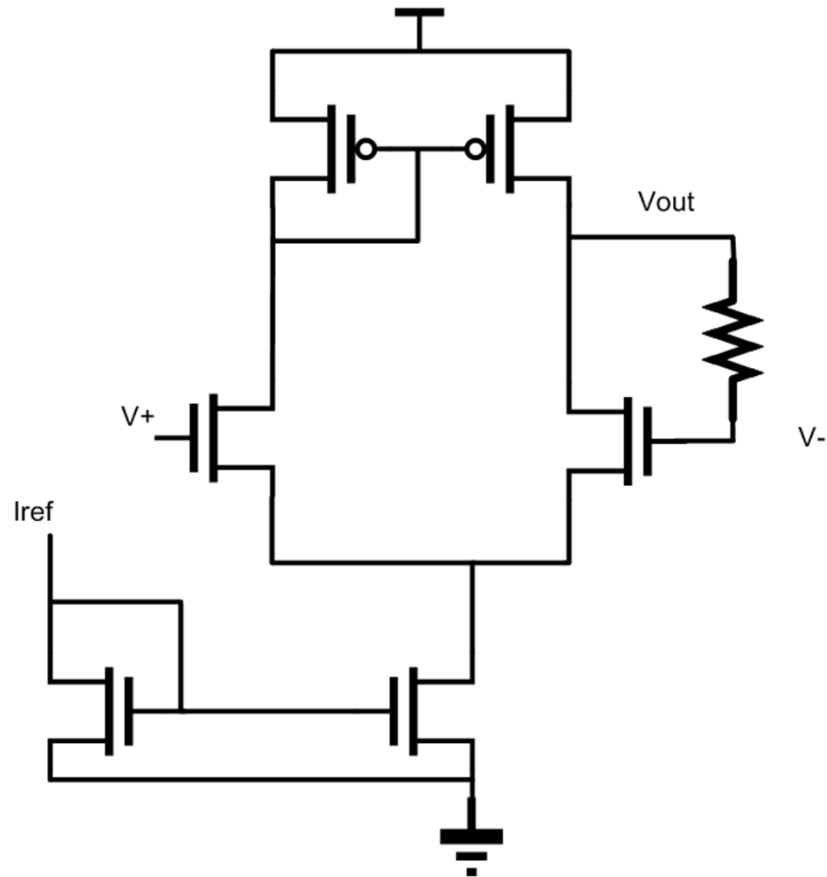
- ▶ Single pole trans-impedance amplifier
- ▶ Bandwidth – 15 MHz
- ▶ 20dB/dec roll-off
- ▶ Power: 300 μW



System Integration and Comparison

- ▶ RC polyphase filters for image rejection
 - ▶ Generates bandpass filter
- ▶ PLL for frequency control
- ▶ Baseband DSP processing

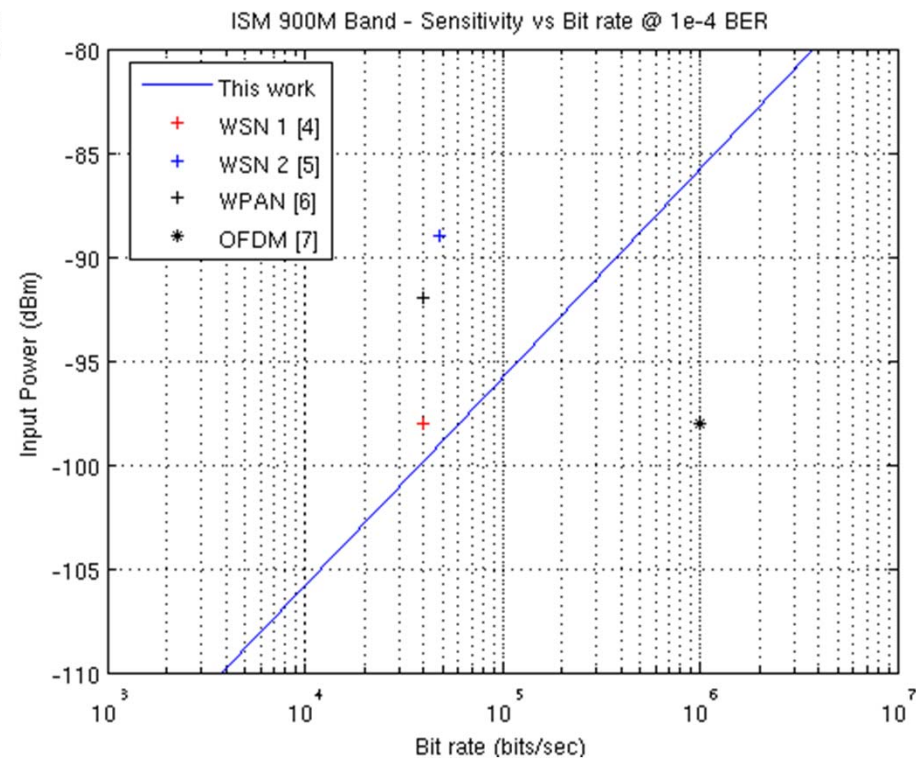
- ▶ Typical BER - 10^{-4}
- ▶ Link Budget Analysis
 - ▶ 900MHz Protocols



Layout

- ▶ DRC and LVS clean
- ▶ Die area – 2.5mm²

LNA
VCO + mixer
IF Amplifier

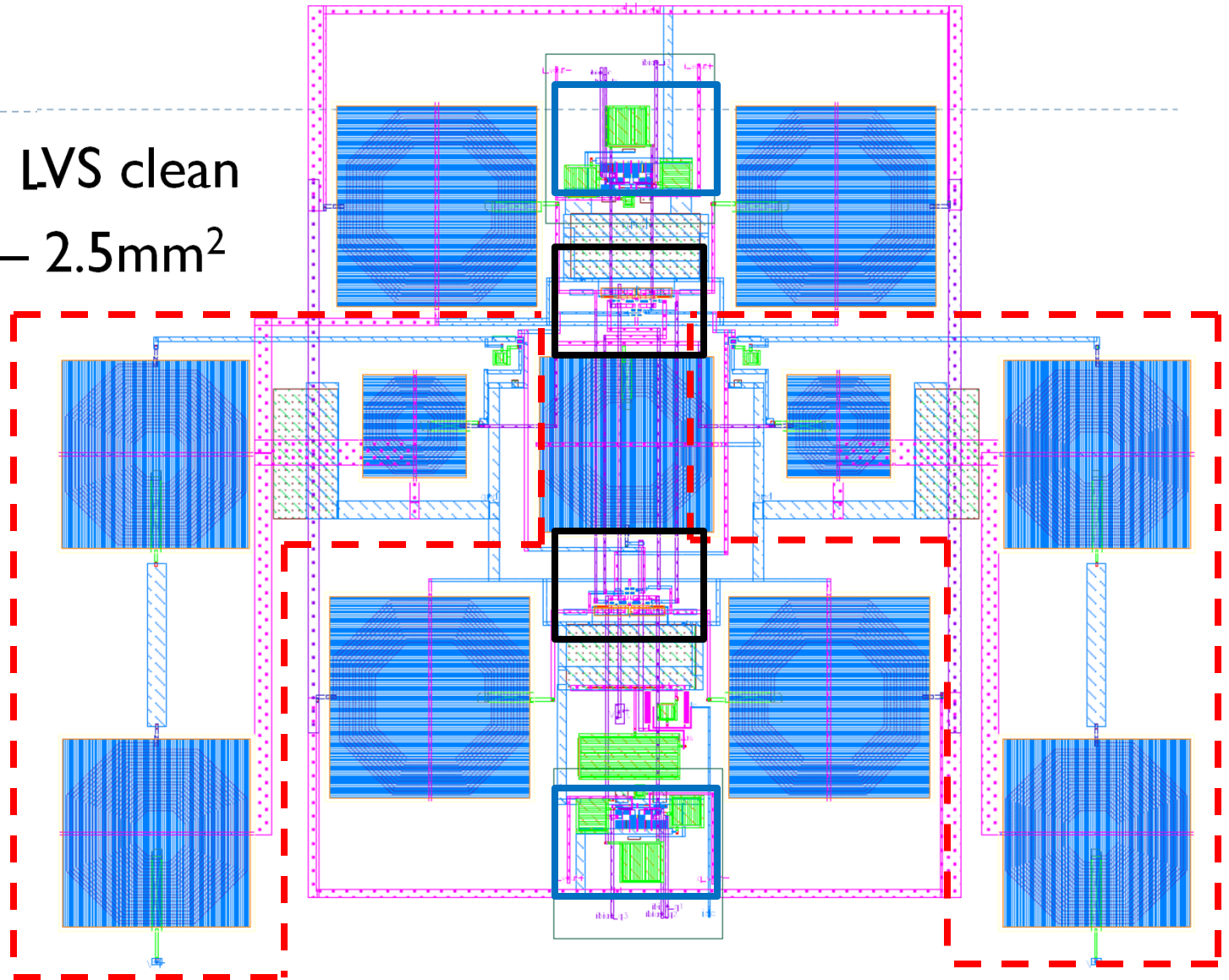


Summary Chart

	QLMV (IF_1)	QLMV (IF_2)	[1] GPS Rx
S_{11} (dB)	< -10	< -10	< -10
IIP3 (dBm)	21.5	- 55	- 30
P_{-1dB} (dBm)	- 41.5	- 65	- 40
Conversion gain (dB)	46	42	42.5
Noise Figure (dB)	9.8	12	6.5
VCO Phase Noise (dBc/Hz) @1 Mhz	-116	-116	-110
VDD (V)	1.2	1.2	1
Current QLMV (mA)	1.8	1.8	1
Current IF Amp (mA)	1	1.8	1


References

- ▶ [1] Kuang-Wei Cheng; Natarajan, K.; Allstot, D.J.; , "A Current Reuse Quadrature GPS Receiver in 0.13 m CMOS," *Solid-State Circuits, IEEE Journal of* , vol.45, no.3, pp.510-523, March 2010
- ▶ [2] A. Liscidini, A. Mazzanti, R. Tonietto, L. Vandi, P. Andreani, and R. Castello, "Single-stage low-power quadrature RF receiver front-end: The LMV cell," *IEEE J. Solid-State Circuits*, vol. 41, pp. 2832–2841, Dec. 2006.
- ▶ [3] K.-W. Cheng and D. J. Allstot, "A gate-modulated CMOS LC quadrature VCO," in *IEEE Radio Freq. Integrated Circuits Symp. Dig.*, 2009, pp. 267–270.
- ▶ [4] RF Link Budget Analysis at 915 MHz band for Wireless Sensor Networks
Abdellah Chehri, Member, IEEE, Hussein Mouftah, Fellow, IEEE, Paul Fortier, Senior, IEEE, and Hasnaa, Aniss, Member, IEEE
- ▶ [5] An Ultra-Low-Power 868/915 MHz RF Transceiver for Wireless Sensor Network Applications
R. van Langevelde I, M. van Elzakker I, D. van Goor, H. Termeer, J. Moss and A.J. Davie
- ▶ [6] IEEE 802.15.4-2006 is a standard which specifies the [physical layer](#) and [media access control](#) for low-rate wireless [personal area networks](#) (LR-WPANs). It is maintained by the [IEEE 802.15](#) working group.
- ▶ [7] <http://doodlelabs.com/products-and-services/ofdm-radio-modules/900-mhz-ism-band-dlm108.html>

Thank You !!!

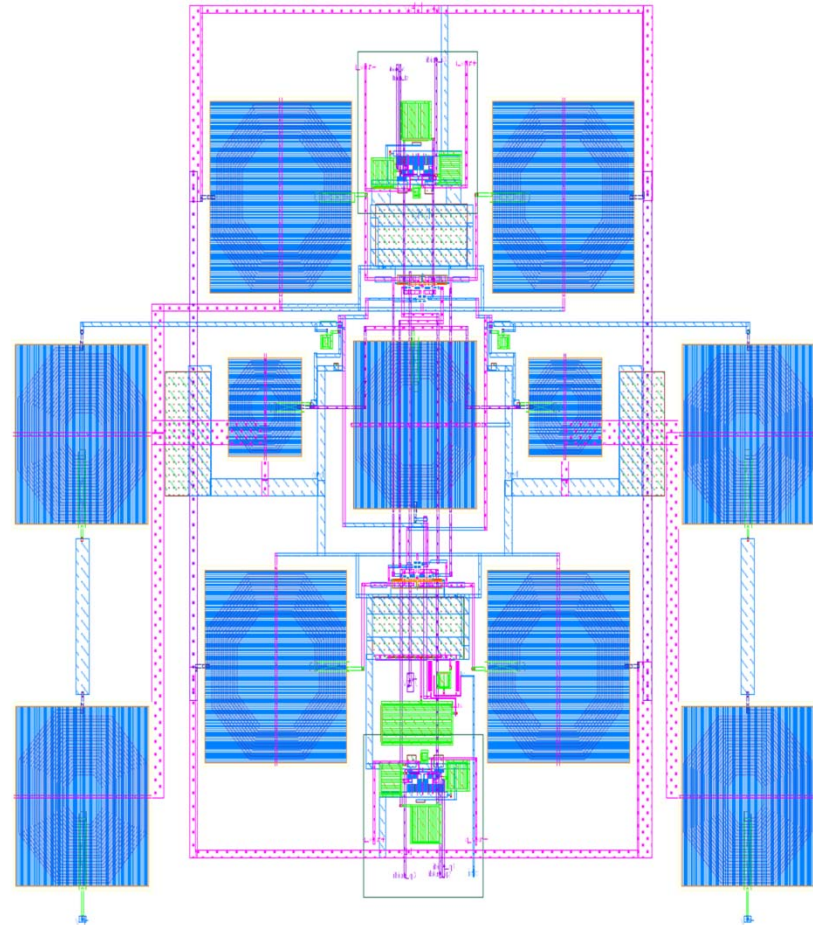


S11

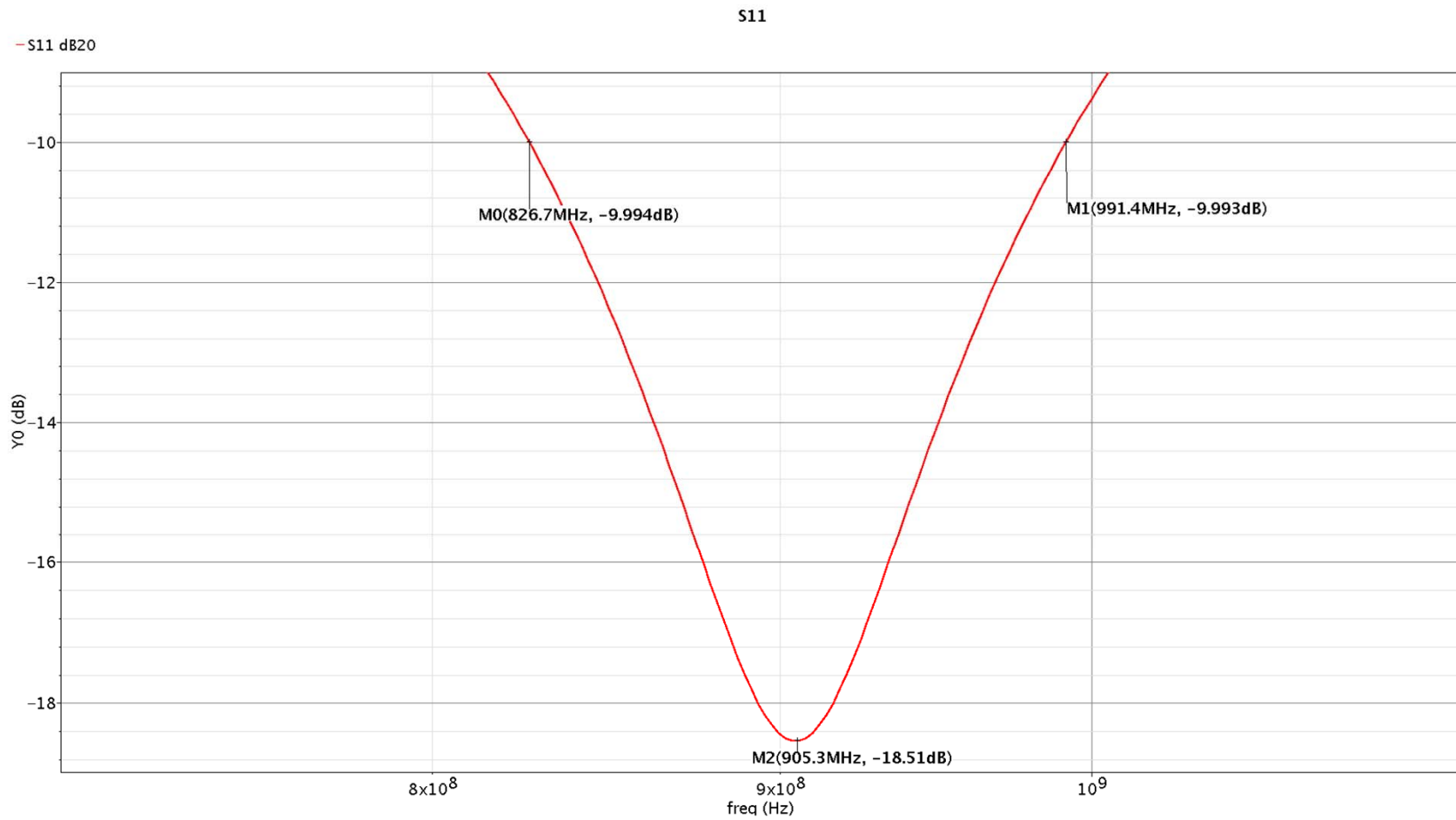

Phase Noise


Phase Noise

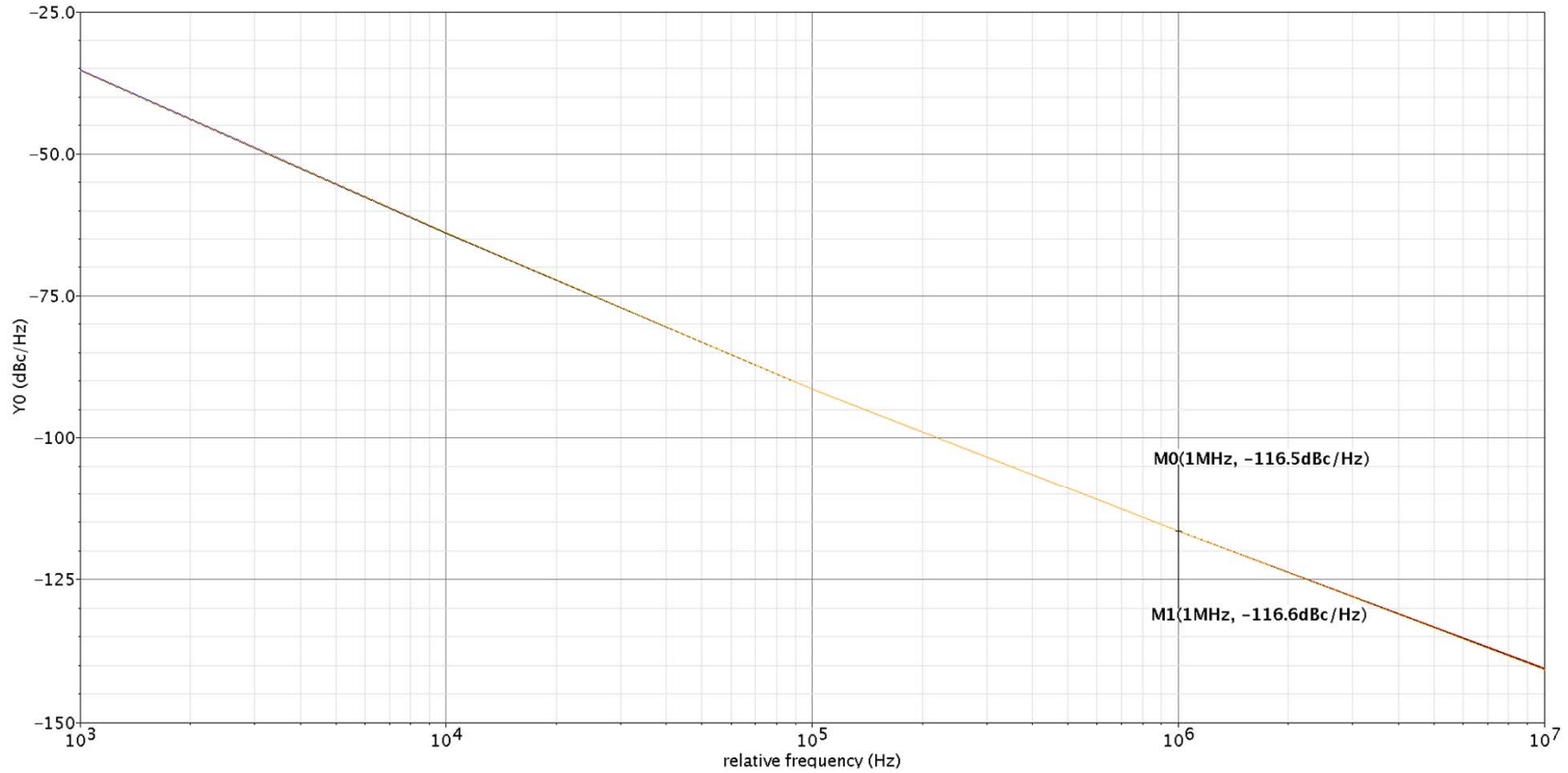- vct="500m";Phase Noise; dBc/Hz, Relative Harmonic = 1 - vct="550m";Phase Noise; dBc/Hz, Relative Harmonic = 1 - vct="600m";Phase Noise; dBc/Hz, Relative Harmonic = 1
- vct="650m";Phase Noise; dBc/Hz, Relative Harmonic = 1 - vct="700m";Phase Noise; dBc/Hz, Relative Harmonic = 1




VCO frequency control


- ▶ V_{control} vs VCO frequency plot:

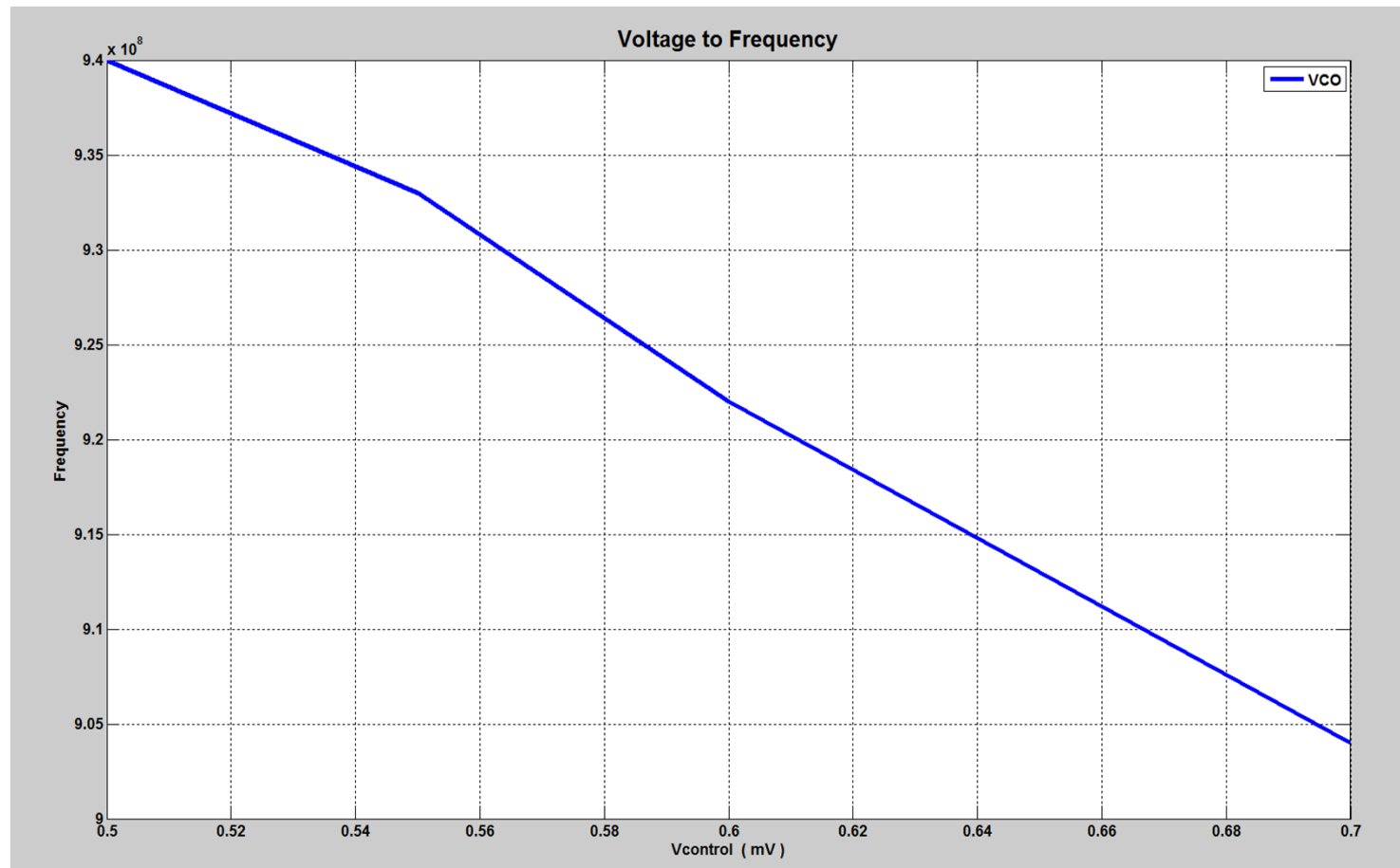


Noise figure for LMV cell

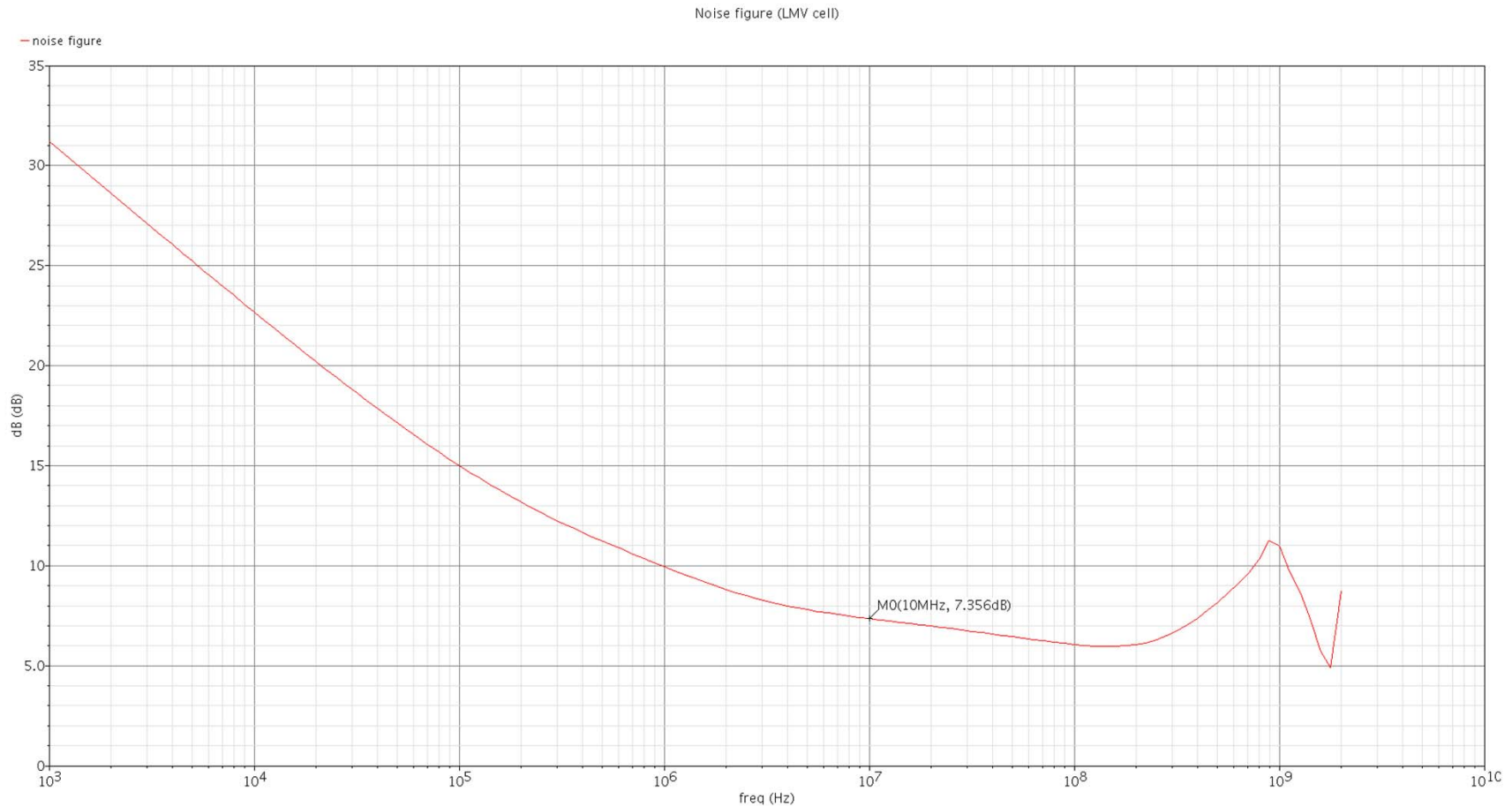

Noise figure

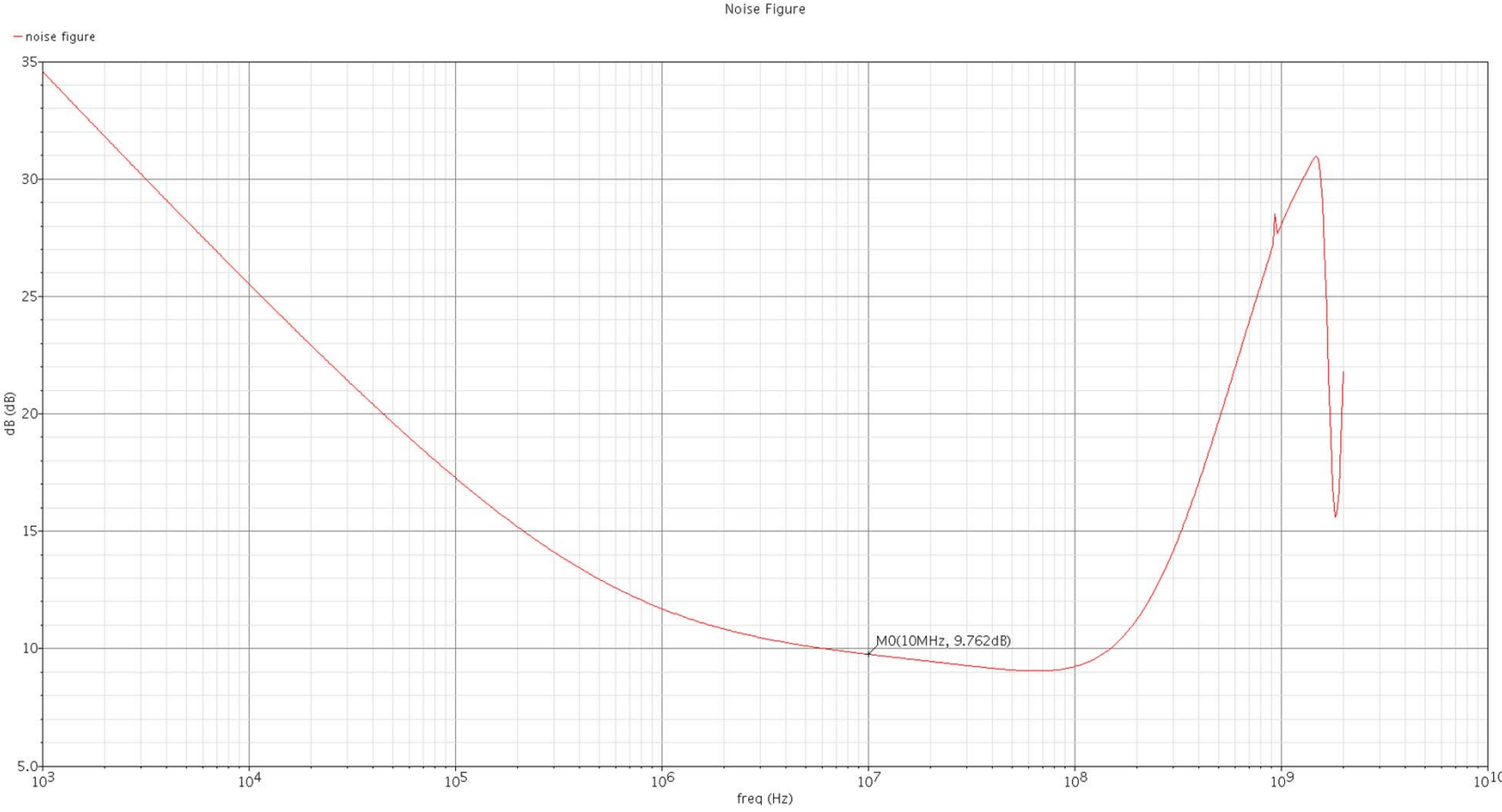

P1dB (-41 dB)

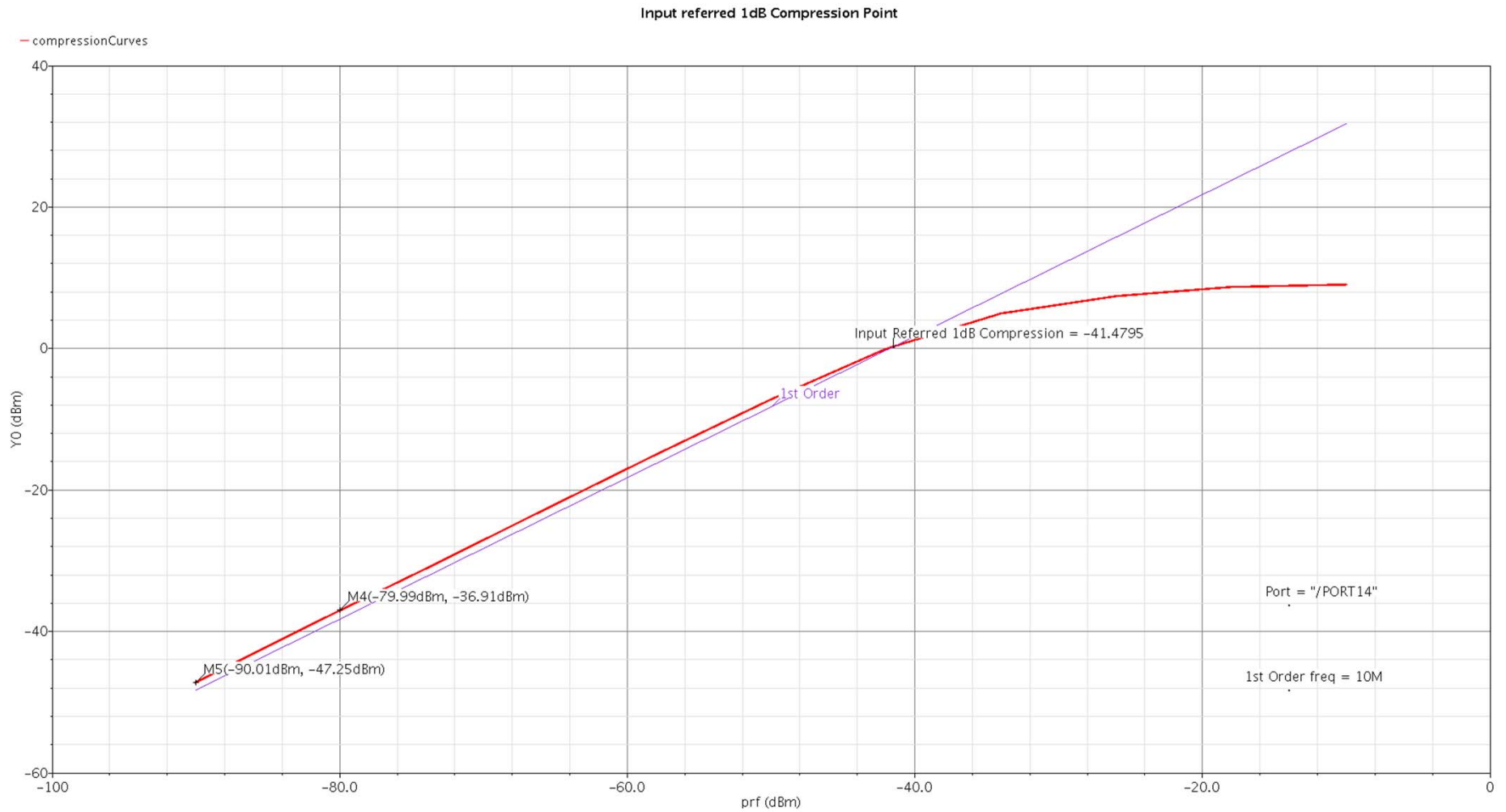

IIP3 = -21.493dB

