

Practice homework, computer engineering part, Engineering 100, section 250

Questions with a "\$" after them are intended to be challenging. Those questions with "\$\$" after them are probably unreasonable. Later I will post answers to *selected* questions.

(updated 11/29@9:20am)

Number representation

- Provide the 8-bit two-complement representation for the following values. If the value can't be represented write "no such representation" instead.
 - 1
 - 0
 - 1
 - 14
 - 14
 - 70
 - 70
 - 99
 - 127
 - 127
 - 128
 - 128
 - 255
- What is the range of representation of the following representation schemes? All answers should be in decimal (e.g. "4 to -4")
 - 12-bit two's complement number
 - 8-bit unsigned number
 - 3-bit two's complement number
 - 32-bit two's complement number
- Shifting
 - If the unsigned number 12 is shifted to the left by 3, what is the value of the number after the shift?
 - In general shifting a number to the left by X is the same as multiplying a number by what?
 - In general shifting a number to the right by X is the same as _____ a number by _____?
- If you had the value 2 in a memory location in the e100 and then you drove it out to HEX3-HEX0, what would be displayed on the HEX displays?
 - What if the value were 17?
 - 2?
 - 15?
 - 1024?

Digital Logic

In this section "+" means OR, "*" means AND, "!" means "NOT", and " \oplus " is XOR

- Write the truth table for
 - $(A+B)*C$
 - $(!A*C)+!B$
 - $A\oplus B$

2. Write the logical statement which corresponds to each of the following truth tables (a-g)

X	Y	Z	a	b	c	d	e	f	g
0	0	0	0	0	0	1	1	0	1
0	0	1	0	1	0	1	0	1	1
0	1	0	0	1	1	1	0	1	1
0	1	1	0	1	0	1	0	1	0
1	0	0	0	1	0	0	0	1	0
1	0	1	0	1	0	1	0	1	0
1	1	0	0	1	0	1	1	0	1
1	1	1	1	1	0	1	0	1	0

(For example, the answer to “a” is $X*Y*Z$)
e, f and g are all pretty tricky (\$))


3. Draw logic gates which correspond to the following logic expressions

a. $(A+B)*C$

b. $(!A*C)+!B$

c. $A\oplus B$

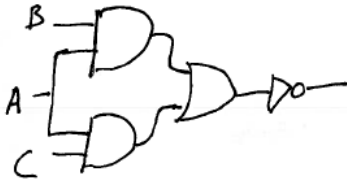4. Write a truth table that corresponds to the following circuit.



E100 programming

- Write an e100 assembly function named SI which takes two arguments, SI_a and SI_b and returns a single value SI_rv. The function is to compute SI_a times SI_b **by using repeated additions** rather than using the multiply instruction. The caller uses SI_ra to store the return address. Your function should include the declaration of all memory locations used (including those mentioned above).
- Write an e100 assembly program which **continuously** reads a 16-bit number from the dip switches, multiplies the value by 4 and then displays the results on the red LEDs.
 - Of LED_RED[15:0], what LED(s) is/are never lit? Why? (HINT: This is more of a number representation problem.)
- Write an e100 assembly program which initially displays “0000” on the HEX digits HEX3-HEX0 and then increments that value once per second.


4. Say we have a new device added to the e100. It uses our standard protocol and has the following ports:

Port number	Port type	Definition	Use
150	in	bit 0: Bob_valid	Bobbity Bob Bob
151	out	bit 0: Bob_ack	
152	out	bits 15-0: Bob_data	


- Is this an input or output device? How can you tell?
- Write an e100 assembly *function* called BobD which takes a single input, BobD_value, and properly passes that data off to the Bob device.

Transistors

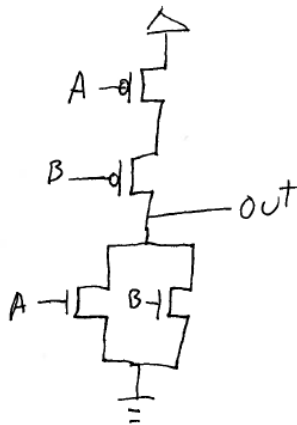- Write the truth table for the following devices. Each entry of the truth table should be either "0", "1", "HiZ" or "Smoke".



a.

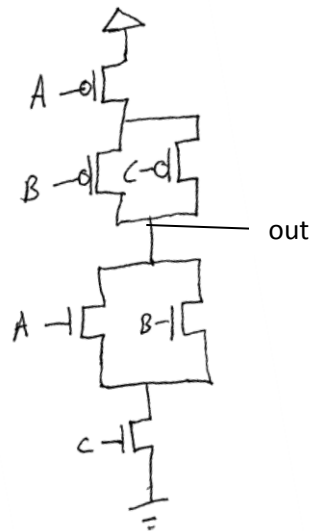


b.


- Draw a "NAND" gate using transistors.
- Draw an "AND" gate using transistors.
- Draw a 3-input "OR" gate using transistors.
 - Do it again and use 8 or fewer transistors if you didn't the first time.
- Draw an XOR gate using transistors. (\$)
- Draw a tri-state device using transistors. (\$, we did this in class but try to figure it out without looking).

Latches and Flip-flops

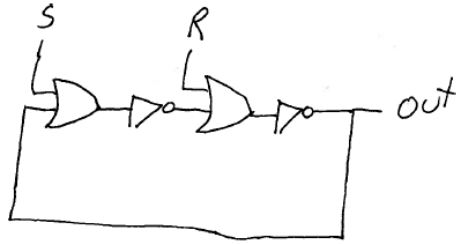1. Write a truth table for the following circuit. Each entry should be either "0", "1", "holds value".




a.

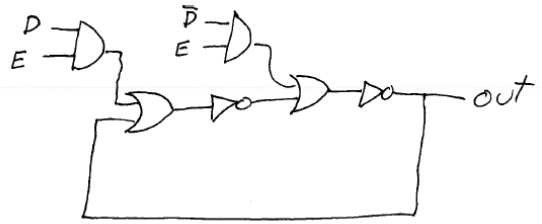


b.

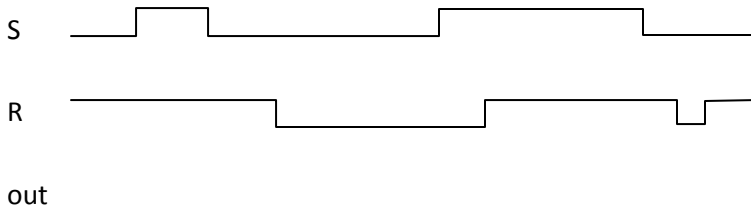
2. Consider a SR-latch (the thing in problem 1a). Finish the following timing diagram.



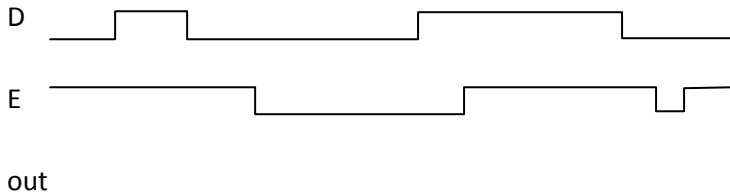3. Now do the same for the D-latch (the thing in problem 1b).



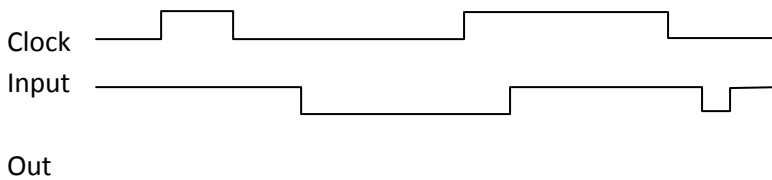4. Now do the same thing for a 1-bit register with no write enable.



5. Design a one-bit register with a write enable using standard gates (AND, OR, NOT). \$\$