

2.8 In the circuit shown in Fig. P2.8, determine  $v_x$ ,  $v_y$ ,  $i_a$ , and  $i_b$ .

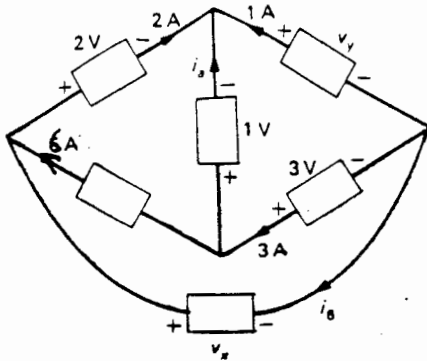


FIGURE P2.8

2.10 In the circuit shown in Fig. P2.10, determine  $v_x$ ,  $v_y$ , and  $i_z$ .

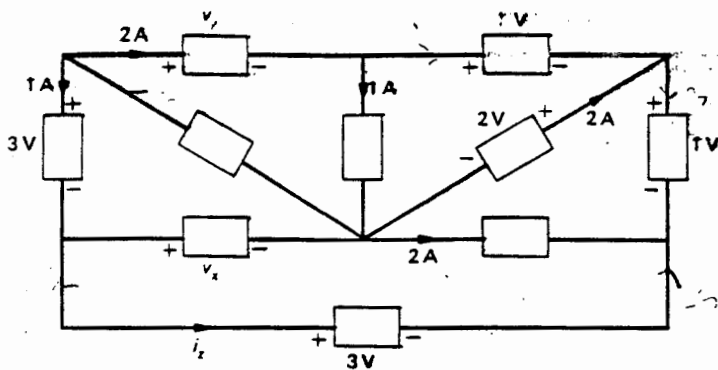


FIGURE P2.10

2.11 Automobile storage batteries are rated in terms of their terminal voltage (12-V) and their ampere-hour (Ah) capacities. For a typical 12-V battery having a 115-Ah capacity, determine the length of time this battery will light a 6-W bulb. (Assume that the battery voltage is constant at 12 V, even though this is not true for real batteries.) Determine the total energy stored in the battery before it is connected to the bulb.

2.12 In the circuit shown in Fig. P2.12, apply KVL, KCL, and Ohm's law to determine the currents and voltages associated with all the elements. Compute the power absorbed by the resistors and the power delivered by the ideal sources. Does conservation of energy result?


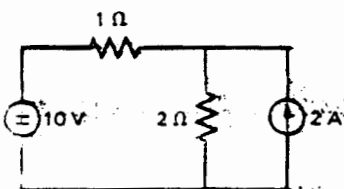


FIGURE P2.12

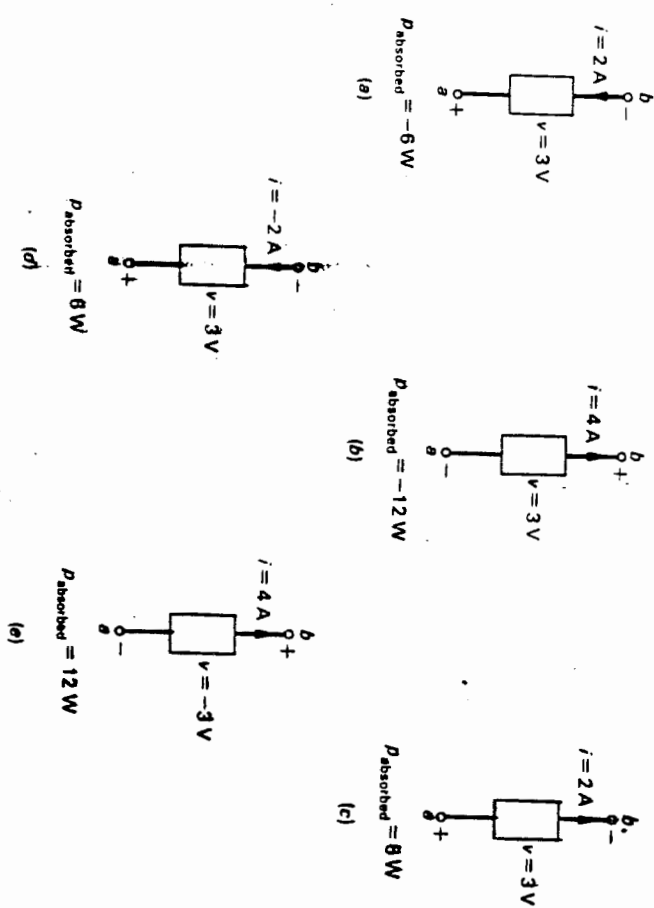

① TEXT #2.8

USING KVL AROUND LOOP SHOWN GIVES


$$V_x - 2 + 1 - 3 = 0 \rightarrow \boxed{V_x = 4V}$$

KVL AROUND RIGHT HALF GIVES

$$3 - 1 - V_y = 0 \rightarrow \boxed{V_y = 2V}$$

KCL AT TOP NODE GIVES  $2 + 1 + i_a = 0 \rightarrow \boxed{i_a = -3A}$

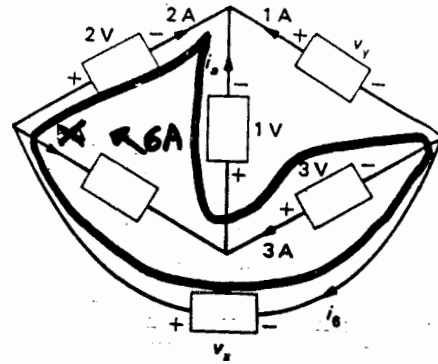KCL AT RIGHT NODE GIVES  $3 + 1 + i_b = 0 \rightarrow \boxed{i_b = -4A}$



② TEXT #2.10

KVL AROUND LOOP SHOWN GIVES


$$V_x + 3 - V_y - 1 - 2 = 0 \rightarrow \boxed{V_x = V_y}$$

KVL AROUND BORDER GIVES

$$3 + 3 - V_y - 1 - 1 = 0 \rightarrow \boxed{V_y = 4V}$$

KCL AT UPPER LEFT  $\rightarrow i_w = 3A$

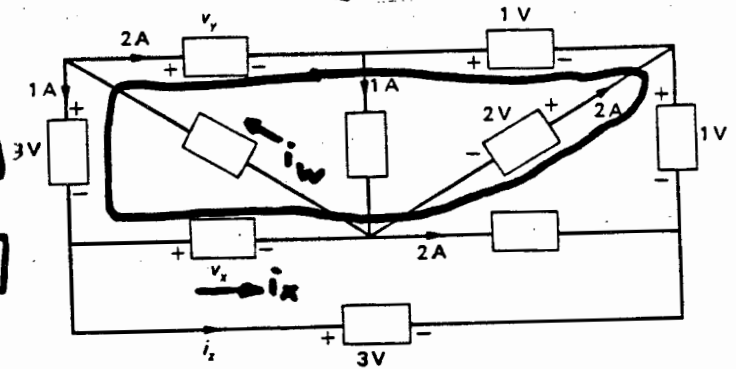KCL AT CENTER  $\rightarrow i_x + 1 = 2 + 2 + i_w \rightarrow i_x = 6A$ .  $1 = i_x + i_z \rightarrow \boxed{i_z = -5A}$



③ TEXT #2.11

$$P = iV. \quad 6W = i(12V) \rightarrow i = 1/2 \text{ AMP.} \quad 115 \text{ A-HR} / (1/2 \text{ AMP}) = \boxed{230 \text{ HOURS}}$$

$$\text{ENERGY} = Pt = iVt = (i t)V = (115 \text{ A-HR})(3600 \text{ SEC/HR})(12V) = \boxed{4.968 \times 10^6 \text{ J}}$$

~ 9 1/2 DAYS

④ TEXT #2.12

LET  $i_1$  = CURRENT LEFT-TO-RIGHT THROUGH  $1\Omega$ .


$$\text{KVL: } 10 - i_1(1\Omega) - (i_1 + 2)(2\Omega) = 0 \rightarrow \boxed{i_1 = 2A}$$

$$V_2 = \text{VOLTAGE ACROSS CURRENT SOURCE} = (i_1 + 2)(2\Omega) = \boxed{8V}$$

CONSERV. OF ENERGY:

$10V$	$: (10V)(-2A) = -20 \text{ W}$	$1\Omega$	$: (2A)^2(1\Omega) = 4 \text{ W}$
$2A$	$: (-2A)(8V) = -16 \text{ W}$	$2\Omega$	$: (8V)^2/2\Omega = 32 \text{ W}$

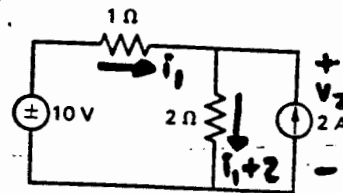$-36 \text{ W DISSIPATED} \rightarrow 36 \text{ W DISSIPATED}$



REF: D. E. JOHNSON  
J. R. JOHNSON  
J. L. HILBURN  
P. D. SCOTT

ELECTRIC CIRCUIT ANALYSIS  
3RD ED.

PRENTICE HALL  
1997