
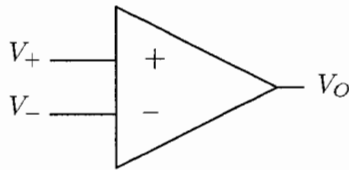


**Circuit Figure:**

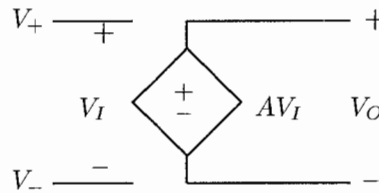

**Circuit Model:**



- : **Inverting** input. **Point** (of triangle): **Output** of op-amp.
- +: **Non-Inverting** input. **Not shown:** Power supply connections.

$$V_O = \begin{cases} A(V_+ - V_-) & \text{if } |A(V_+ - V_-)| < 12V \\ 12V & \text{if } A(V_+ - V_-) > 12V \\ -12V & \text{if } A(V_+ - V_-) < -12V \end{cases} \quad \begin{array}{l} \text{Dependent source} \\ \text{is linear only over a} \\ \text{limited input range} \end{array}$$

**A:** *Open-loop gain*  $A \approx 200,000!$  But output actually *clips* at  $\pm 12V$ .

$R_{IN}$  : Assume  $R_{IN} \rightarrow \infty$  (actually  $\approx 2M\Omega$ );  $R_{OUT} = 0$  (actually  $\approx 70\Omega$ )

**210:** We assume **negative feedback**:  $\exists$  connection between output and  $V_-$

**EX: Inverting amplifier:**

**Node:**  $\frac{V_- - V_I}{R_I} + \frac{V_- - V_O}{R_F} = 0$  at  $V_-$

**Device:**  $V_O = A(V_+ - V_-) = -AV_-$

**Combine:**  $\frac{V_O}{V_I} = -\frac{R_F}{R_I} \frac{1}{1 + \frac{1}{A}(1 + \frac{R_F}{R_I})} \approx -\frac{R_F}{R_I} v_i$

**Also:**  $V_- = -\frac{V_O}{A} \approx 0 = V_+ : V_- \approx V_+$

**“Golden Rules” for Ideal Op-Amp Circuits with Negative Feedback:**

- $I_+ = I_- = 0$  (input currents=0). Note *output* current  $\neq 0!$   
KCL does *not* apply to ideal op-amp: no power supply connections!
- $V_+ = V_-$  (virtual short at input). Actually differ by few *mV*.

**Note:** Input looks like both open and short circuit simultaneously!

**EX:** Redo inverting amplifier circuit above using golden rules:


**Node:**  $V_- = V_+ = 0$ .  $I_- = 0 \rightarrow I = \frac{V_I}{R_I} = -\frac{V_O}{R_F} \rightarrow \frac{V_O}{V_I} = -\frac{R_F}{R_I}$ . Easier!

**See:** Overleaf for: Non-inverting amp; follower; summer; differential amp.

**Note:** All of these assume op-amp  $|V_O| < 12V$ ; if not,  $V_O$  clips at  $\pm 12V$ .


**Note:** For analysis with finite  $R_{IN}$  and nonzero  $R_{OUT}$ , see pp. 206-208.

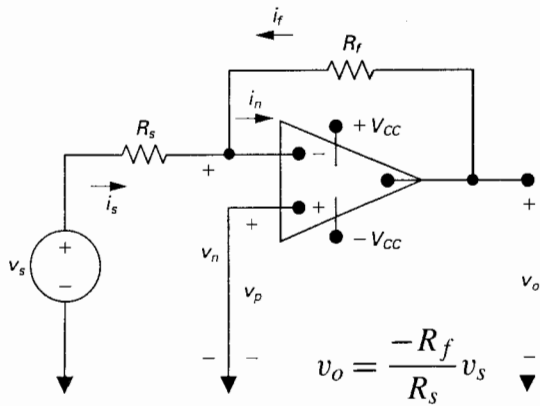**CMRR:** Differential amp Common-Mode Rejection Ratio =  $\frac{\text{differential mode gain}}{\text{commonmode gain}}$ .




An inverting-amplifier circuit.

$$v_o = -\frac{R_f}{R_s} v_s$$

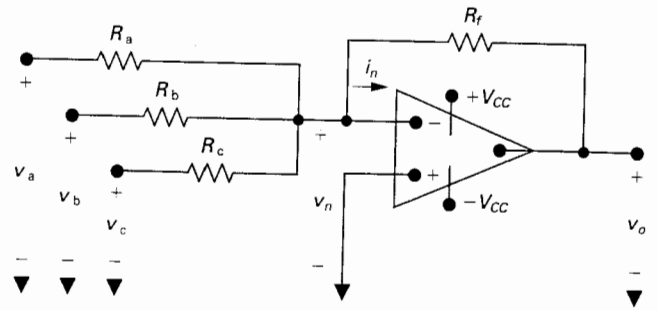


A summing amplifier.
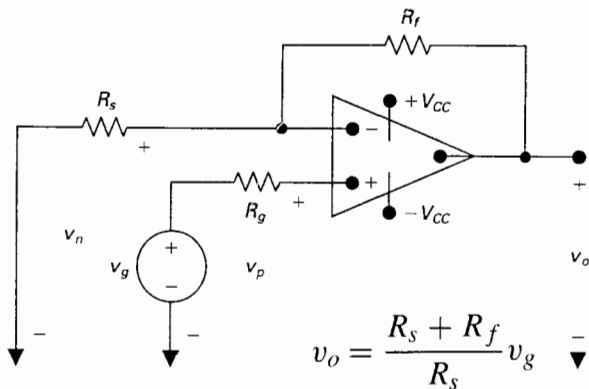
$$v_o = -\left(\frac{R_f}{R_a} v_a + \frac{R_f}{R_b} v_b + \frac{R_f}{R_c} v_c\right)$$




A noninverting amplifier.

$$v_o = \frac{R_s + R_f}{R_s} v_g$$

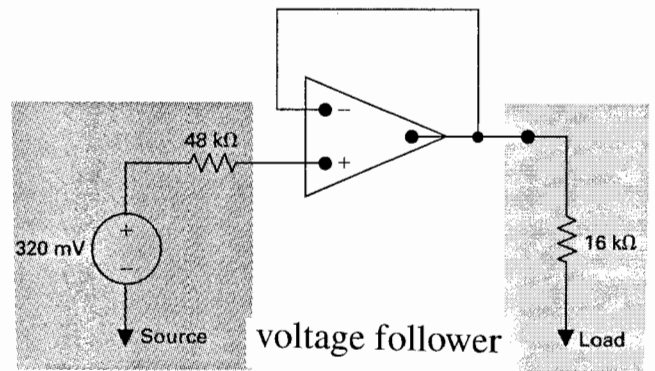


voltage follower

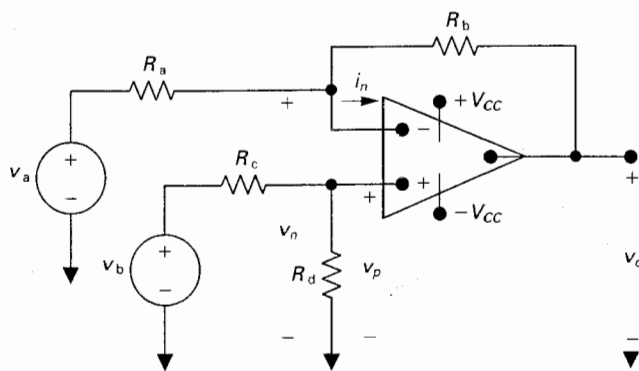

A difference amplifier.
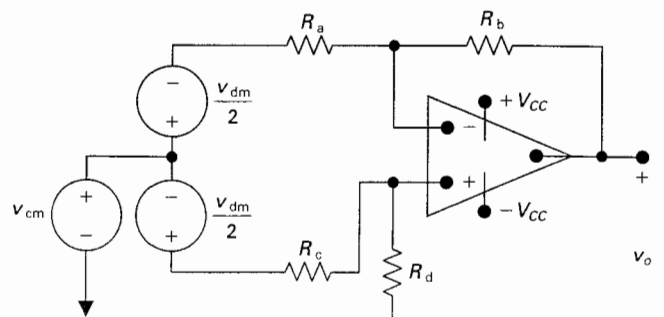
$$v_o = \frac{R_d(R_a + R_b)}{R_a(R_c + R_d)} v_b - \frac{R_b}{R_a} v_a$$



$$v_{cm} = (v_a + v_b)/2 \quad v_{dm} = v_b - v_a$$

$$v_o = \left[\frac{R_a R_d - R_b R_c}{R_a(R_c + R_d)}\right] v_{cm} + \left[\frac{R_d(R_a + R_b) + R_b(R_c + R_d)}{2R_a(R_c + R_d)}\right] v_{dm}$$

$$= A_{cm} v_{cm} + A_{dm} v_{dm}$$

Now, substitute  $R_c = R_a$  and  $R_d = R_b$ .

$$v_o = (0) v_{cm} + \left(\frac{R_b}{R_a}\right) v_{dm}$$