

HOW TO GET POWER: Read **The Prince** by N. Machiavelli.

HOW TO DEFINE IT: Power(watts) is energy(joules) per unit time(seconds).

To move charge  $q$  "upward" across potential difference  $v$  takes energy  $E = vq$ .

A charge  $q$  "falling" from higher to lower potential gains energy  $E = vq$ .

This energy has to be dissipated somewhere.

If this happens continuously in time, as with *current* (flowing charge),

$$\text{Power(watts)} = \frac{dE}{dt} = \frac{d}{dt}(vq) = v \frac{dq}{dt} = vi = (\text{volts})(\text{amps}).$$

If potential difference caused by resistor for which  $v = iR$ , Power= $vi = i^2R = v^2/R$ .

Note this is always non-negative. Makes sense: resistors dissipate power (get warm).

### Instantaneous and Average Power for Sinusoidal Voltages and Currents

Now let  $v(t) = V_0 \cos(\omega t + \phi)$  for any  $\omega \neq 0, V_0, \phi$ .

DEF: *Instantaneous power* dissipated= $p(t) = v(t)i(t) = i^2(t)R = v^2(t)/R$ .

$$\text{Here } p(t) = \frac{1}{R} V_0^2 \cos^2(\omega t + \phi) = \frac{1}{R} V_0^2 \frac{1}{2} (1 + \cos(2\omega t + 2\phi)).$$

This is a sinusoid+constant, and the frequency of the sinusoid has doubled.

DEF: *Average power* dissipated= $\bar{p} = \frac{1}{P} \int_{t_0}^{t_0+P} p(t) dt$  where  $P = \frac{2\pi}{\omega}$ =period. Here

$$\bar{p} = \frac{1}{P} \int_{t_0}^{t_0+P} \frac{1}{R} V_0^2 \frac{1}{2} (1 + \cos(2\omega t + 2\phi)) dt = \frac{V_0^2}{2R} + \frac{V_0^2}{2R} \frac{1}{P} \int_{t_0}^{t_0+P} \cos(2\omega t + 2\phi) dt = \frac{V_0^2}{2R}.$$

IN WORDS: the average value of a constant is the constant (here  $\frac{V_0^2}{2R}$ );

the average value of a sinusoid over an integer number of periods is zero.

### RMS (Root Mean Square) Voltage and Current

Being lazy, we would like to use the same formulae  $vi = i^2R = v^2/R$  for both *constant*  $v$  and  $i$  and *sinusoidal*  $v$  and  $i$ .

We can do this by defining the **rms voltage** to be  $V_{rms} = \frac{V_0}{\sqrt{2}}$ ,

so that  $V_{rms}$  is the peak value of voltage divided by  $\sqrt{2}$ .

Average power dissipated is  $\bar{p} = \frac{V_{rms}^2}{R} = \frac{V_0^2}{2R}$  which agrees with the correct answer.

Similarly, we define the **rms current** to be  $I_{rms} = I_0/\sqrt{2}$  where  $I_0 = \frac{V_0}{R}$ ,

so that  $I_{rms}$  is the peak value of current divided by  $\sqrt{2}$ .

Average power dissipated is  $\bar{p} = I_{rms}^2 R = I_0^2 R/2 = \frac{V_0^2}{2R}$ , again correct.

EXAMPLE: A wall socket puts out about  $v(t) = 170 \cos(2\pi 60t)$  volts.

$V_{rms} = \frac{170}{\sqrt{2}} = 120$  volts, which sounds familiar.

But the *peak* voltage at the wall socket is 170 volts!