

# Fault Modeling

- Why model faults?
- Some real defects in VLSI and PCB
- Common fault models
- Stuck-at faults
  - Single stuck-at faults
  - Fault equivalence
  - Fault dominance and checkpoint theorem
  - Classes of stuck-at faults and multiple faults
- Transistor faults
- Summary

# Why Model Faults?

- I/O function tests inadequate for manufacturing (functionality versus component and interconnect testing)
- Real defects (often mechanical) too numerous and often not analyzable
- A fault model identifies targets for testing
- A fault model makes analysis possible
- Effectiveness measurable by experiments

# Some Real Defects in Chips

- Processing defects
  - Missing contact windows
  - Parasitic transistors
  - Oxide breakdown
  - . . .
- Material defects
  - Bulk defects (cracks, crystal imperfections)
  - Surface impurities (ion migration)
  - . . .
- Time-dependent failures
  - Dielectric breakdown
  - Electromigration
  - . . .
- Packaging failures
  - Contact degradation
  - Seal leaks
  - . . .

Ref.: M. J. Howes and D. V. Morgan, *Reliability and Degradation - Semiconductor Devices and Circuits*, Wiley, 1981.

# Observed PCB Defects

Defect classes	Occurrence frequency (%)
Shorts	51
Opens	1
Missing components	6
Wrong components	13
Reversed components	6
Bent leads	8
Analog specifications	5
Digital logic	5
Performance (timing)	5


Ref.: J. Bateson, *In-Circuit Testing*, Van Nostrand Reinhold, 1985.

# Common Fault Models

- Single stuck-at faults
- Transistor open and short faults
- Memory faults
- PLA faults (stuck-at, cross-point, bridging)
- Functional faults (processors)
- Delay faults (transition, path)
- Analog faults
- For more examples, see Section 4.4 (p. 60-70) of the book.
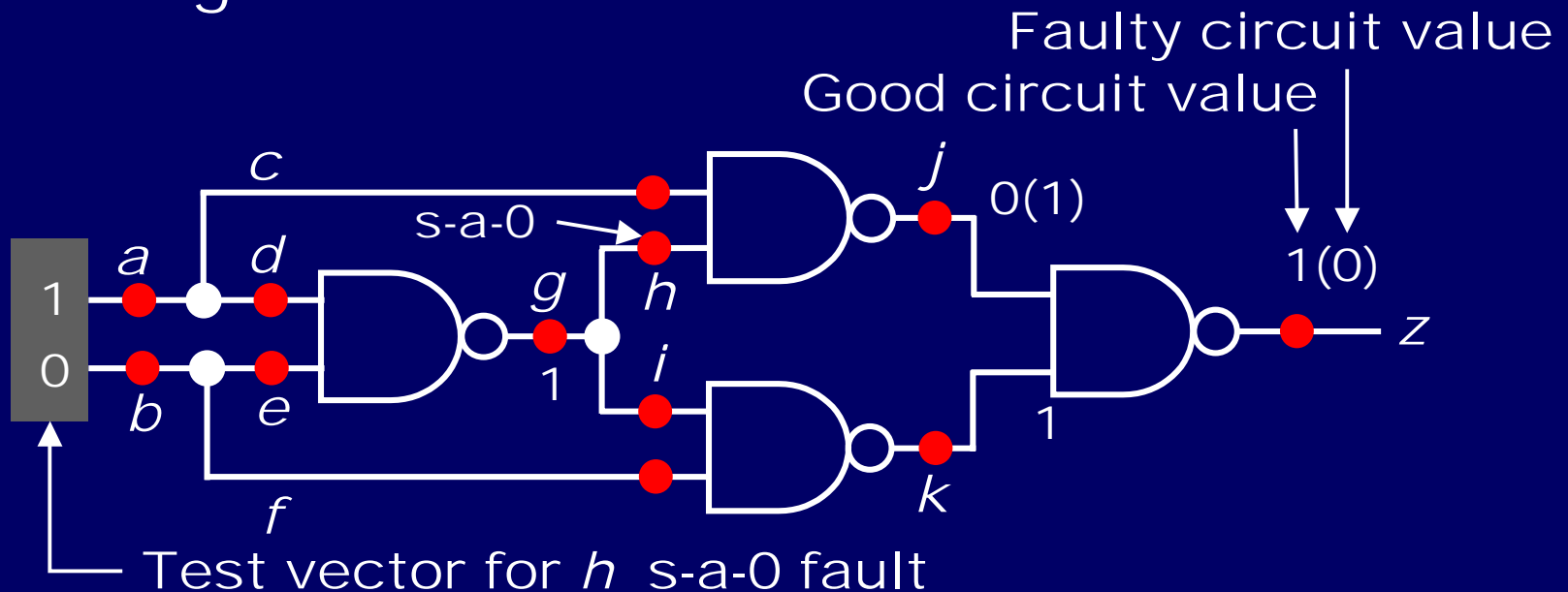
# Single Stuck-at Fault








- Three properties define a single stuck-at fault
  - Only one line is faulty
  - The faulty line is permanently set to 0 or 1
  - The fault can be at an input or output of a gate
- Example: XOR circuit has 12 fault sites (●) and 24 single stuck-at faults



# Fault Equivalence


- Number of fault sites in a Boolean gate circuit =  $\#PI + \#gates + \#(fanout\ branches)$ .
- Fault equivalence: Two faults  $f_1$  and  $f_2$  are equivalent if all tests that detect  $f_1$  also detect  $f_2$ .
- If faults  $f_1$  and  $f_2$  are equivalent then the corresponding faulty functions are identical.
- Fault collapsing: All single faults of a logic circuit can be divided into disjoint equivalence subsets, where all faults in a subset are mutually equivalent. A collapsed fault set contains one fault from each equivalence subset.

# Equivalence Rules

 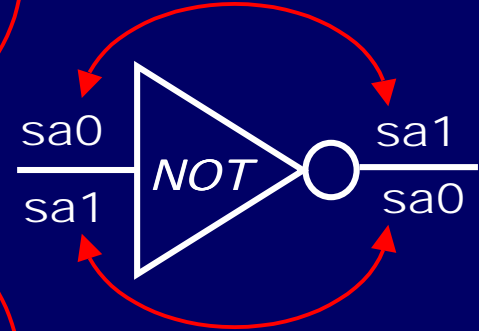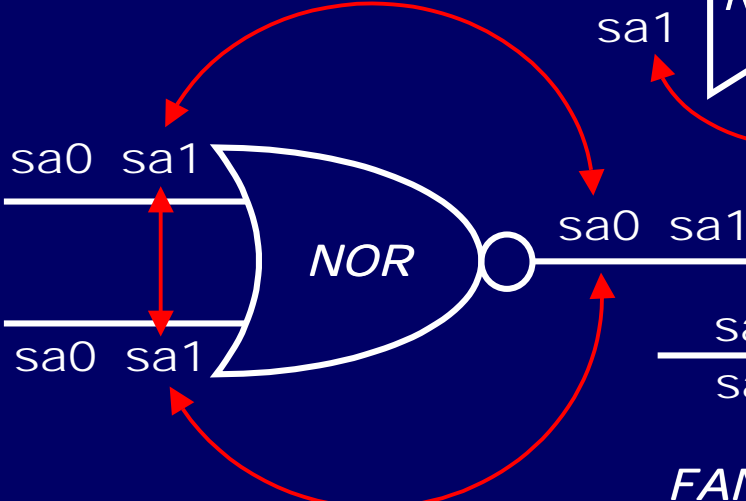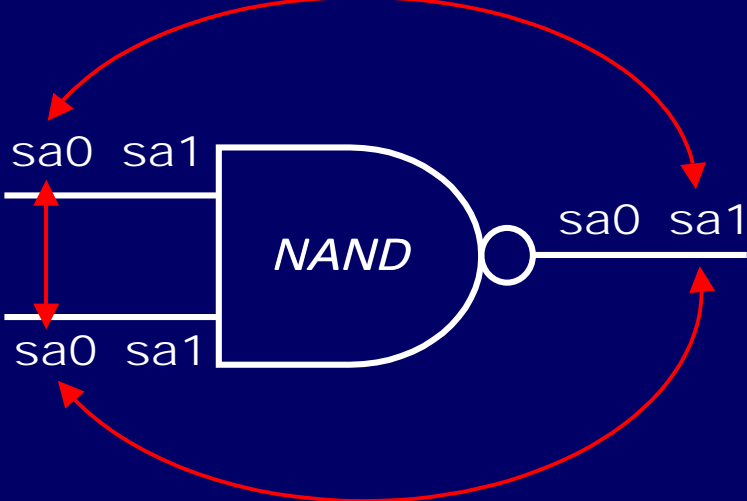 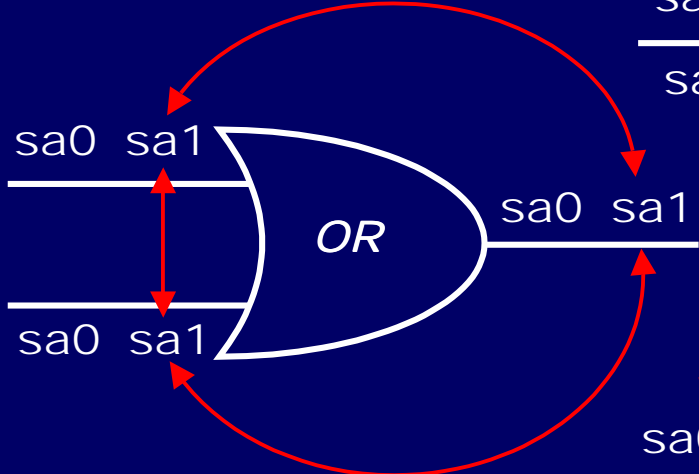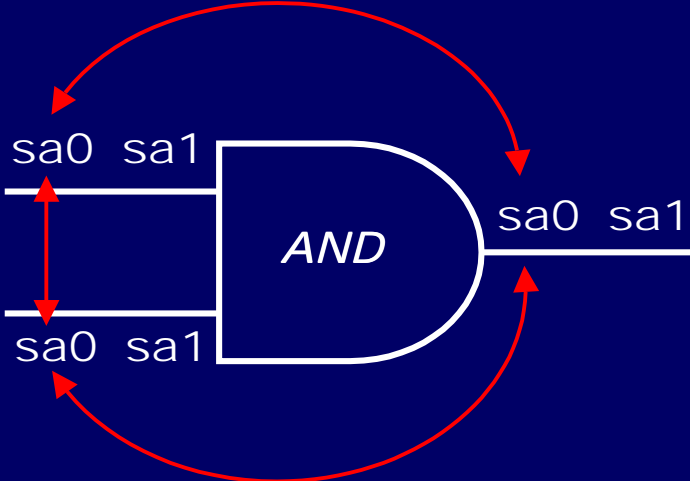




# Equivalence Example

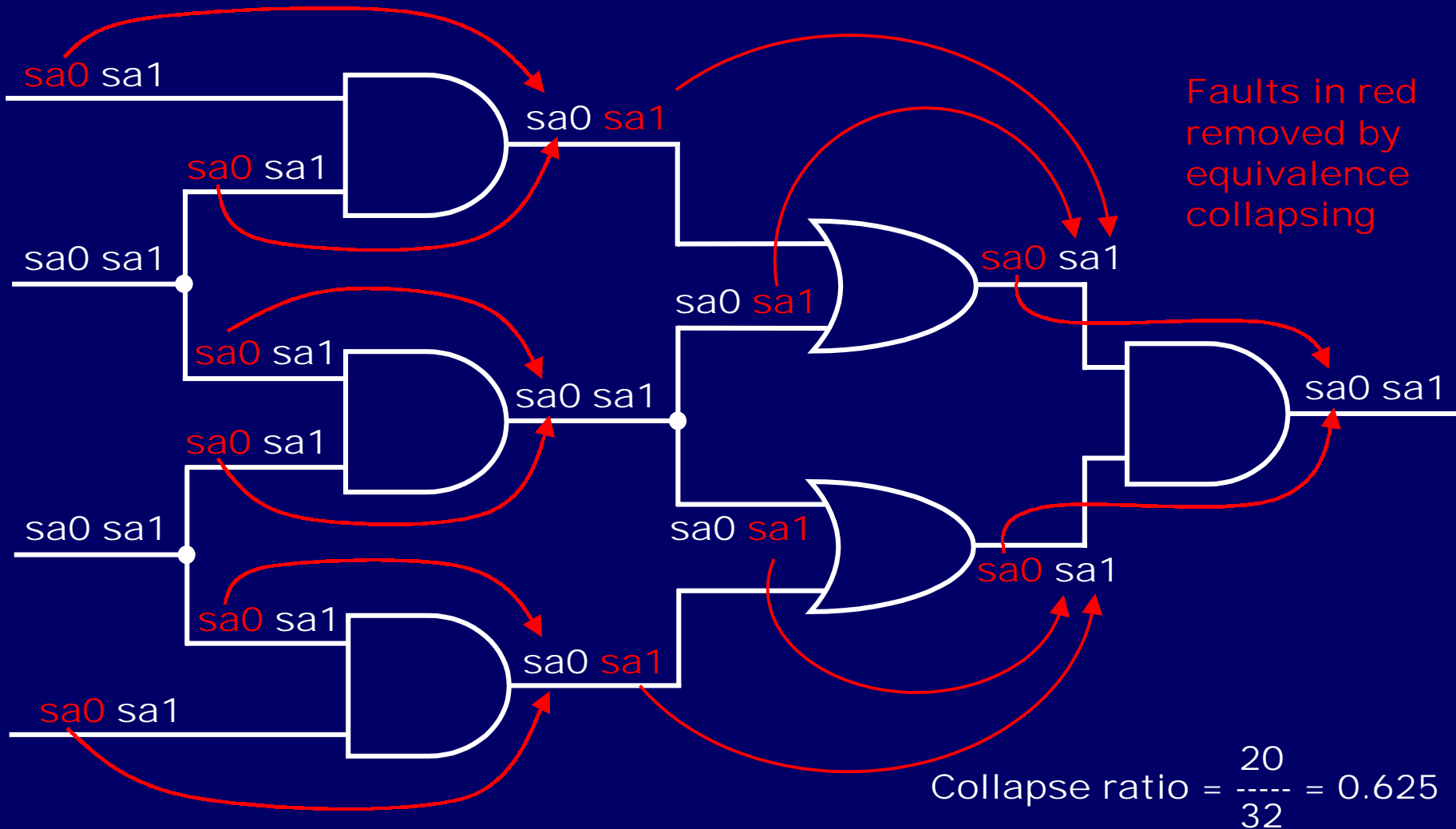

# Fault Dominance


- If all tests of some fault F1 detect another fault F2, then F2 is said to dominate F1.
- Dominance fault collapsing: If fault F2 dominates F1, then F2 is removed from the fault list.
- When dominance fault collapsing is used, it is sufficient to consider only the input faults of Boolean gates. See the next example.
- In a tree circuit (without fanouts) PI faults form a dominance collapsed fault set.
- If two faults dominate each other then they are equivalent.

# Dominance Example

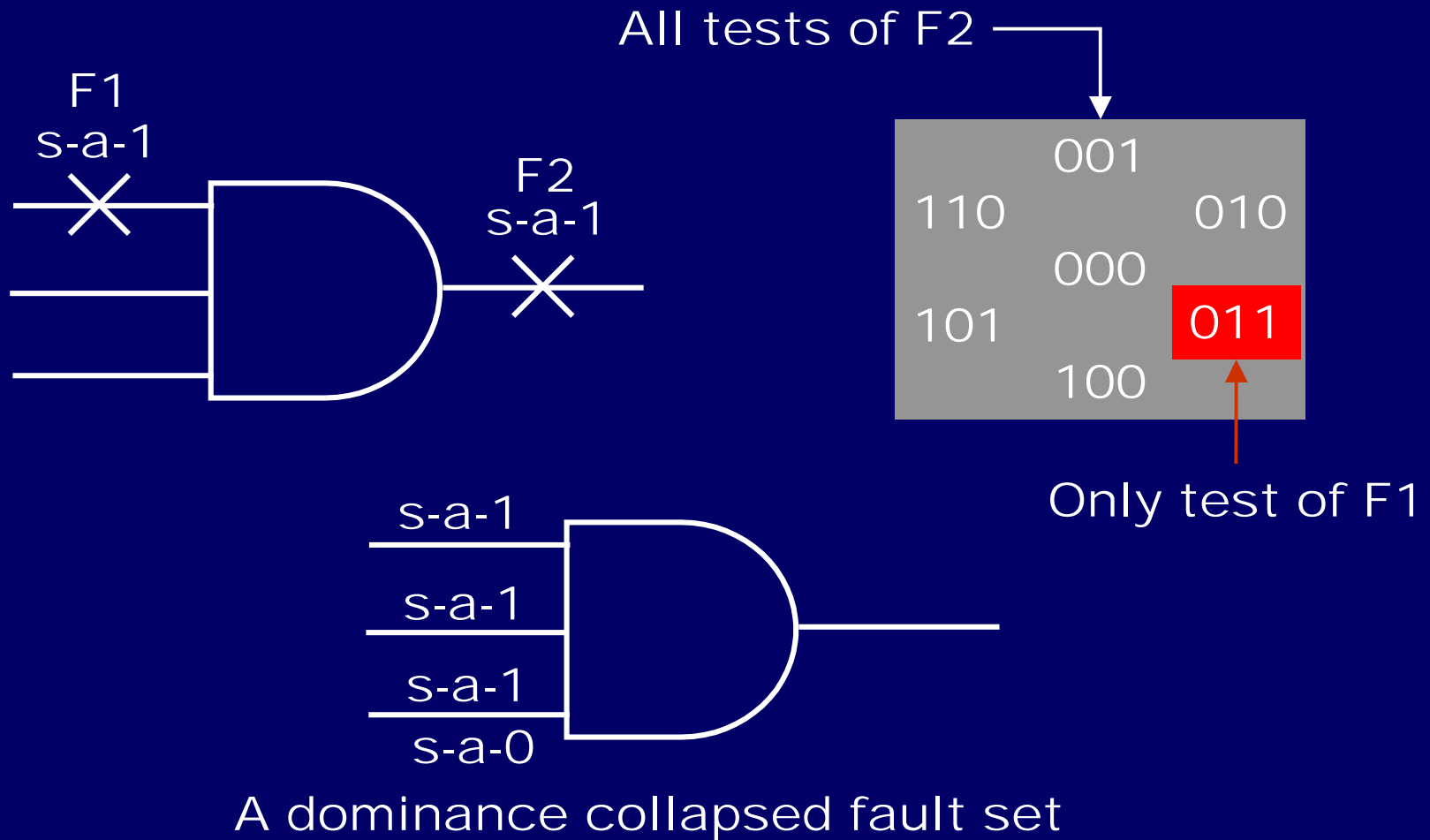
 
# Checkpoints

- Primary inputs and fanout branches of a combinational circuit are called *checkpoints*.
- Checkpoint theorem: A test set that detects all single (multiple) stuck-at faults on all checkpoints of a combinational circuit, also detects all single (multiple) stuck-at faults in that circuit.



# Classes of Stuck-at Faults

- Following classes of single stuck-at faults are identified by fault simulators:
  - *Potentially-detectable fault* -- Test produces an unknown (X) state at *primary output* (PO); detection is probabilistic, usually with 50% probability.
  - *Initialization fault* -- Fault prevents initialization of the faulty circuit; can be detected as a potentially-detectable fault.
  - *Hyperactive fault* -- Fault induces much internal signal activity without reaching PO.
  - *Redundant fault* -- No test exists for the fault.
  - *Untestable fault* -- Test generator is unable to find a test.

# Multiple Stuck-at Faults

- A multiple stuck-at fault means that any set of lines is stuck-at some combination of (0,1) values.
- The total number of single and multiple stuck-at faults in a circuit with  $k$  single fault sites is  $3^k - 1$ .
- A single fault test can fail to detect the target fault if another fault is also present, however, such masking of one fault by another is rare.
- Statistically, single fault tests cover a very large number of multiple faults.

# Transistor (Switch) Faults



- MOS transistor is considered an ideal switch and two types of faults are modeled:
  - Stuck-open -- a single transistor is permanently stuck in the open state.
  - Stuck-short -- a single transistor is permanently shorted irrespective of its gate voltage.
- Detection of a stuck-open fault requires two vectors.
- Detection of a stuck-short fault requires the measurement of quiescent current ( $I_{DDQ}$ ).

# Stuck-Open Example

Vector 1: test for A s-a-0  
(Initialization vector)


Vector 2 (test for A s-a-1)

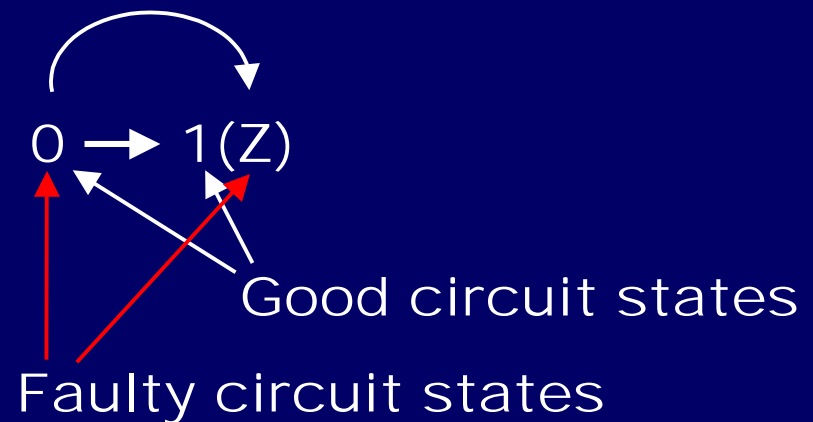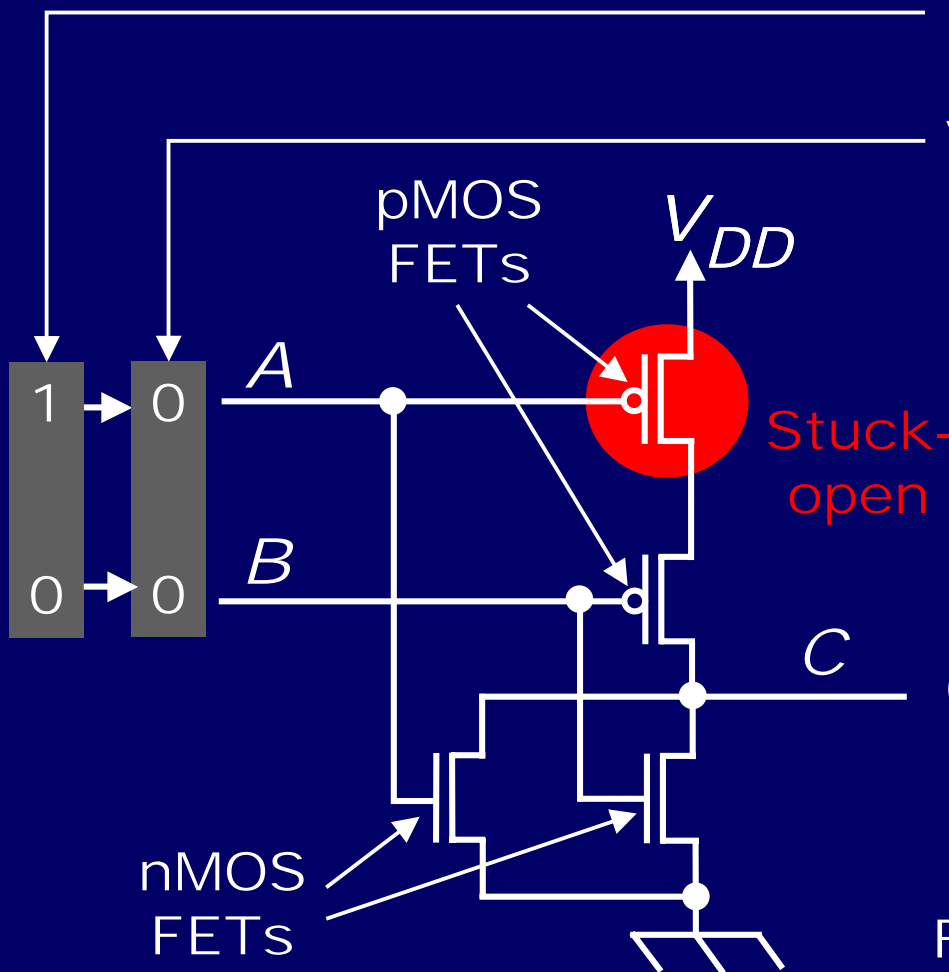*Two-vector s-op test  
can be constructed by  
ordering two s-at tests*





# Stuck-Short Example

 

# Summary

- Fault models are analyzable approximations of defects and are essential for a test methodology.
- For digital logic single stuck-at fault model offers best advantage of tools and experience.
- Many other faults (bridging, stuck-open and multiple stuck-at) are largely covered by stuck-at fault tests.
- Stuck-short and delay faults and technology-dependent faults require special tests.
- Memory and analog circuits need other specialized fault models and tests.


# Logic Simulation

- What is simulation?
- Design verification
- Circuit modeling
- True-value simulation algorithms
  - Compiled-code simulation
  - Event-driven simulation
- Summary

# Simulation Defined

- Definition: Simulation refers to modeling of a design, its function and performance.
- A software simulator is a computer program; an emulator is a hardware simulator.
- Simulation is used for design verification:
  - Validate assumptions
  - Verify logic
  - Verify performance (timing)
- Types of simulation:
  - Logic or switch level
  - Timing
  - Circuit
  - Fault


# Simulation for Verification

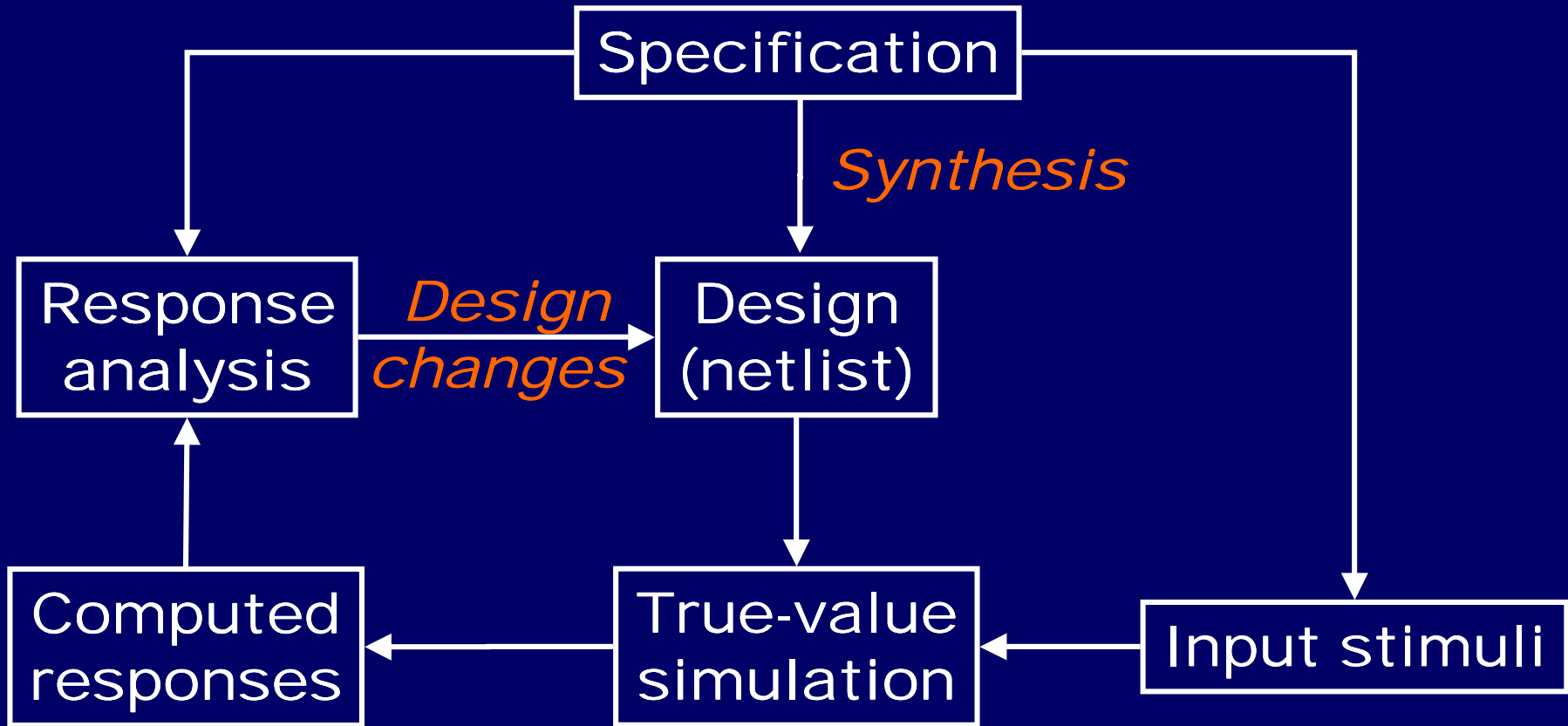

# Modeling for Simulation

- Modules, blocks or components described by
  - Input/output (I/O) function
  - Delays associated with I/O signals
  - Examples: binary adder, Boolean gates, FET, resistors and capacitors
- Interconnects represent
  - ideal signal carriers, or
  - ideal electrical conductors
- Netlist: a format (or language) that describes a design as an interconnection of modules. Netlist may use hierarchy.

# Example: A Full-Adder

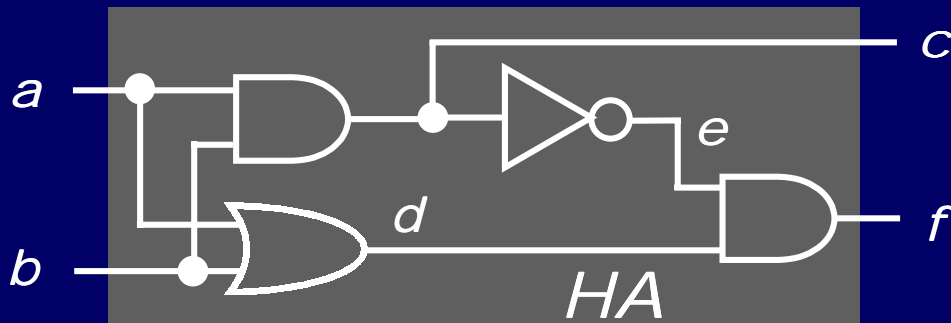


HA;  
 inputs:  $a, b$ ;  
 outputs:  $c, f$ ;  
 AND: A1, ( $a, b$ ), ( $c$ );  
 AND: A2, ( $d, e$ ), ( $f$ );  
 OR: O1, ( $a, b$ ), ( $d$ );  
 NOT: N1, ( $c$ ), ( $e$ );




FA;  
 inputs:  $A, B, C$ ;  
 outputs: Carry, Sum;  
 HA: HA1, ( $A, B$ ), ( $D, E$ );  
 HA: HA2, ( $E, C$ ), ( $F, \text{Sum}$ );  
 OR: O2, ( $D, F$ ), (Carry);

# Logic Model of MOS Circuit

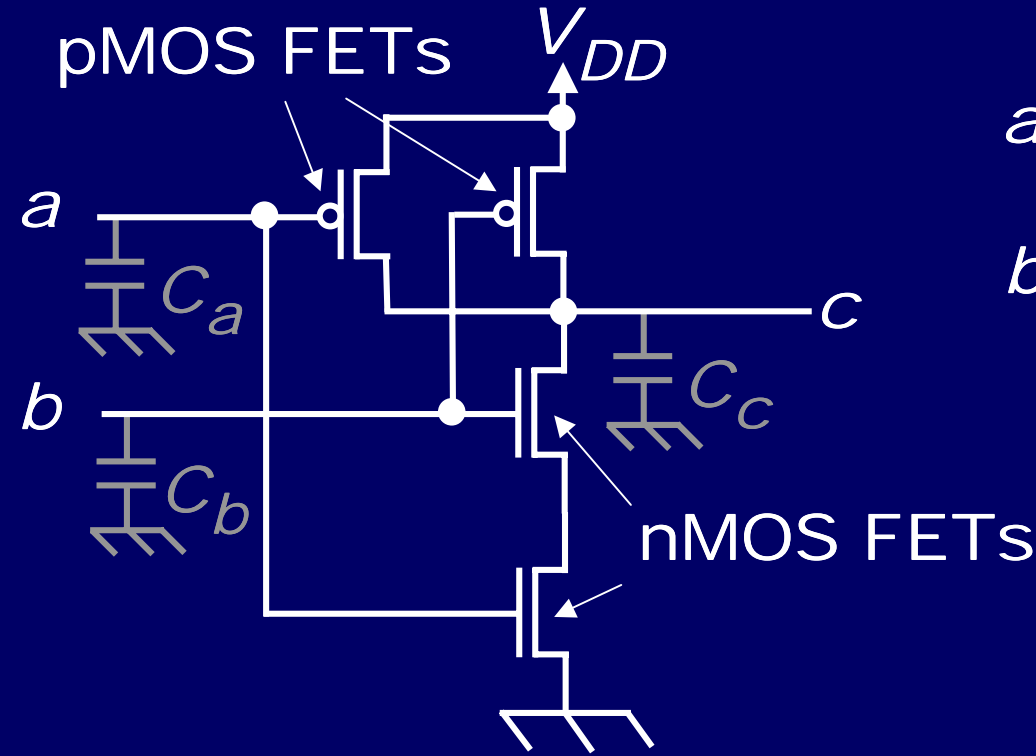

 $C_a$ ,  $C_b$  and  $C_c$  are parasitic capacitances




$D_a$  and  $D_b$  are interconnect or propagation delays

$D_c$  is inertial delay of gate




# Options for Inertial Delay

(simulation of a NAND gate)

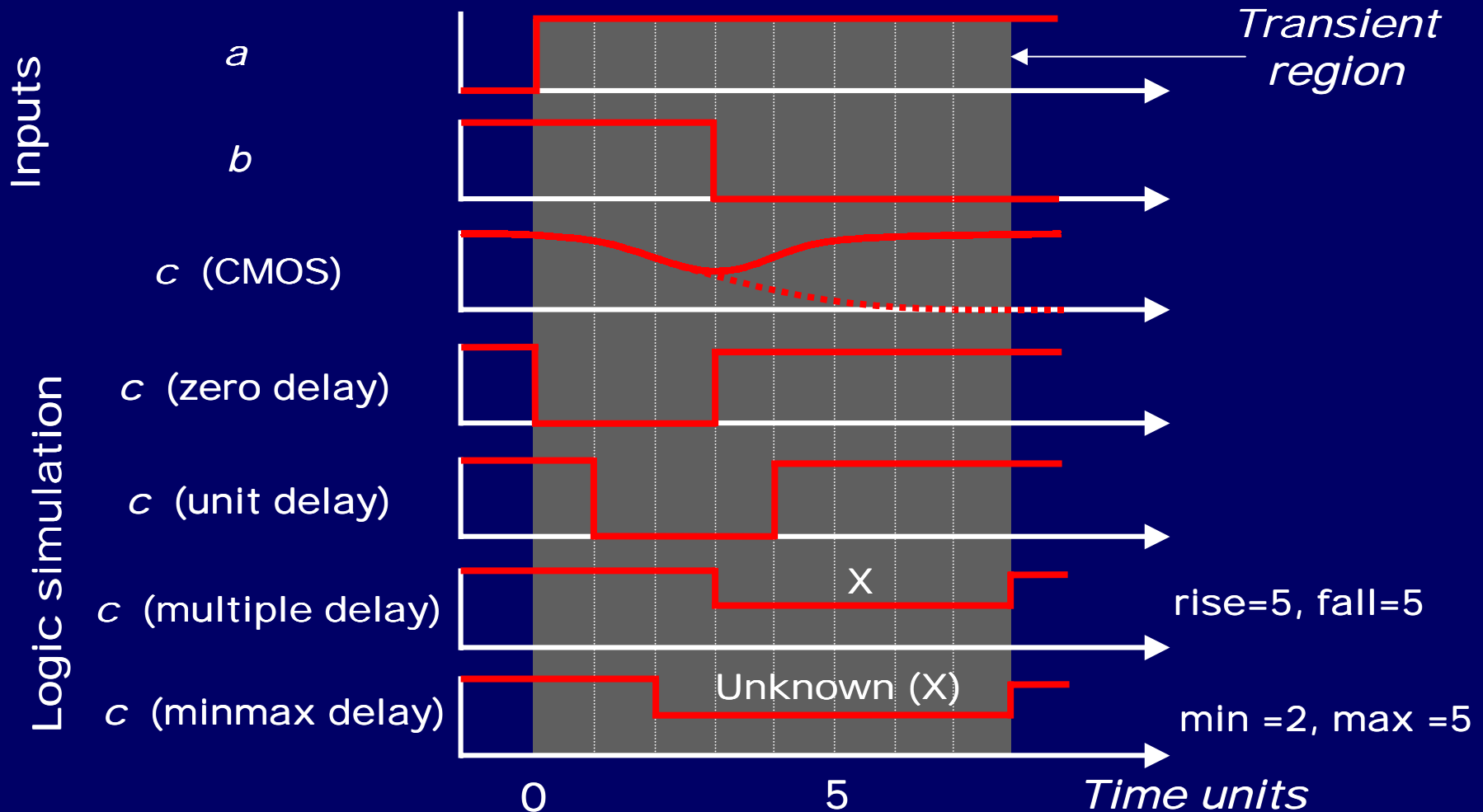
 
# Signal States

- Two-states (0, 1) can be used for purely combinational logic with zero-delay.
- Three-states (0, 1, X) are essential for timing hazards and for sequential logic initialization.
- Four-states (0, 1, X, Z) are essential for MOS devices. See example below.
- Analog signals are used for exact timing of digital logic and for analog circuits.



# Modeling Levels

Modeling level	Circuit description	Signal values	Timing	Application
Function, behavior, RTL	Programming language-like HDL	0, 1	Clock boundary	Architectural and functional verification
Logic	Connectivity of Boolean gates, flip-flops and transistors	0, 1, X and Z	Zero-delay unit-delay, multiple-delay	Logic verification and test
Switch	Transistor size and connectivity, node capacitances	0, 1 and X	Zero-delay	Logic verification
Timing	Transistor technology data, connectivity, node capacitances	Analog voltage	Fine-grain timing	Timing verification
Circuit	Tech. Data, active/passive component connectivity	Analog voltage, current	Continuous time	Digital timing and analog circuit verification



# True-Value Simulation Algorithms

- Compiled-code simulation
  - Applicable to zero-delay combinational logic
  - Also used for cycle-accurate synchronous sequential circuits for logic verification
  - Efficient for highly active circuits, but inefficient for low-activity circuits
  - High-level (e.g., C language) models can be used
- Event-driven simulation
  - Only gates or modules with input events are evaluated (*event means a signal change*)
  - Delays can be accurately simulated for timing verification
  - Efficient for low-activity circuits
  - Can be extended for fault simulation

# Compiled-Code Algorithm

- Step 1: Levelize combinational logic and encode in a compilable programming language
- Step 2: Initialize internal state variables (flip-flops)
- Step 3: For each input vector
  - Set primary input variables
  - Repeat (until steady-state or max. iterations)
    - Execute compiled code
  - Report or save computed variables

# Event-Driven Algorithm (Example)

  


Time stack

t = 0
1
2
3
4
5
6
7
8


Scheduled events	Activity list
$c = 0$	$d, e$
$d = 1, e = 0$	$f, g$
$g = 0$	
$f = 1$	$g$
$g = 1$	

# Time Wheel (Circular Stack)

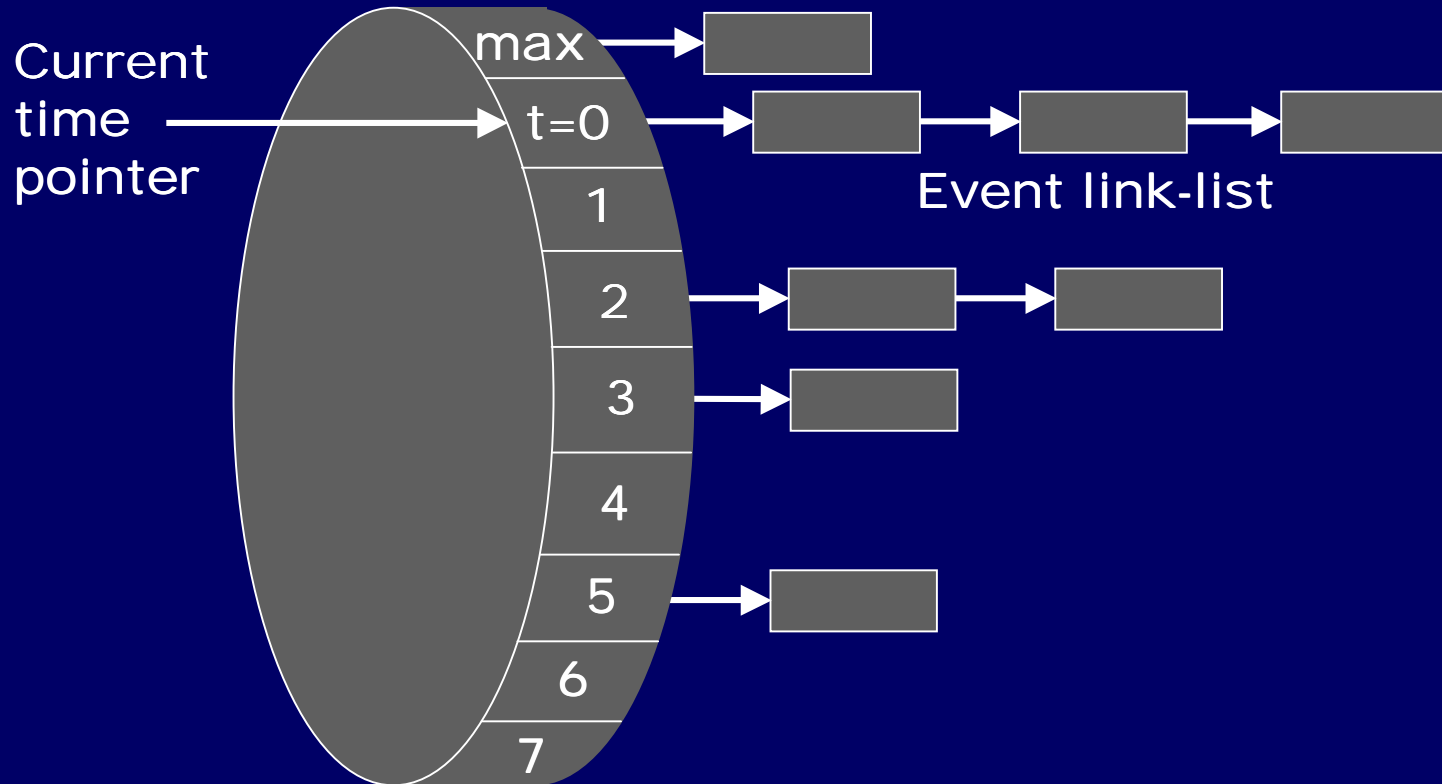
 
# Efficiency of Event-driven Simulator

- Simulates events (value changes) only
- Speed up over compiled-code can be ten times or more; in large logic circuits about 0.1 to 10% gates become active for an input change





# Summary

- Logic or true-value simulators are essential tools for design verification.
- Verification vectors and expected responses are generated (often manually) from specifications.
- A logic simulator can be implemented using either compiled-code or event-driven method.
- Per vector complexity of a logic simulator is approximately linear in circuit size.
- Modeling level determines the evaluation procedures used in the simulator.