


## Combinational Automatic Test-Pattern Generation (ATPG) Basics

- Algorithms and representations
- Structural vs. functional test
- Definitions
- Search spaces
- Completeness
- Algebras
- Types of Algorithms


## Origins of Stuck-Faults

- Eldred (1959) - First use of structural testing for the Honeywell *Datamatic 1000* computer
- Galey, Norby, Roth (1961) - First publication of stuck-at-0 and stuck-at-1 faults
- Seshu & Freeman (1962) - Use of stuck-faults for parallel fault simulation
- Poage (1963) - Theoretical analysis of stuck-at faults

## Functional vs. Structural ATPG

 

## Carry Circuit

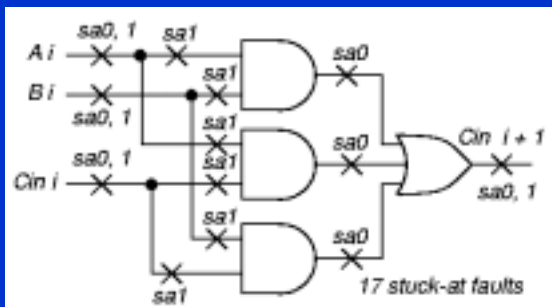


## Functional vs. Structural (Continued)

- Functional ATPG – generate complete set of tests for circuit input-output combinations
  - 129 inputs, 65 outputs:
  - $2^{129} = 680,564,733,841,876,926,926,749,214,863,536,422,912$  patterns
  - Using 1 GHz ATE, would take  $2.15 \times 10^{22}$  years
- Structural test:
  - No redundant adder hardware, 64 bit slices
  - Each with 27 faults (using fault equivalence)
  - At most  $64 \times 27 = 1728$  faults (tests)
  - Takes 0.000001728 s on 1 GHz ATE
- Designer gives small set of functional tests – augment with structural tests to boost coverage to 98+ %

## Definition of Automatic Test-Pattern Generator


- Operations on digital hardware:
  - Inject fault into circuit modeled in computer
  - Use various ways to activate and propagate fault effect through hardware to circuit output
  - Output flips from expected to faulty signal
- Electron-beam (E-beam) test observes internal signals – “picture” of nodes charged to 0 and 1 in different colors
  - Too expensive
- Scan design – add test hardware to all flip-flops to make them a giant shift register in test mode
  - Can shift state in, scan state out
  - Widely used – makes sequential test combinational
  - Costs: 5 to 20% chip area, circuit delay, extra pin, longer test sequence

## Circuit and Binary Decision Tree

 
 
## Binary Decision Diagram

- BDD – Follow path from source to sink node – product of literals along path gives Boolean value at sink
- Rightmost path:  $A \bar{B} \bar{C} = 1$
- Problem: Size varies greatly with variable order



## Algorithm Completeness

- Definition: Algorithm is *complete* if it ultimately can search entire binary decision tree, as needed, to generate a test
- *Untestable fault* - no test for it even after entire tree searched
- Combinational circuits only - untestable faults are *redundant*, showing the presence of unnecessary hardware

## Algebras: Roth's 5-Valued and Muth's 9-Valued

Symbol	Meaning	Good Machine	Failing Machine	
$\overline{D}$	1/0	1	0	Roth's Algebra
$\overline{D}$	0/1	0	1	
0	0/0	0	0	
1	1/1	1	1	
X	X/X	X	X	
G0	0/X	0	X	Muth's Additions
G1	1/X	1	X	
F0	X/0	X	0	
F1	X/1	X	1	

## Roth's and Muth's Higher-Order Algebras

- Represent two machines, which are simulated simultaneously by a computer program:
  - Good circuit machine (1<sup>st</sup> value)
  - Bad circuit machine (2<sup>nd</sup> value)
- Better to represent both in the algebra:
  - Need only 1 pass of ATPG to solve both
  - Good machine values that preclude bad machine values become obvious sooner & vice versa
- Needed for complete ATPG:
  - Combinational: Multi-path sensitization, Roth Algebra
  - Sequential: Muth Algebra -- good and bad machines may have different initial values due to fault

## Exhaustive Algorithm


- For  $n$ -input circuit, generate all  $2^n$  input patterns
- Infeasible, unless circuit is partitioned into cones of logic, with  $\leq 15$  inputs
  - Perform exhaustive ATPG for each cone
  - Misses faults that require specific activation patterns for multiple cones to be tested

## Random-Pattern Generation

- Flow chart for method
- Use to get tests for 60-80% of faults, then switch to D-algorithm or other ATPG for rest


 
## Boolean Difference Symbolic Method (Sellers *et al.*)



$$g = G(X_1, X_2, \dots, X_n) \quad \text{for the fault site}$$

$$f_j = F_j(g, X_1, X_2, \dots, X_n)$$

$$1 \leq j \leq m$$

$$X_i = 0 \text{ or } 1 \text{ for } 1 \leq i \leq n$$

## Boolean Difference (Sellers, Hsiao, Bearnson)

- Shannon's Expansion Theorem:  

$$F(X_1, X_2, \dots, X_n) = X_2 \cdot F(X_1, 1, \dots, X_n) + \overline{X_2} \cdot F(X_1, 0, \dots, X_n)$$
- Boolean Difference (partial derivative):  


$$\frac{\partial F_j}{\partial g} = F_j(1, X_1, X_2, \dots, X_n) \oplus F_j(0, X_1, \dots, X_n)$$
- Fault Detection Requirements:  

$$G(X_1, X_2, \dots, X_n) = 1$$

$$\frac{\partial F_j}{\partial g} = F_j(1, X_1, X_2, \dots, X_n) \oplus F_j(0, X_1, \dots, X_n) = 1$$

 
## Path Sensitization Method Circuit Example

- 1 Fault Sensitization
- 2 Fault Propagation
- 3 Line Justification



 
## Path Sensitization Method Circuit Example

- Try path  $f-h-k-L$  blocked at  $j$ , since there is no way to justify the 1 on  $i$



 
## Path Sensitization Method Circuit Example

- Try simultaneous paths  $f-h-k-L$  and  $g-l-j-k-L$  blocked at  $k$  because  $D$ -frontier (chain of  $D$  or  $\bar{D}$ ) disappears


 
## Path Sensitization Method Circuit Example

- Final try: path  $g-l-j-k-L$  - test found!



## Boolean Satisfiability

- 2SAT:  $x_j \bar{x}_j + x_j \bar{x}_k + x_l \bar{x}_m \dots = 0$

$$x_p x_y + x_r \bar{x}_s + x_t \bar{x}_u \dots = 0$$

- 3SAT:  $x_j \bar{x}_j x_k + x_j \bar{x}_k \bar{x}_l + x_l \bar{x}_m \bar{x}_n \dots = 0$

$$x_p x_y + x_r \bar{x}_s x_t + x_t x_u \bar{x}_v \dots = 0$$

## Satisfiability Example for AND Gate

- $\sum a_k b_k c_k = 0$  (non-tautology) or
- $\prod (a_k + b_k + c_k) = 1$  (satisfiability)



- AND gate signal relationships:
  - If  $a = 0$ , then  $z = 0$
  - If  $b = 0$ , then  $z = 0$
  - If  $z = 1$ , then  $a = 1$  AND  $b = 1$
  - If  $a = 1$  AND  $b = 1$ , then  $z = 1$
- Sum to get:  $\overline{a}z + \overline{b}z + ab\overline{z} = 0$   
(third relationship is redundant with 1<sup>st</sup> two)


Cube:  
 $\overline{a}z$   
 $\overline{b}z$   
 $zab$   
 $ab\overline{z}$

## Pseudo-Boolean and Boolean False Functions

- **Pseudo-Boolean function:** use ordinary + -- integer arithmetic operators
  - Complementation of  $x$  represented by  $1 - x$
  - $F_{pseudo-Bool} = 2z + ab - az - bz - abz = 0$
- **Energy function representation:** let any variable be in the range (0, 1) in pseudo-Boolean function
- **Boolean false expression:**  
 $f_{AND}(a, b, z) = z \oplus (ab) = \overline{a}z + \overline{b}z + ab\overline{z}$
 
## AND Gate Implication Graph

- Really efficient
- Each variable has 2 nodes, one for each literal
- If ... then clause represented by edge from if literal to then literal
- Transform into *transitive closure graph*
  - When node true, all reachable states are true
- ANDing operator  $\wedge$  used for 3SAT relations



## Computational Complexity

- Ibarra and Sahni analysis - *NP-Complete* (no polynomial expression found for compute time, presumed to be exponential)
- Worst case:
  - $no\_pl$  inputs,  $2^{no\_pl}$  input combinations
  - $no\_ff$  flip-flops,  $4^{no\_ff}$  initial flip-flop states
  - (good machine 0 or 1 × bad machine 0 or 1)
  - work to forward or reverse simulate  $n$  logic gates  $\alpha n$
- Complexity:  $O(n \times 2^{no\_pl} \times 4^{no\_ff})$

## History of Algorithm Speedups

Algorithm	Est. speedup over D-ALG (normalized to D-ALG time)	Year
D-ALG	1	1966
PODEM	7	1981
FAN	23	1983
TOPS	292	1987
SOCRATES	1574 † ATPG System	1988
Waicukauski et al.	2189 † ATPG System	1990
EST	8765 † ATPG System	1991
TRAN	3005 † ATPG System	1993
Recursive learning	485	1995
Tafertshofer et al.	25057	1997

## Analog Fault Modeling Impractical for Logic ATPG

- Huge # of different possible analog faults in digital circuit
- Exponential complexity of ATPG algorithm
  - a 20 flip-flop circuit can take days of computing
  - Cannot afford to go to a lower-level model
- Most test-pattern generators for digital circuits cannot even model at the transistor switch level (see textbook for 5 examples of switch-level ATPG)