 


EECS 373 - Fall 14 - Homework #1 - Key  
 Prabal Dutta

Q1a.  $F = (A+B') \cdot (A+C)$

A	B	C	$(A+B')$	$(A+C)$	F
0	0	0	1	0	0
0	0	1	1	1	1
0	1	0	0	0	0
0	1	1	0	1	0
1	0	0	1	1	1
1	0	1	1	1	1
1	1	0	1	1	1
1	1	1	1	1	1


Q1b.



Q2a.  $Z = S_0' \cdot A + S_0 \cdot B$


A	B	$S_0$	Z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Q2b.

 

A	B	$C_{in}$	$C_{out}$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Q3b.

 

Q4a.  $Y = (A \cdot B') + (B \cdot C') + (A \cdot C)$

↓ Verilog


assign Y = (A &amp; ~B) | (B &amp; ~C) | (~A &amp; C);

Q4b. Assume the following truth table:


$S_1$	$S_0$	Z
0	0	A
0	1	B
1	0	C
1	1	D

↓ Verilog

assign Z = ( $\neg S_1 \cdot \neg S_0 \cdot A$ ) | ( $\neg S_1 \cdot S_0 \cdot B$ ) ...  
 | ( $S_1 \cdot \neg S_0 \cdot C$ ) | ( $S_1 \cdot S_0 \cdot D$ );

 

↓ redrawn using 2 input gates

 


Q5a.  $Z = f(A, B, C, D, S_0, S_1) \rightarrow$   
 $\downarrow \text{Verilog}$

$S_1$	$S_0$	$Z$
0	0	A
0	1	B
1	0	C
1	1	D

} Next truth  
table

```
module MUX41(A, B, C, D, S0, S1, Z);
    input A, B, C, D, S0, S1;
    output Z;
    wire Z;
    assign Z = (S1, & S0 & A) | (S1, & S0 & B) | (S1, & S0 & C) | (S1, & S0 & D);
endmodule
```

 Q5b. The key here is realizing there will be some unused inputs in the last stage mux. A possible design:



Also, note that there are other possible designs. For example, if mux M3's S<sub>1</sub> and S<sub>0</sub> inputs are connected to φ and S[2], respectively, then M3.A = tmp1 and M3.B = tmp2, rather than the way it is drawn here.

$$Z = f(A[7:0], S[2:0])$$

$\downarrow \text{Verilog}$

```
module MUX81(A, S, Z);
```

```
input [7:0] A;
```

```
input [2:0] S;
```

```
output Z;
```

```
wire Z, tmp1, tmp2;
```

```
MUX41 M1 (A[6], A[5], A[4], A[3], S[0], S[1], tmp1);
```

```
MUX41 M2 (A[5], A[4], A[3], A[2], S[0], S[1], tmp2);
```

```
MUX41 M3 (tmp1, tmp2, S[2], S[3], Z);
```

```
endmodule
```

In this example, we didn't write out the entire parameter list in the module declaration, e.g.


module MUX81(A0, A1, A2, ..., A7, S0, S1, S2, Z);  
but instead chose to pass the arrays

Q6. In this case, Y must a reg and not a wire:



always @\*

$$Y = (A \& \neg B) | (B \& \neg C) | \neg (A \& C);$$

Q7.

 

  Q8. Build a modulo-4 counter:  $\overbrace{0 \rightarrow 1 \rightarrow 2 \rightarrow 3}$



Q10. Consider a D flip flop (DFF) :

with inputs D and CLK and output Q, as shown to the right:

- Setup time - the time before a rising edge of the CLK during which D must be stable (must not change)
- Hold time - the time after a rising edge of the clock during which D must be stable (must not change)

