

Advanced Verilog

EECS 270 v10/23/06

Continuous Assignments

review

- Continuously assigns right side of expression to left side.
- Limited to basic Boolean and ? operators. For example a 2:1 mux:
 - ? operator
`assign D = (A==1) ? B : C; // if A then D = B else D = C;`
 - Boolean operators
`assign D = (B & A) | (C & ~A); // if A then D = B else D = C;`

Procedural Assignments

- Executes a procedure allowing for more powerful constructs such as if-then-else and case statement.
- For example 2:1 mux:
 - if-then-else
if (A) then D = B else D = C;
 - case
case(A)
1'b1 : D = B;
1'b0 : D = C;
endcase

This is obviously much easier to implement and read than Boolean expressions!!

Always Block

- An always block is an example of a procedure.
- The procedure executes a set of assignments when a defined set of inputs **change**.

2:1 mux Always Block

```
Module mux_2_1(a, b, out, sel);  
  input a, b, sel;  
  output out;  
  
  reg out;  
  
  always @(a or b or sel)  
  
  begin  
    if (sel) out = a;  
    else out = b;  
  end  
  
endmodule
```

Declare Module and IO as before.

All data types in always blocks must be declared as a 'reg' type.

This is required even if the data type is for combinational logic.

The always block 'executes' whenever signals named in the sensitivity list change.

Literally: always execute at a or b or sel.

Sensitivity list should include conditional (sel) and right side (a, b) assignment variables.

As Easier Way to Implement the Sensitivity List

- Recent versions of Verilog provides a means to implement the sensitivity list without explicitly listing each potential variable.
- Instead of listing variables as in the previous example

```
always @(a or b or sel)
```

Simply use

```
always @*
```

The * operator will automatically identify all sensitive variables.

Blocking vs Non-Blocking Assignments

- Blocking (=) and non-blocking (<=) assignments are provided to control the execution order within an always block.
- Blocking assignments **literally block** the execution of the next statement until the current statement is executed.
 - **Consequently, blocking assignments result in ordered statement execution.**

For example:

```
assume a = b = 0 initially;  
a = 1;    //executed first  
b = a;    //executed second  
then a = 1, b = 1 after ordered execution
```

Blocking vs Non-Blocking Cont

- Non-blocking assignments **literally do not block** the execution of the next statements. The right side of all statements are determined first, then the left sides are assigned together.
 - **Consequently, non-blocking assignments result in simultaneous or parallel statement execution.**


For example:

```
assume a = b = 0 initially;  
a <= 1; }  
b <= a; } Execute together (in parallel)  
then a = 1, b = 0 after parallel execution
```

Result is different from ordered exec!!! Does not preserve logic flow

To Block or Not to Block ?

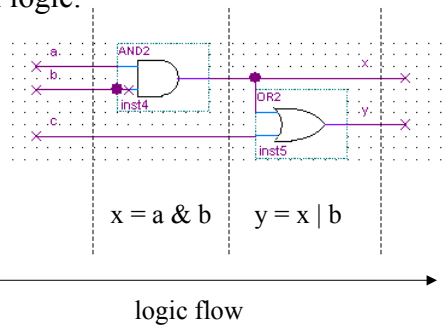- Ordered execution mimics the inherent logic flow of combinational logic.
- Hence blocking assignments generally work better for combinational logic.
- For example:



To Block or Not to Block ? cont

```

Module blocking(a,b,c,x,y);
  input a,b,c;
  output x,y;
  reg x,y;
  always @*
  begin
    x = a & b;
    y = x | c;
  end
endmodule

```

Blocking behavior	a	b	c	x	y
Initial values	1	1	0	1	1
a changes → always block execs	0	1	0	1	1
x = a & b; //make assignment	0	1	0	0	1
y = x c; //make assignment	0	1	0	0	0

```

Module nonblocking(a,b,c,x,y);
  input a,b,c;
  output x,y;
  reg x,y;
  always @*
  begin
    x <= a & b;
    y <= x | c;
  end
endmodule


```

Non-blocking behavior	a	b	c	x	y
Initial values	1	1	0	1	1
a changes → always block execs	0	1	0	1	1
x = a & b;	0	1	0	1	1
y = x c; //x not passed from here	0	1	0	1	1
make x, y assignments	0	1	0	0	1

non-blocking behavior does not preserve logic flow!!


Sequential Logic

 - Can be generalized as a series of combinational blocks with registers to hold results.



Sequential Example

 - Shift registers are used to implement multiplication/division and other functions.
- Consider a simple 2-bit “right” shift:




common clock

No combinational logic for simple shift, just simple pass thru

clk	D0	Q0	Q1
initial	1	0	0
rising edge	1	1	0
rising edge	0	0	1

Sequential Example Cont 1

 - Notice that the inputs of each stage are “evaluated” then latched into the registers at each rising clock edge.



Sequential Example Cont 2

- Because the shift logic evaluates inputs in parallel and latches result on a rising clk edge, a **non-blocking always** procedure sensitive to a rising clock can be used to implement.

```
1 module shft2b(clk, D0, Q0, Q1);  
2   input clk, D0;  
3   output Q0, Q1;  
4   reg Q0, Q1;  
5   always @ (posedge clk)  
6   begin  
7     Q0 <= D0;  
8     Q1 <= Q0;  
9   end  
10 endmodule
```

Sensitive to rising clock edge. Note that in this case we must explicitly specify sensitivity to the rising edge of clock. Simply using the * will not work.

process statements in parallel


Sequential Example Cont 3

- What if we used blocking statements instead.
Notice the following results:


```

1 module shift2b(clk, D0, Q0, Q1);
2   input  clk, D0;
3   output Q0, Q1;
4   reg   Q0, Q1;
5   always @ (posedge clk)
6   begin
7     Q0 = D0;
8     Q1 = Q0;
9   end
10  endmodule

```

 

 The logic statements are simplified to $Q0 = Q1 = D0$. Logic is evaluated on rising edge of clk. Verilog is synthesized as one stage logic.



Summary

- **Combinational logic:** Use **blocking statements** with always blocks with the * operator to mimic logic flow of combinational logic.
- **Sequential logic:** Use **non-blocking statements** with always blocks sensitive to rising clock edge to mimic parallel sequential logic.

Modeling Finite State Machines with Verilog

- Finite State Machines can be modeled with three general functions:
 1. Next State Logic (combinational)


Combinational logic that determines next state based on current state and inputs.
 2. State Register (sequential)

Sequential logic that holds the value of the current state.
 3. Output Logic (combinational)

Combinational logic that sets the output based on current state.


FSM Example: A Simple Arbiter

 - Four inputs: reset, clock req_0 and req_1.
- Two outputs: gnt_0 and gnt_1.
- When req_0 is asserted and req_1 is not asserted, gnt_0 is asserted
- When req_1 is asserted and req_0 is not asserted, gnt_1 is asserted
- When both req_0 and req_1 are asserted then gnt_0 is asserted; in other words, priority is given to req_0 over req_1.



Modeling the Arbiter in Verilog

 - Identify the combinational and sequential components.
- Express each component as a combinational or sequential always block.




Arbiter Next State Always Block

```

always @*
begin
  case(state)
  IDLE : if (req_0 == 1'b1)
          next_state = GNT0;
         else if (req_1 == 1'b1)
          next_state = GNT1;
         else
          next_state = IDLE;
  GNT0 : if (req_0 == 1'b1)
          next_state = GNT0;
         else
          next_state = IDLE;
  GNT1 : if (req_1 == 1'b1)
          next_state = GNT1;
         else
          next_state = IDLE;
  default: next_state = IDLE;
  endcase
end

```

 Use this combinational always block to implement **state transition logic** with case and if-then-else constructs




Arbiter State Register Always Block

```

always @(posedge clock)
begin
  if (reset == 1'b1)
    state <= IDLE;
  else
    state <= next_state;
end

```

 

- The state register will be loaded with next_state from the next state logic on the rising edge of clock.
- Reset will set the state register to IDLE state on RESET and the rising edge of clock.


Arbiter Output Always Block

```

always @*
begin
  case(state)
  IDLE : begin
    gnt_0 = 1'b0;
    gnt_1 = 1'b0;
  end
  GNT0 : begin
    gnt_0 = 1'b1;
    gnt_1 = 1'b0;
  end
  GNT1 : begin
    gnt_0 = 1'b0;
    gnt_1 = 1'b1;
  end
  default : begin
    gnt_0 = 1'b0;
    gnt_1 = 1'b0;
  end
  end
endcase
end

```

 Use a combinational always block to implement logic output based on state.



Integrate Into One Module

Module and IO Declaration

```
module arbiter (clock, reset, req_0, req_1, gnt_0, gnt_1);  
    input clock, reset, req_0, req_1; // Input declarations  
    output gnt_0, gnt_1; // Output declarations  
    reg gnt_0, gnt_1;  
  
    parameter IDLE=3'b001; // State definitions  
    parameter GNT0=3'b010; // This example uses a one-hot encoding for its three  
    parameter GNT1=3'b100; // states. You can use a different encoding scheme.  
  
    reg [2:0] state; // Sequential variable to store the current state  
    reg [2:0] next_state; // Combinational variable used to calculate the next state
```

Next State Always Block

```
always @* // Combinational logic block  
begin  
    case(state)  
        IDLE : if (req_0 == 1'b1) // Implements transitions in state diagram  
                next_state = GNT0; // (see Fig. 2 for state diagram)  
            else if (req_1 == 1'b1)  
                next_state = GNT1;  
            else  
                next_state = IDLE;  
        GNT0 : if (req_0 == 1'b1)  
                next_state = GNT0;  
            else  
                next_state = IDLE;  
        GNT1 : if (req_1 == 1'b1)  
                next_state = GNT1;  
            else  
                next_state = IDLE;  
    default: next_state = IDLE;  
    endcase  
end // end of always @*
```

State Register Always Block

```
always @(posedge clock) // Sequential logic-implements flip-flops (with  
begin // reset) to store value of current state; reset  
    if (reset == 1'b1) // returns machine to initial state  
        state <= IDLE;  
    else  
        state <= next_state;  
    end // end of always @ (posedge clock)
```

Output Always Block

```
always @* // Output logic-determines outputs from current state  
begin  
    case(state)  
        IDLE : begin  
                gnt_0 = 1'b0;  
                gnt_1 = 1'b0;  
            end  
        GNT0 : begin  
                gnt_0 = 1'b1;  
                gnt_1 = 1'b0;  
            end  
        GNT1 : begin  
                gnt_0 = 1'b0;  
                gnt_1 = 1'b1;  
            end  
    default: begin  
                gnt_0 = 1'b0;  
                gnt_1 = 1'b0;  
            end  
    endcase  
end // end of always @ (state)  
endmodule
```