

Killing Two Birds with One Stone:

Learning to Write Better Verilog While
Learning About the SPI Bus.

And Error Correction
(Time allowing)

```
//-----
2 // Design Name : decoder_using_case
3 // File Name : decoder_using_case.v
4 // Function : decoder using case
5 // Coder : Deepak Kumar Tala (minor changes by Mark Brehob)
6 //-----
7 module decoder_using_case (
8 binary_in , // 3-bit binary input
9 decoder_out , // 8-bit out
10 enable // Enable for the decoder
11 );
12 input [3:0] binary_in ;
13 input enable ;
14 output [7:0] decoder_out ;
15
16 reg [7:0] decoder_out ;
17
18 always @ (enable or binary_in)
19 begin
20 decoder_out = 0;
21 if (enable) begin
22 case (binary_in)
23 3'h0 : decoder_out = 8'h01;
24 3'h1 : decoder_out = 8'h02;
25 3'h2 : decoder_out = 8'h04;
26 3'h3 : decoder_out = 8'h08;
27 3'h4 : decoder_out = 8'h10;
28 3'h5 : decoder_out = 8'h20;
29 3'h6 : decoder_out = 8'h40;
30 3'h7 : decoder_out = 8'h80;
31
32 endcase
33 end
34 end
35
36 endmodule
```

```
//-----  
2 // Design Name : decoder_using_assign  
3 // File Name : decoder_using_assign.v  
4 // Function : decoder using assign  
5 // Coder : Deepak Kumar Tala (Minor changes by Mark Brehob)  
6 //-----  
7 module decoder_using_assign (  
8 binary_in , // 3-bit binary input  
9 decoder_out , // 8-bit out  
10 enable // Enable for the decoder  
11 );  
12 input [2:0] binary_in ;  
13 input enable ;  
14 output [7:0] decoder_out ;  
15  
16 wire [7:0] decoder_out ;  
17  
18 assign decoder_out = (enable) ? (1 << binary_in) : 8'b0 ;  
19  
20 endmodule
```

```
1 //-----
2 // Design Name: 3 to 8 decoder
3 // Coder:         Deepak Kumar Tala (changes by Mark Brehob)
4 //-----
5 module decoder_using_assign (
6     input  [2:0]    binary_in,
7     input          enable,
8     output [7:0]    decoder_out
9 );
10
11     assign decoder_out = (enable) ? (1 << binary_in) : 16'b0 ;
12
13 endmodule
```

Option 1:

- `decoder_using_assign inst1(in, enable, out);`

Option 2a:

- `decoder_using_assign inst1(.binary_in(.in), .enable(enable),
 .decoder_out(out));`

Option 2b:

- `decoder_using_assign inst1(
 .binary_in (in), //input [2:0]
 .enable (enable), //input
 .decoder_out (out) //output [7:0]
);`

```
1 module sync_and_edges (
2     input          clk,
3     input          async_in,
4     output         sync_out,
5     output         rising_edge,
6     output         falling_edge
7 );
8     reg            [2:0]    tmp;
9
10    always@ (posedge clk)
11        tmp <= {tmp[1:0], async_in};
12
13    assign rising_edge    =tmp[2:1]==2'b01;
14    assign falling_edge  =tmp[2:1]==2'b10;
15    assign sync_cout     =tmp[1];
16 endmodule
```

So what does this code do?

```
always@ (posreg clk)
    tmp <= {tmp[1:0], async_in};
```

- It's just a shift register.


```
always@ (posreg clk) begin
    tmp[2] <= tmp[1];
    tmp[1] <= tmp[0];
    tmp[0] <= async_in;
end
```

Serial communication

- When working with an embedded system, one key thing is communicating with external devices:
 - Sensors
 - Actuators (e.g. motors)
 - Displays
- Some devices have their own unique protocols.
 - Servos are a common example
 - You control them via pulse-width modulation
 - Basically a fixed period with a variable duty cycle.

Example: Servos

Their own fairly unique protocol


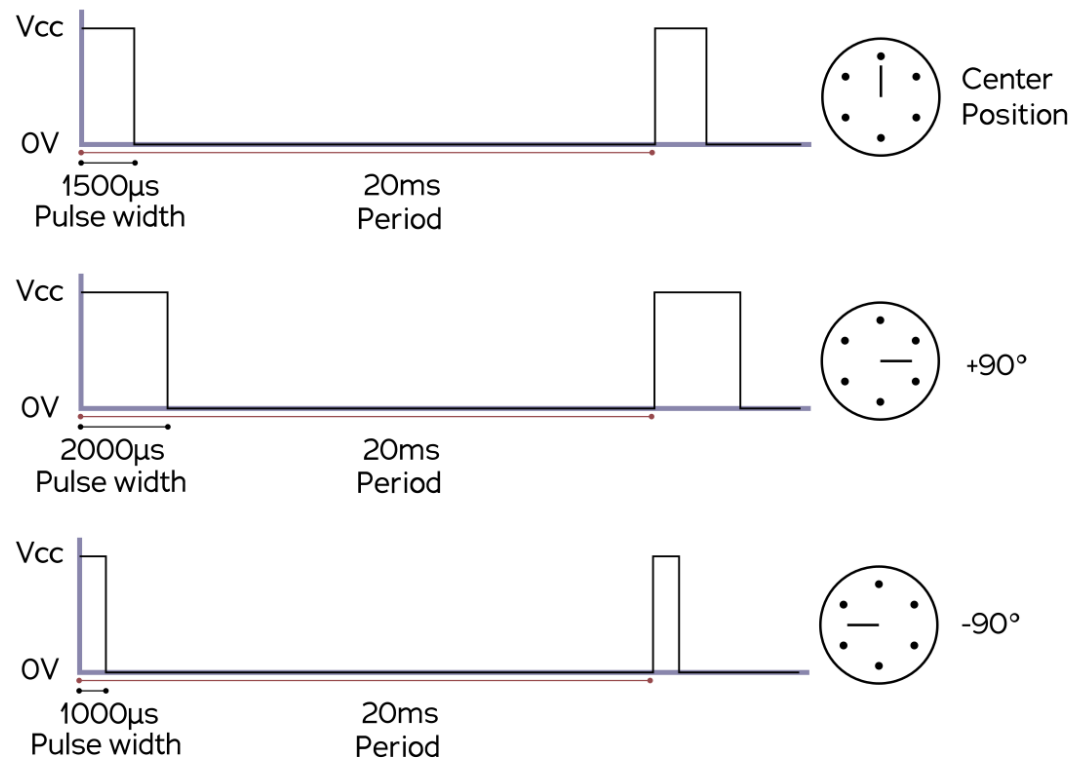


Standard interfaces

- There are three fairly standard interfaces in embedded systems
 - And a handful of others that see some use
- UART
 - Old protocol that was standard on PCs for years.
 - Most embedded systems that use USB really use UART and have a USB-to-UART converter chip.
- I2C
 - Fairly advanced protocol.
 - Addressable—each device has its own address and you can connect (in theory) dozens of devices to the same bus.


SPI—Serial Peripheral Interface

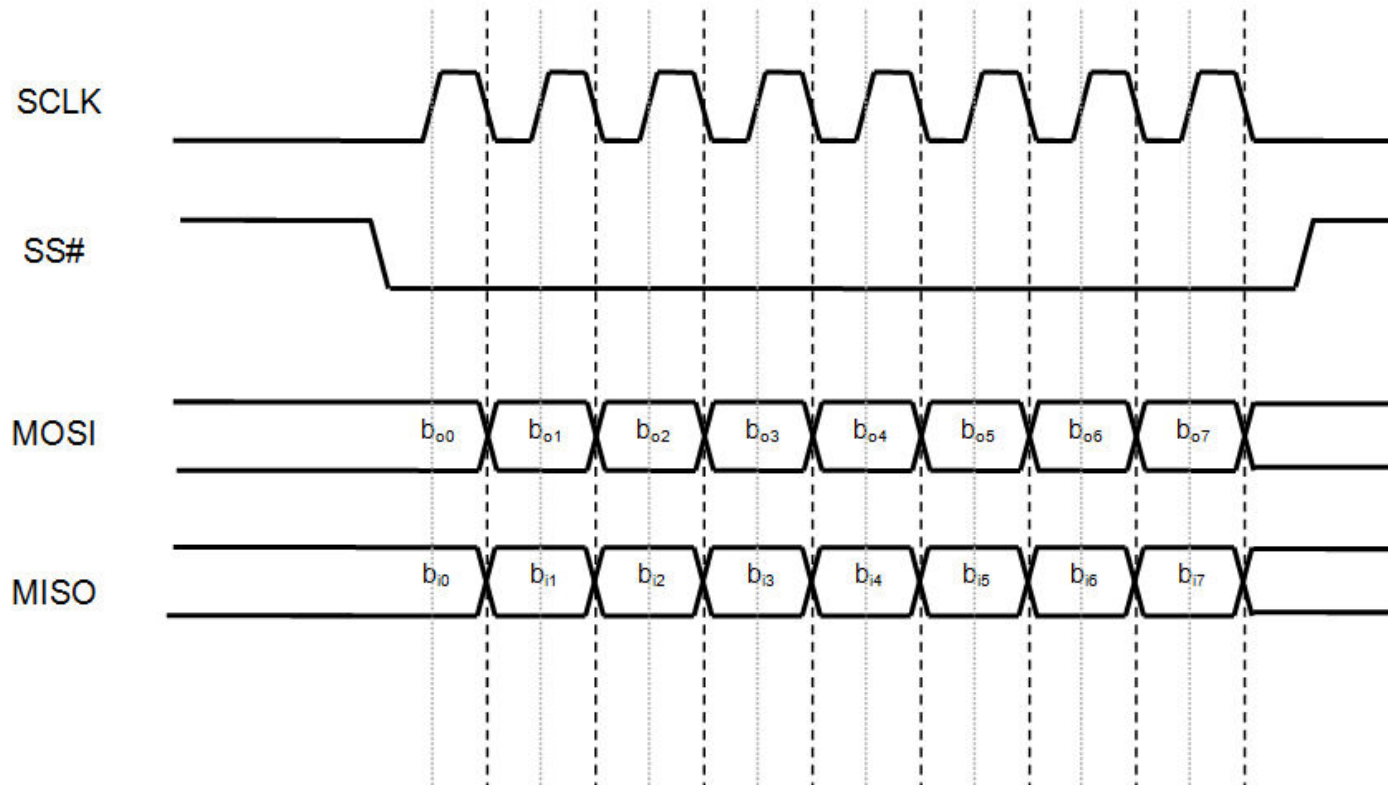 - 4 wires:
 - Clock
 - Data from master to servant
 - Data from servant to master
 - Select
- Runs in full duplex
 - Data goes both ways at the same time.
- Not really a standard, more of a hack.
 - So lots of weird issues to deal with as different people build slightly different interfaces...



What do we need to do?

Interface

 

```
1 module SPI_servant(  
2     input          clk,  
3     input          SCK,  
4     input          MOSI,  
5     input          SSEL,  
6     input          [7:0] SSW,  
7     output         MISO,  
8     output reg     [7:0] SLED  
9 );
```

Synchronize and edges

```
//*****  
// Get 3 versions of each SPI input:  
// Synchronized, rising edge, and falling edge.  
wire SCK_s, SCK_re, SCK_fe;  
wire MOSI_s, MOSI_re, MOSI_fe;  
wire SSEL_s, SSEL_re, SSEL_fe;  
  
sync_and_edges SCK_inst (clk, SCK, SCK_s, SCK_re, SCK_fe );  
sync_and_edges SSEL_inst(clk, SSEL, SSEL_s, SSEL_re, SSEL_fe);  
sync_and_edges MOSI_inst(clk, MOSI, MOSI_s, MOSI_re, MOSI_fe);
```

```
1 module sync_and_edges (  
2     input          clk,  
3     input          async_in,  
4     output         sync_out,  
5     output         rising_edge,  
6     output         falling_edge  
7 );  
8     reg            [2:0]    tmp;  
9  
10    always@(posedge clk)  
11        tmp <= {tmp[1:0], async_in};  
12  
13    assign rising_edge      =tmp[2:1]==2'b01;  
14    assign falling_edge    =tmp[2:1]==2'b10;  
15    assign sync_cout       =tmp[1];  
16 endmodule
```

Getting data

```
24 //*****
25 // Shift data in.  Could use a counter, but will assume
26 // the input is well-formed (SSEL low then 8 clocks then SSEL high)
27
28     reg    [7:0]    data_received;
29     always@(posedge clk)
30     begin
31         if(SSEL_s)
32             data_received<=data_received; // hold (just for clarity)
33         else if(SCK_re)
34             data_received<={data_received[6:0],MOSI_s};
35
36         if(SSEL_re)
37             SLED<=data_received; //once SS is high, data done.
38     end
```


Sending Data

```
40 //*****
41 // Send data out. We set data on falling edge. Need
42 // to be sure we have the right data at the start too.
43
44     reg    [7:0]    data_to_send;
45     assign MISO=SSEL_s?data_to_send[7]:1'bz;
46     always@(posedge clk)
47     begin
48         if(SSEL_fe)
49             data_to_send<=SSW; // grab data
50         if(SCK_fe)
51             data_to_send<={data_to_send[6:0],1'b0}; // shift on falling edge.
52     end
53
```


```

1 module SPI_servant(
2     input          clk,
3     input          SCK,
4     input          MOSI,
5     input          SSEL,
6     input          [7:0] SSW,
7     output         MISO,
8     output reg     [7:0] SLED
9 );
10
11
12 //*****
13 // Get 3 versions of each SPI input:
14 // Synchronized, rising edge, and falling edge.
15     wire SCK_s, SCK_re, SCK_fe;
16     wire MOSI_s, MOSI_re, MOSI_fe;
17     wire SSEL_s, SSEL_re, SSEL_fe;
18
19     sync_and_edges SCK_inst (clk, SCK, SCK_s, SCK_re, SCK_fe );
20     sync_and_edges SSEL_inst(clk, SSEL, SSEL_s, SSEL_re, SSEL_fe);
21     sync_and_edges MOSI_inst(clk, MOSI, MOSI_s, MOSI_re, MOSI_fe);
22
23
24 //*****
25 // Shift data in.  Could use a counter, but will assume
26 // the input is well-formed (SSEL low then 8 clocks then SSEL high)
27
28     reg [7:0] data_received;
29     always@(posedge clk)
30     begin
31         if(SSEL_s)
32             data_received<=data_received; // hold (just for clarity)
33         else if(SCK_re)
34             data_received<={data_received[6:0],MOSI_s};
35
36         if(SSEL_re)
37             SLED<=data_received; //once SS is high, data done.
38     end
39
40 //*****
41 // Send data out.  We set data on falling edge.  Need
42 // to be sure we have the right data at the start too.
43
44     reg [7:0] data_to_send;
45     assign MISO=SSEL_s?data_to_send[7]:1'bz;
46     always@(posedge clk)
47     begin
48         if(SSEL_fe)
49             data_to_send<=SSW; // grab data
50         if(SCK_fe)
51             data_to_send<={data_to_send[6:0],1'b0}; // shift on falling edge.
52     end
53
54 endmodule

```

One more application: Error correction

 - Say we are storing data (or communicating with it)
 - Sometimes it goes bad.
 - Why?
- How can we recover it?
 - Have some redundancy!
- But keeping a copy of the data is too much.
 - I don't want 100% overhead!



Example block code:

Hamming(7,4)

- Hamming(7,4)-code.
 - Take 4 data elements (d_1 to d_4)
 - Add 3 parity bits (p_1 to p_3)
 - $p_1 = P(d_1, d_2, d_4)$
 - $p_2 = P(d_1, d_3, d_4)$
 - $p_3 = P(d_2, d_3, d_4)$
 - If any one bit goes bad (p or d) can figure out which one.
 - Just check which parity bits are wrong. That will tell you which bit went wrong.
 - If more than one went wrong, scheme fails.
- Much more efficient on larger blocks.
 - E.g. (136,128) code exists.
- Example:
 - Say
 - $d[1:4] = 4'b0011$
 - Then:
 - $p_1 = P(0,0,1) = 1$
 - $p_2 = P(0,1,1) = 0$
 - $p_3 = P(0,1,1) = 0$
 - If d_2 goes bad (is 1)
 - Then received p_1 and p_3 are wrong.
 - Only d_3 covered by both (and only both)
 - *So d_3 is the one that flipped.*