

EECS 270 Midterm

Spring '05, Prof. Mark Brehob

Name: _____ uname: _____

Sign the honor code:

I have neither given nor received aid on this exam.

Scores:

#	Points
1	/15
2	/15
3	/15
4	/15
5	/20
6	/15
7	/5
Total	/100


NOTES:

- This exam will last 120 minutes.
- Throughout this exam * = AND, +=OR, !=NOT \oplus = XOR
- Open book (our text only!), open notes. No computers, cell phones, or other communication devices.


1. Using a K-map find the minimal product-of-sums for $\Pi_{WXYZ}=(3,4,5,7,9,14,15)+d(10,13)$. Put a star in each of the distinguished one-cells.
[15]

2. Functionality of latches and flip-flops

 a. Show the values of Q and QN for an SR latch with the following inputs. [9]




 
b. Show the value of the output of a D-flip-flop given the following input. You should assume the initial value of Q is 0. [6]



3. Find the *minimal sum-of-products* of the following logic equation using the Quine-McCluskey algorithm. You must ***clearly*** show your work for credit, using the algorithm as discussed in class. Solving the problem in some other way will result in 0 points. **[15]**

$$\Sigma_{wxyz}=(0,1,12,13,15)+d(4,14)$$

  
4. Analyze the following circuit by showing the values at nodes L1 and L2 at each step. Assume both latches are initially outputting zero. The boxes are D latches. [15]



L1


L2

 5. Consider a device (named DIFF) which takes two 4 bit *unsigned* numbers as input and outputs a 4 bit unsigned number which is equal to the larger of the two minus the smaller of the two. So for example, if 12 and 4 were the two binary numbers provided as input, the output would be 8.
- a. What would be the output (in binary) if the two inputs were 1000 and 0011?
[2]
 - b. Design a circuit that computes the result of taking the larger minus the smaller value. 4-bit unsigned binary numbers. You should write your solution on the following page and use the notation for the inputs and outputs provided below. A3, B3, and D3 are the most significant bits. You may use: [18]
 - AND gates, OR gates, XOR gates as well as NOT gates
 - 4-bit adders (inputs and output are both 4-bits) with carry-in and carry-out.
 - 8 to 3 encoders (all wires active high)
 - 3 to 8 decoders (all wires active high)
 - 4-bit unsigned comparator (all wires active high, has an EQ and GT output)
 - 2 to 1 MUXes (all wires active high)
 - 8 to 4 MUXes (all wires active high)



(This page left blank to give you space for your answer to the previous problem)

 6. Consider a device that takes as input a 4-bit 2's complement number and outputs a 6-bit 2's complement number that is equal to twice the input value. So if the input were -1 as a 4-bit 2's complement number, the output should be -2 as a 6-bit 2's complement number.
- If the input were 0010 what should the output be (in binary)? [2]
 - If the input were 0110 what should the output be (in binary)? [2]
 - If the input were 1010 what should the output be (in binary)? [2]
 - Using only AND, OR, NOT, and XOR gates, design a circuit which implements the above function. Use the naming convention found in the figure below. A3 and T5 are the most significant bits. [9]



7. If the 74x153 has the following input values:
- A, 1G, 1C0, 1C2, 2G and 2C1 are all zero
 - All other inputs are one
- What is the value of 1Y and 2Y? **[5]**