

Quiz 2 – Spring 2022 – EECS 270

Name: _____ uname: _____

This quiz is graded out of 100 points and is worth about 4% of your class grade. You will have 20 minutes for this quiz. Closed everything including calculators! To receive partial credit, work must be shown.

1. Write the **canonical *product-of-sums*** for the following truth table. [20 points]

X	Y	Z	A
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0


A= _____

Notice this is Product-of-Sums!


2. Fill-in-the-blank [20 points, -5 for each wrong or blank answer]

- The time *before* the rising edge of the clock when no input should be changing is called the _____
- _____ is -9 as an 8-bit 2's complement number
- A signal with a frequency of 100MHz has a period of _____ ns
- $(A*B)+(A*C) =$ _____ according to the distributive theorem.

 
3. Complete the following timing diagrams. If the value is unknown (or oscillating) at some point, clearly indicate that with hashes (as shown).



 
- a) Complete the timing diagram below for an SR latch with enable. **[10 points]**



 - b) Complete the timing diagram below for both a D latch and a D flip-flop. **[20 points]**



4.

 

Draw flip-flops and gates which implement the above state transition diagram. All flip-flops are set to 0 when the system is initialized (to the initial state should be where the flip-flop(s) are zero).

Your answer will be graded in part on clarity and simplicity. **[30 points]**