

Quiz 3 – EECS 270, Spring '22

Name: key unique name: key

Honor code:


I have not given or received aid on this quiz, nor have I observed anyone else doing so:

Sign here: _____

This quiz is graded out of 100 points and is worth about 3% of your class grade. You will have 20 minutes for this quiz. **Closed everything including calculators!** To receive partial credit, work must be shown.


1. Find the minimum product-of-sums of $\sum_{(a,b,c,d)=(2,4,6,9,10,12,13)+d(11,15)}$ using a K-map. Show your work and clearly circle your answer. [40]

note: this is Product-of-sums!!!

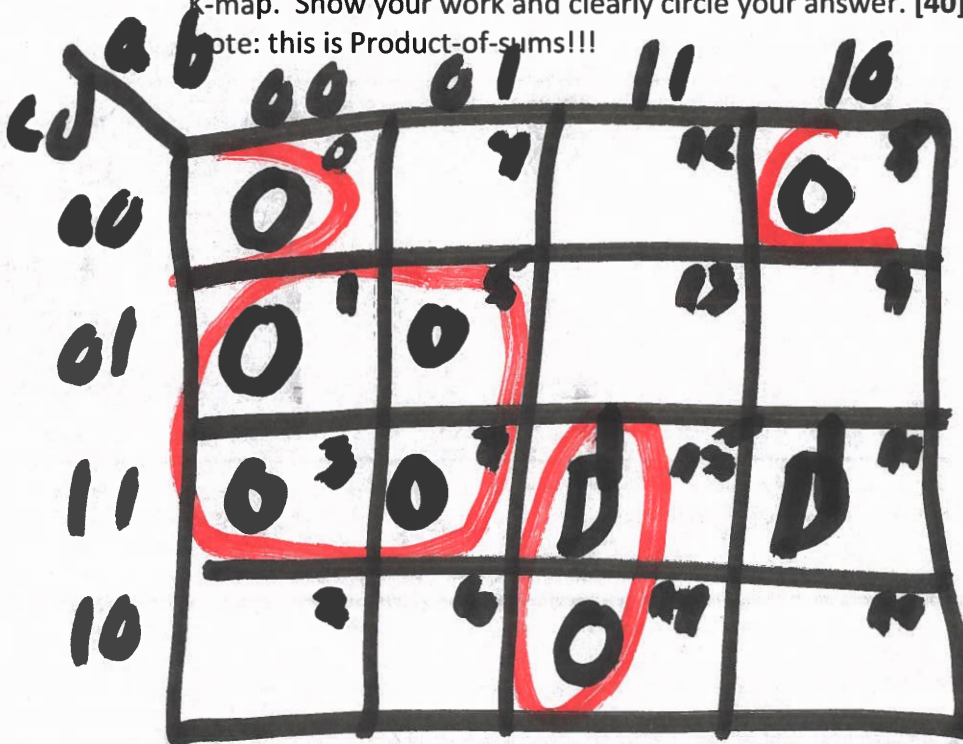

$$(b+c+d) \cdot (a+d) (\bar{a} + \bar{b} + \bar{c})$$

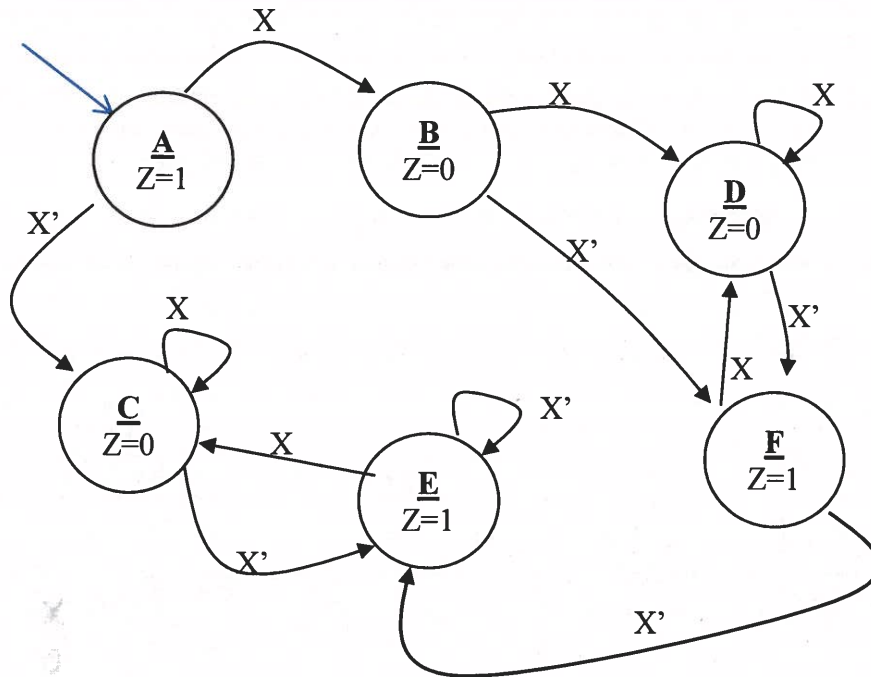2. Reduce the number of states in the state transition diagram as much as possible using the partitioning method. Show your work and draw the reduced state diagram. [60 points]



Final result has 3 states: A, BCD, EF.

A	BCD				
B	BCD	BCD			
C	BCD	BCD	EC FD		
D	BCD	BCD	FD FD	FD EC	
E	EC ED	BCD	X	X	X
	F	A	B	C	D