

Name: Key unique name: Key


Honor code:

I have not given or received aid on this quiz, nor have I observed anyone else doing so:

Sign here: Key

This quiz is graded out of 100 points and is worth about 4% of your class grade.

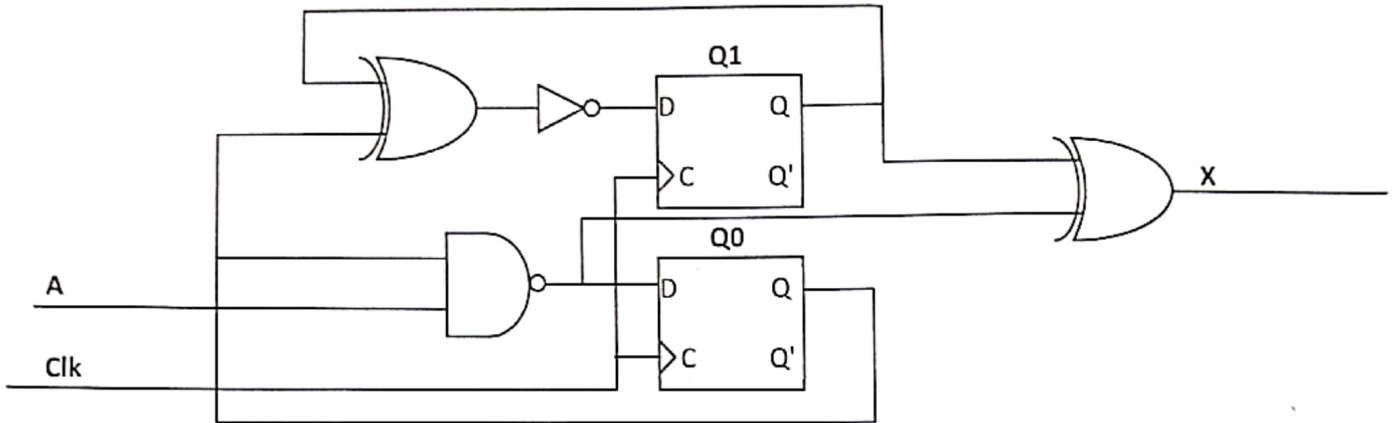Closed everything including calculators! To receive partial credit, work must be shown.




- 1) Draw the state transition diagram for the above circuit. You should assume "00" is the initial state. Please label each state as "Q1Q0" (so if Q1=1 and Q0=0 the label would be "10"). Don't include unreachable states (if any). [50]

$$D_1 = \overline{Q_0 \oplus Q_1}$$

$$D_0 = \overline{A \cdot Q_0}$$

$$X = (\overline{A \cdot Q_0}) \oplus Q_1$$

Q ₁	Q ₀	A	D ₁	D ₀	X
0	0	0	1	1	1
0	0	1	1	1	1
0	1	0	0	1	1
0	1	1	0	0	0
1	0	0	0	1	0
1	0	1	0	1	0
1	1	0	1	1	0
1	1	1	1	0	1

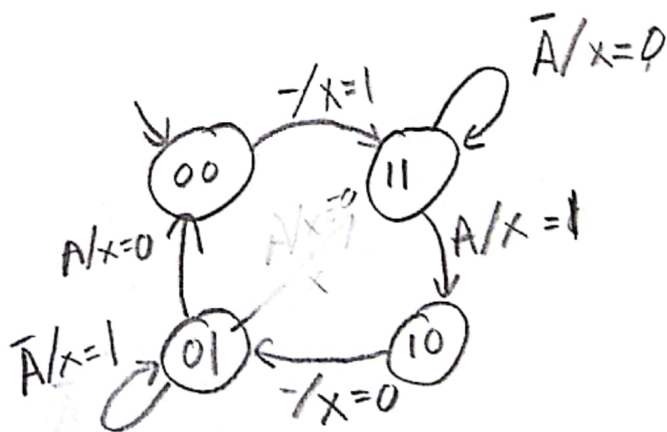

2) Find the minimal sum-of-products of F using the Quine-McClusky algorithm. For this problem we'll be grading your answer primarily based on your work so be sure to be careful, clear and neat. Use the format provided. [50]

$$F = \sum_{A,B,C,D}(0,5,8,10,11,14,15)$$

	Column I	✓
0	0000	✓
8	1000	✓
5	0101	
10	1010	✓
11	1011	✓
14	1110	✓
15	1111	✓

	Column II	✓
0,8	X000	
8,10	10X0	
10,11	101X	✓
11,15	1X11	✓
14,15	111X	✓
10,14	1X10	✓

	Column III	✓
10,11,14,15	1X1X	
	1X1X	

List of Prime Implicants (Provide in the form AB, AC', D)

$\bar{A}\bar{B}\bar{C}D, \bar{B}\bar{C}D, A\bar{B}D, AC$

1010
1110

List of distinguished ones (provide the binary value of each distinguished one):

0000, 0101, 1011, 1110, 1111

Minimal sum-of-products: $\bar{A}\bar{B}\bar{C}D + \bar{B}\bar{C}D + AC$

