

# EECS 270 *Practice* final

Spring '04, Prof. Mark Brehob

Name: \_\_\_\_\_ UM ID: \_\_\_\_\_

Sign the honor code:

~~I have neither given nor received aid on this exam.~~

Scores:

#	Points
1	/18
2	/25
3	/20
4	/15
5	/12
6	/10
<b>Total</b>	<b>/100</b>

## NOTES:

- This exam is intended to be taken in 120 minutes.
- Throughout this exam \* = AND, +=OR, !=NOT  $\oplus$  = XOR
- Open book, open note.

1. Short answer [18]

- a. Using only 2-input AND, OR, and XOR gates as well as inverters draw a circuit which takes 6 bits as an input and outputs a 1 if the parity of those bits is odd. Label the inputs as I[0:5] and the output as “Odd\_P”. Your solution must have 8 or less gates (including the inverters). [5]

- b. Using only T flip-flops and standard gates, design a device which divides a clock by 8 and has a duty cycle of  $1/8^{\text{th}}$ . [8]

c. Fill-in-the-blank [5]

- i. What is the clock frequency if the clock period is 20ns?

\_\_\_\_\_

- ii. What is the difference between DRAM and SRAM?

\_\_\_\_\_

- iii. Write the number  $23_{16}$  as a binary number \_\_\_\_\_

- iv. Exactly how many *bits* of memory are in 1 Kbyte of RAM? provide a number (with no units)

\_\_\_\_\_

- v. Write  $10.01_2$  as a base 10 number. \_\_\_\_\_

2. Consider a state machine that has one input (I) and one output (X). X is to go high whenever the last 4 values of “I” were “1010”. An example input/output pair follows. [25]

I= 01010011001010100011  
X= 00001000000001010000

- a. Is this a Mealy or Moore machine? Briefly explain. [2]
- b. Design a *state transition diagram* for this machine. [13]
- c. Design the state machine using AND, OR, XOR and NOT gates (or inversion bubbles) and D flip-flops [10]

3. A circuit has three inputs and two outputs. The two inputs,  $I[1:0]$  represent the number  $N$  and  $I_1$  is the most significant bit of that number. The two outputs,  $Z[1:0]$  are to be assigned as follows. If the current  $N$  is less than the previous  $N$  then  $Z_0=1$ . If the current  $N$  is greater than the previous  $N$  then  $Z_1=1$ . Otherwise  $Z_0=Z_1=1$ .


a. Draw a Mealy state diagram which performs this task. Clearly label your states. [10]

b. Draw a Moore state-diagram which performs this task. Clearly label your states. [10]


4. MSI Logic and minimization **[15]**

You are to find the minimal product-of-sums for a two-bit adder. The adder takes two 2-bit inputs ( $A[1:0]$  and  $B[1:0]$ ) and generates a 2-bit output  $Z[1:0]$  and a carry-out bit  $C_{out}$ .  $A_1$ ,  $B_1$ , and  $C_1$  are all the most significant bits. You are to use K-map(s) and clearly show your work.

 5. Draw the state machine that corresponds to the following circuit. Label your states in terms of the flip-flops values in the order (Q1,Q2). Be sure to include all states. [12]



 6. Fill in the following truth table with either “1”, “0” or “HiZ” [10]



A	B	C	Out
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

