

EECS 470 Lab 5

SystemVerilog

Department of Electrical Engineering and Computer Science
College of Engineering
University of Michigan

Thursday, February 8th, 2024

Overview

Administrivia

Motivation

Multidimensional Arrays

Unique and Priority

Assertions

For Loops

Generate Blocks

Lab Assignment

Crazy times are here

Homework

- ▶ HW 3 is due is next Wednesday, February 14th

Exam

- ▶ Exam is next Thursday, February 15th

Project

- ▶ Project proposals due Tuesday, February 13th
- ▶ Group meetings Thursday and Friday, February 15th -16th
- ▶ Then 3 weeks (one of which is Spring break) until milestone 1 meetings

Project 2 Feedback

Implementations + Style

- ▶ Give every signal a default value in `always_comb` blocks
 - ▶ Do this before you write anything else
 - ▶ This makes avoiding latches easy
- ▶ Be very aware of how your Verilog translates to hardware
 - ▶ Ex: If you use “*”, that makes a (very expensive) multiplier

Free Response

- ▶ Each pipeline stage requires overhead (setup + hold time, wiring)
- ▶ You should be able to analyze the latency of your module
 - ▶ Understand the latency associated with your design choices
 - ▶ Don't rely on Verdi to tell you how long something takes to compute

Motivation

Why SystemVerilog? Why now?

- ▶ Extra features that will be useful in your projects
- ▶ Not all features are easy to use: many have a steep learning curve
- ▶ The goal isn't to go wild and try to use everything...
- ▶ Instead, think about which are worthwhile to incorporate

What is SystemVerilog?

1. 1995 – Verilog HDL
2. 2001 – Verilog 2001
3. 2005 – SystemVerilog
 - ▶ Emphasis on creating a combined Hardware Description Language and Hardware Verification Language
 - ▶ Ability to debug at the “system” level
 - ▶ Provides the basis for very powerful, object-oriented testbenches
 - ▶ The framework for industry verification tools, e.g. UVM

Multidimensional Arrays

Example

- ▶ `logic [127:0] [63:0] multi_d_array [3:0];`
- ▶ `assign multi_d_array[3][101] = 64'hFFFF_FFFF;`

Explanation

- ▶ “[127:0]” and “[63:0]” are called “packed” dimensions
- ▶ “[3:0]” is an “unpacked” dimension
- ▶ When referencing for read/write, unpacked dimensions come first, then packed dimensions
- ▶ Related to how the wires get laid out in hardware

Multidimensional Arrays

Example

- ▶ `logic [127:0] [63:0] multi_d_array [3:0];`
- ▶ `assign multi_d_array[3][101] = 64'hFFFF_FFFF;`

Explanation

- ▶ Old Verilog only allows one packed dimension
- ▶ SystemVerilog allows as many as you need
- ▶ We recommend packed arrays for most designs

Multidimensional Arrays

Example

- ▶ `logic [31:0] one_d_array;`
- ▶ `logic [15:0] [1:0] two_d_array;`
- ▶ `assign two_d_array = one_d_array;`

Explanation

- ▶ Packed arrays are laid out as a contiguous set of bits
- ▶ Allows easy copying from one array to another

Unique/priority if/case


```
input a, b, c;
input [1:0] sel;
output z;
case (sel)
    2'b00: z = a;
    2'b01: z = b;
    2'b10: z = c;
endcase
```

How will the synthesis tool convert this design to hardware?

Unique/priority if/case

```
input a, b, c;
input [1:0] sel;
output z;
case (sel)
    2'b00: z = a;
    2'b01: z = b;
    2'b10: z = c;
endcase
```

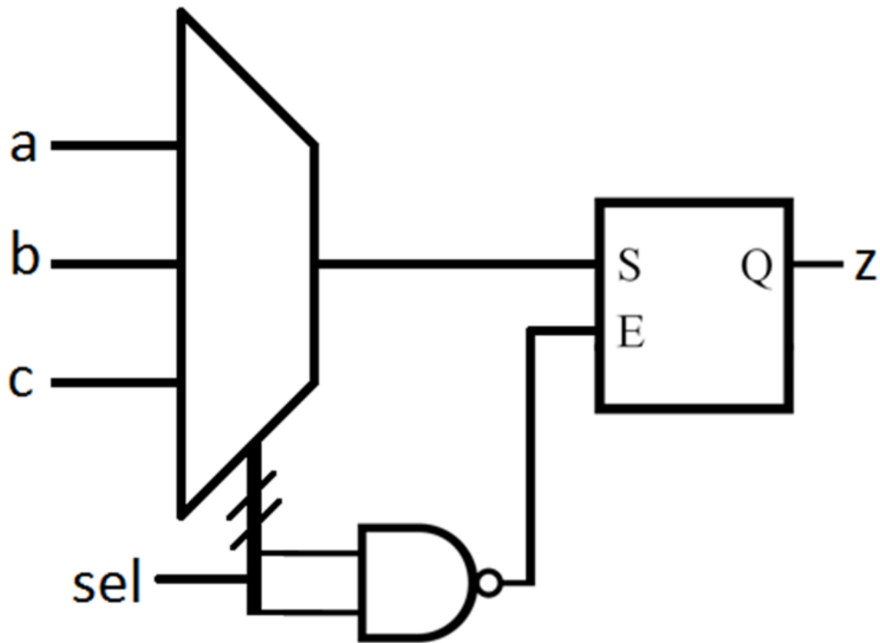A latch will be generated, since a value for z was not specified when `sel == 2'b11`



Unique/priority if/case

What if you know sel will never equal 2'b11?

- ▶ You could add a dummy state, but that adds unnecessary logic and potentially hides errors
- ▶ SystemVerilog has a “priority” construct for exactly this problem
 - ▶ Tells synthesis tool not to generate a latch
 - ▶ Checks at run-time that each state is reachable

Unique/priority if/case

```
input a, b, c;
input [1:0] sel;
output z;
priority case (sel)
    2'b00: z = a;
    2'b01: z = b;
    2'b10: z = c;
endcase
```

During behavioral simulation, if sel is 2'b11, a warning will be generated:

RT Warning: No condition matches in priority case statement.

Unique/priority if/case

Another code example:

```
input [1:0] sel;
output logic [1:0] z;
if (sel[1])
    z = a;
else if (sel[0])
    z = b;
else
    z = c
```

What hardware will be generated by this code?


Unique/priority if/case

Another code example:

```
input [1:0] sel;
output logic [1:0] z;
if (sel[1])
    z = a;
else if (sel[0])
    z = b;
else
    z = c
```

Tool will give priority to higher bits, since it assumes multiple bits could be high?

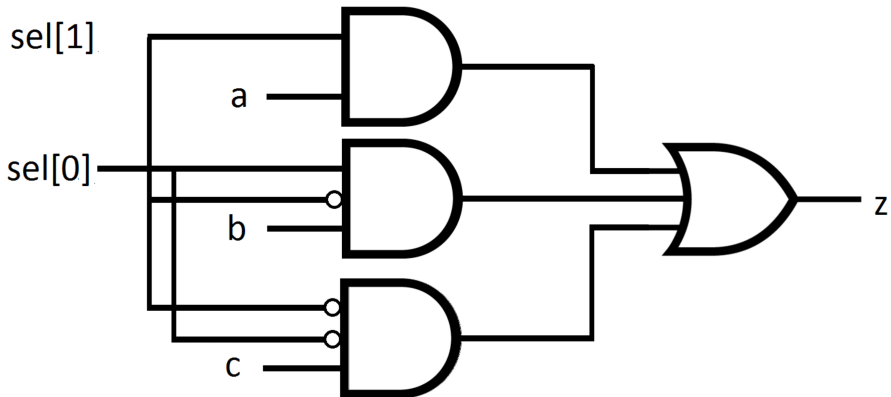- ▶ But what if we're using one-hot encoding?



Unique/priority if/case

SystemVerilog has “unique” if/case statement

```
input [1:0] sel;
output logic [1:0] z;
unique if (sel[1])
    z = a;
else if (sel[0])
    z = b;
else
    z = c
```

- ▶ Tells synthesis tool to assume one-hot encoding
- ▶ Ignores priority logic and doesn't generate any latches
- ▶ Generates simulation warning if multiple bits are high

Unique/priority if/case

Unique & Priority used for both if and case statements

- ▶ Replaces “full_case” and “parallel_case” pragmas from old Verilog
- ▶ Useful for simplifying logic and clarifying design choices

Assertions

Assertions

- ▶ Strategy for automated testing: check that certain conditions are true
- ▶ Statements declaring some kind of invariant
- ▶ Can be inserted in testbenches or RTL (ignored by synthesis)
- ▶ Two types:
 - ▶ Immediate: directly called in code
 - ▶ Concurrent: running in background

Immediate Assertions

Need to check that some expression is true...

```
adder a1(a, b, c);  
initial begin  
    if ((a+b) != c)  
        $display("Error!");  
end
```

Better done by immediate assertion...

```
adder a1(a, b, c);  
initial begin  
    assert ((a+b) == c);  
end
```

Concurrent Assertions

- ▶ Idea: Embed invariants about your design in the module itself
- ▶ Verify your design automatically every clock cycle!
 - ▶ Describe high-level functional correctness of your design...
 - ▶ ...and have simulator check these invariants in the background
- ▶ Very helpful for documenting your design
 - ▶ Describe what should be true at all times
 - ▶ Lay out sequences of events that should occur
- ▶ Makes writing a testbench much simpler
- ▶ SystemVerilog supports an entire assertion language (!)
 - ▶ Very powerful, but can be confusing

Assertion Syntax Basics

- ▶ Clocked behavior
 - ▶ `@(posedge clock) disable iff(reset)` : examine at every positive clock edge, except if reset is high
 - ▶ `clocking cb @(posedge clock) ... endclocking` : Everything in this block should be evaluated at the positive clock edge
- ▶ Implication
 - ▶ `s1 |-> s2`: If s1 is true, then s2 must also be true *at the same time*
 - ▶ `s1 |=> s2`: If s1 is true, then s2 must also be true the *next cycle*
- ▶ Timing windows
 - ▶ `(a && b) |-> ##[1:3] c;`
 - ▶ If a and b are true, then 1-3 cycles later, c must be true
 - ▶ `int x; (a, x=data) ##[1:$] c`
 - ▶ when a is true, save data to x and then wait $[1, \infty)$ cycles until c

Assertions

Assertions

- ▶ For more information on assertions, check out “[A Practical Guide to SystemVerilog Assertions](#)”
- ▶ An example set of assertions is used to test lab 5. See the source code for the example

“For” loops

“You want ‘for’ loops? You can’t handle ‘for’ loops!”

- ▶ We told you earlier in the semester that “for” loops are not a thing
- ▶ We lied, sort of... but they don’t work the way they do in software
- ▶ In software we think about iterations of loops
 - ▶ Iteration 1, then Iteration 2, then Iteration 3... etc...
- ▶ In hardware, loops need to unroll completely at design time
 - ▶ Self-modifying hardware is still not a thing...
 - ▶ So either everything runs in parallel (good)
 - ▶ Or loop can “break” when a certain condition is true (can get ugly)

For loops

Does this make sense for actual hardware?

```
parity = 0;
for (int i=0; i<32; i++) begin
    if (in[i])
        parity = ~parity;
end
```

For loops

Designing synthesizable “for” loops

- ▶ “For” loops can be valuable, just different than software
 - ▶ Just another way of doing combinational logic, not a replacement for sequential logic
 - ▶ Very limited ability to change signals referenced in the loop
- ▶ Great for condensing repetitive code, because everything will be done in parallel
- ▶ Visualize how a loop can be built into hardware at synthesis time

For loops

Blocking assignment in loops

```
always_comb begin
    for (int i=0; i<32; i++)
        a = i;
end
```

- ▶ What will a equal?
- ▶ 31, because if we unrolled the loop, the assignment to 31 would be last

For loops

Break Statements

```
always_comb begin
    for (int i=0; i<32; i++)
        a = i;
        if (condition[i]) break;
end
```

- ▶ Effect: break out of loop once condition is true

For Loops

wor and wand

- ▶ For loops lend themselves to another type of wire: `wor` and `wand`
- ▶ Those wire types allow you to do multiple assignments to one signal
- ▶ The final value will be the logical OR (for `wor`) or AND (for `wand`) of all assignments.

Index Part-Select

- ▶ “-:” and “+:” are shorthand for selecting based by an index and width
- ▶ Syntax: `signal[<start>+:<width>]` or `signal[<end>-:<width>]`
- ▶ Example: `array[WIDTH*i+:WIDTH]` takes the bits from `WIDTH*i` to `WIDTH*(i+1)-1`

For loops

Max loop iterations

- ▶ Design Compiler sets a maximum number of loop iterations to prevent infinite loops
 - ▶ This is configured to be 1024 by default
 - ▶ If you need more, add this line to your .tcl file:
`set hdlin_while_loop_iterations (iterations)`

Final advice

- ▶ Remember: don't use Verilog as a way to avoid thinking about actual hardware
 - ▶ This results in synthesis problems or overly complex designs
- ▶ First think about how to build the hardware, then think about the Verilog constructs that can allow you to describe your design easily

Generic Designs

Goal: complex designs with a single parameter

- ▶ Want to make designs where we can easily change certain features
 - ▶ For example, the number of ROB entries
- ▶ The multiplier in P2 could be modified using parameters
- ▶ We can build complex designs... remember module arrays?

```
one_bit_adder add_8 [7:0] (  
    .a(a), .b(b), .cin({carries, cin}),  
    .sum(sum), .cout({cout, carries}));
```

- ▶ What if we couldn't condense everything to a single parameter?
 - ▶ An adder is simple, just an array of smaller adders
 - ▶ What about more complex structures like the priority selectors from P1 that are trees of smaller selectors?

Generate Blocks

Generate blocks give control

- ▶ Using a generate block to build hardware:

```
generate
  genvar i;
  for (i=0; i<N; i++) begin
    one_bit_adder add_8 (
      .a    (a[i]),
      .b    (b[i]),
      .cin  (carries[i]),
      .sum  (sum[i]),
      .cout(carries[i+1]));
  end
endgenerate
```

Generic Designs

Goal: complex designs with a single parameter

- ▶ How does this work?
 - ▶ The tool will “elaborate” the design
 - ▶ Evaluate “if” statements and unroll “for” loops
- ▶ Important: all conditions must be deterministic at compile time

Generate Blocks

Another example: the Priority selectors from P1:


```
generate
  genvar i;
  for (i=0; i<N; i++) begin
    localparam left_right = i[0];

    ps2 ps_i (
      .req      (sub_reqs[i]),
      .en       (sub_gnts[i/2][left_right])
      .gnt      (sub_gnts[i]),
      .req_up   (sub_reqs[i/2][left_right]));
  end
endgenerate
```

Lab Tips

- ▶ Circular Buffers aka FIFOs are used all over the place in HW design
 - ▶ Any time you need to buffer data from source to destination
 - ▶ Storing stalled requests until hazards are resolved
 - ▶ Also a very common interview question
- ▶ Goal: design a generic FIFO that you can reuse in your final project
- ▶ Key parameters:
 - ▶ Depth: how many entries are in the FIFO
 - ▶ Width: # bits in each entry
 - ▶ Alert depth: when to send an alert that the buffer is almost full
- ▶ Nuances:
 - ▶ Head and tail need to wrap around ("circular" buffer)
 - ▶ How do you track empty, full, and almost full?

Lab Diagram

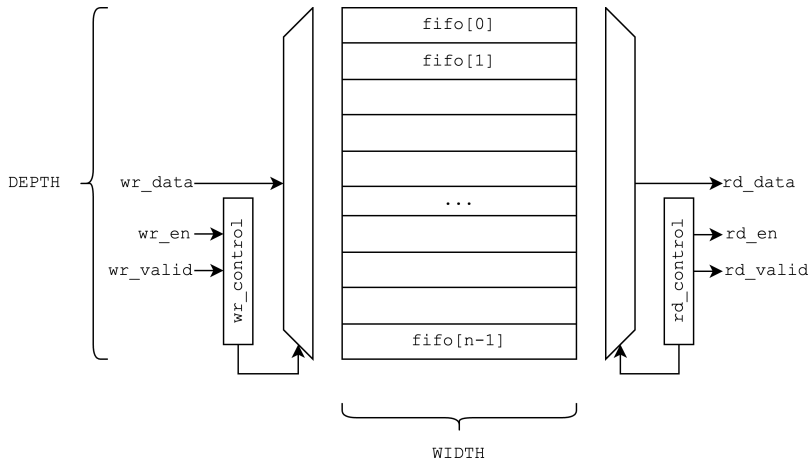

Design Decisions

- ▶ One-hot vs encoded read/write pointers:
 - ▶ Encoded is more space efficient and easier to read/use
 - ▶ One-hot is faster (addition is just a shift) but requires more area
- ▶ Options for differentiating empty and full states:
 - ▶ Keep a separate count for number of entries
 - ▶ Track which entries are valid or not
 - ▶ Have one extra bit for full vs empty
 - ▶ Make it so you always have at least one empty slot
- ▶ How do you drive the read data?
 - ▶ Does this need to be combinational or sequential?
 - ▶ Does it need to be 0 when data is invalid?
- ▶ What if you need to do multiple reads and writes per cycle?
 - ▶ This isn't part of the lab, but may be needed for superscalar processors

Lab Assignment

- ▶ Assignment is posted to the course website as **Lab 5 Assignment**.
- ▶ **NOTE:** we are giving you two weeks for this one because it is more challenging
- ▶ If you get stuck. . .
 - ▶ Ask a neighbor, quietly
 - ▶ Put yourself in the **help queue**
- ▶ When you finish the assignment, sign up in the **help queue** and mark that you would like to be checked off.
- ▶ If you are unable to finish today, the assignment needs to be checked off by a GSI/IA in office hours *before* the end of next week.